 


# Lecture X

## Final Review


吳文中

# “States” in a Circuit




Control of an alarm system.



# A Basic Latch Built with NOR Gates

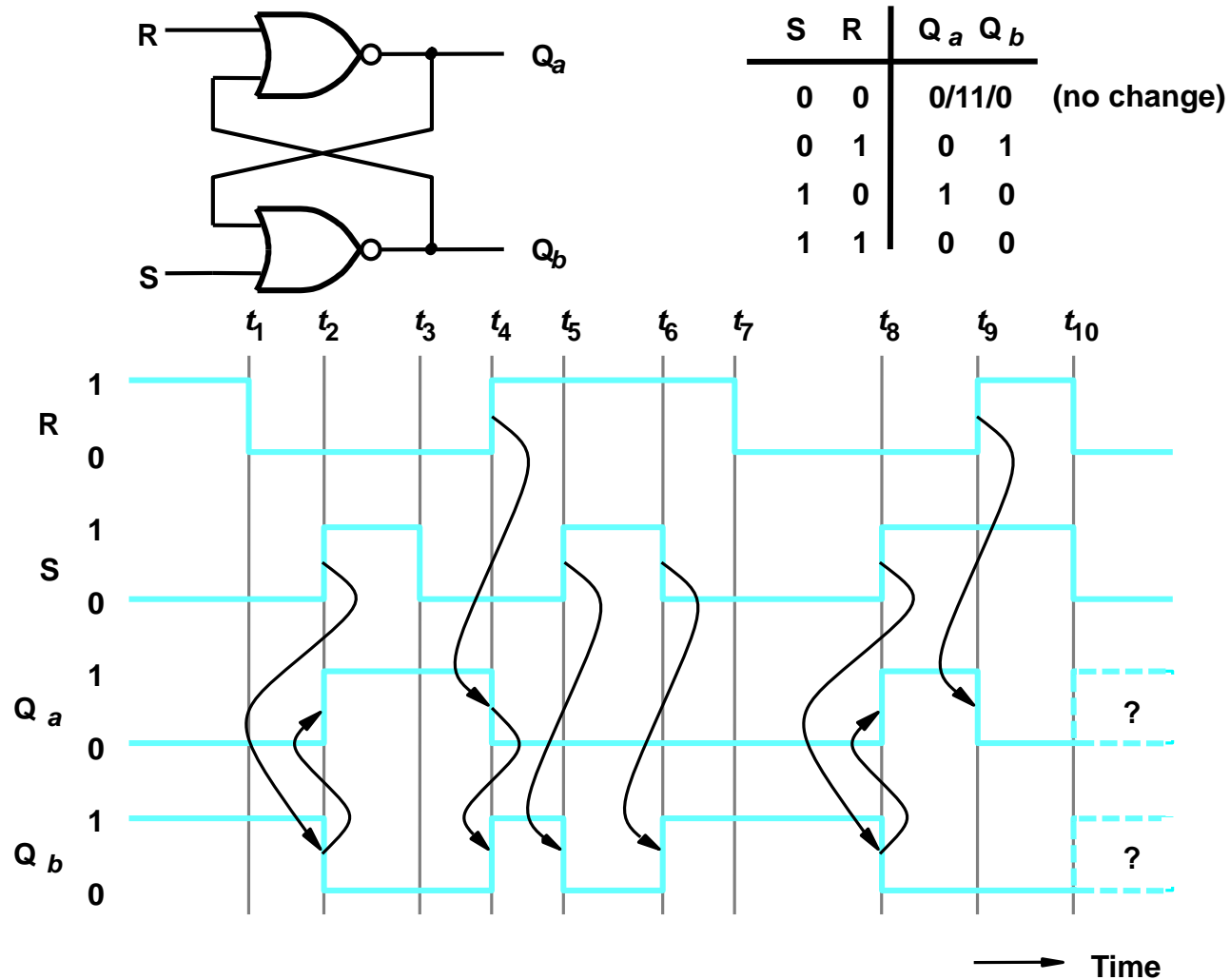


# Gated SR Latch

 

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

  


# Gated SR Latch with NAND Gates


 


Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x




# Gated D Latch

 

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

 
 


# Master-Slave D Flip-Flop

   

# A Positive-edge-triggered D Flip-Flop

 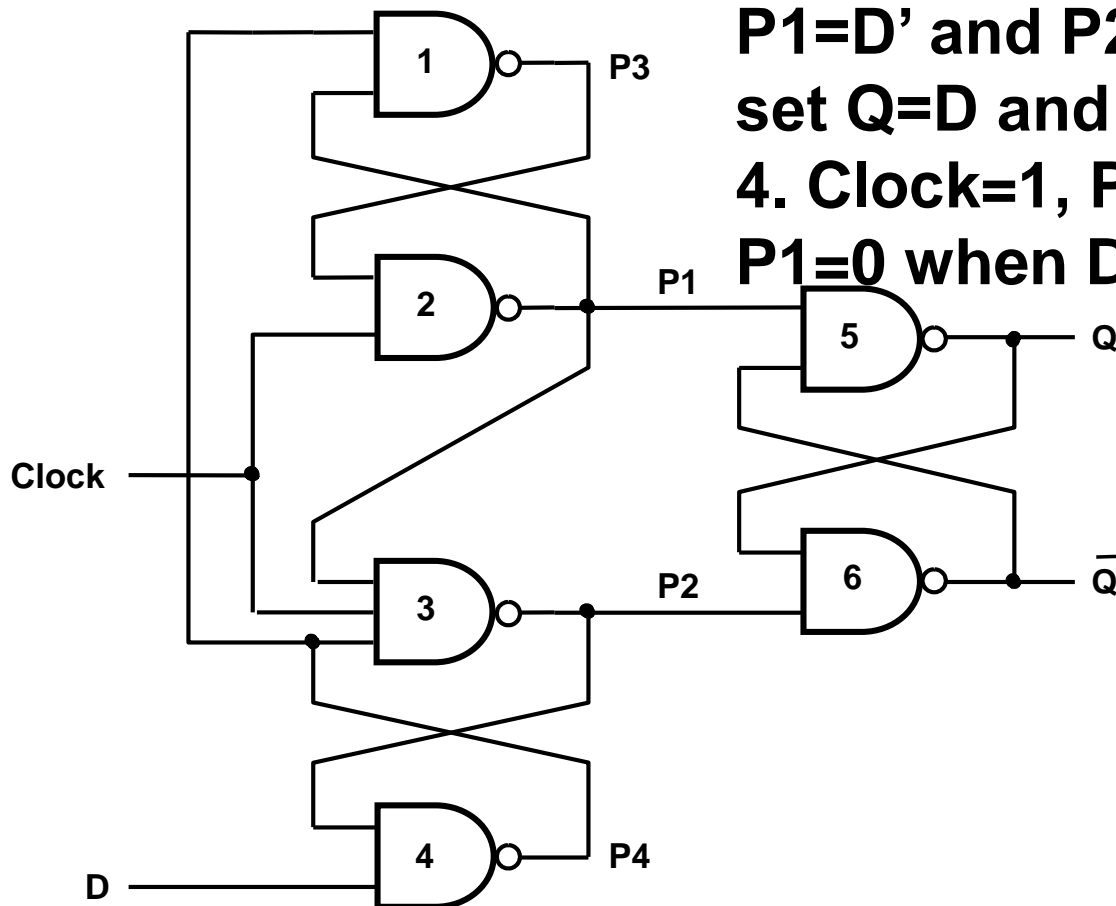
1. Clock=0, P1=P2=1; Latch Hold.
2. P4=D' and P3 = D
3. Clock 0 to 1 (positive edge), P1=D' and P2=D which set Q=D and Q'=D'
4. Clock=1, P2=0 when D=0; P1=0 when D=1





(b) Graphical symbol






# Level-Sensitive versus Edge-Triggered

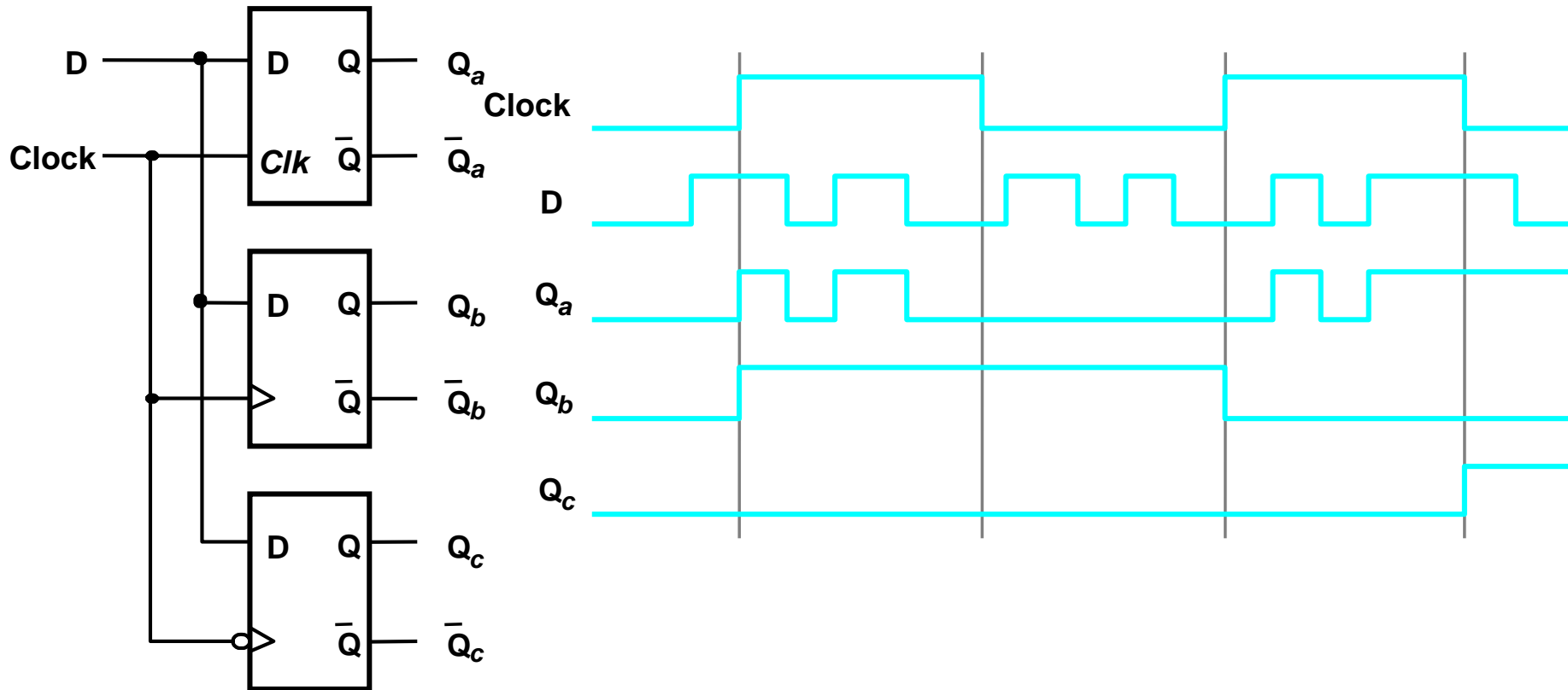
  
# Master-Slave D Flip-flop with Clear and Preset




  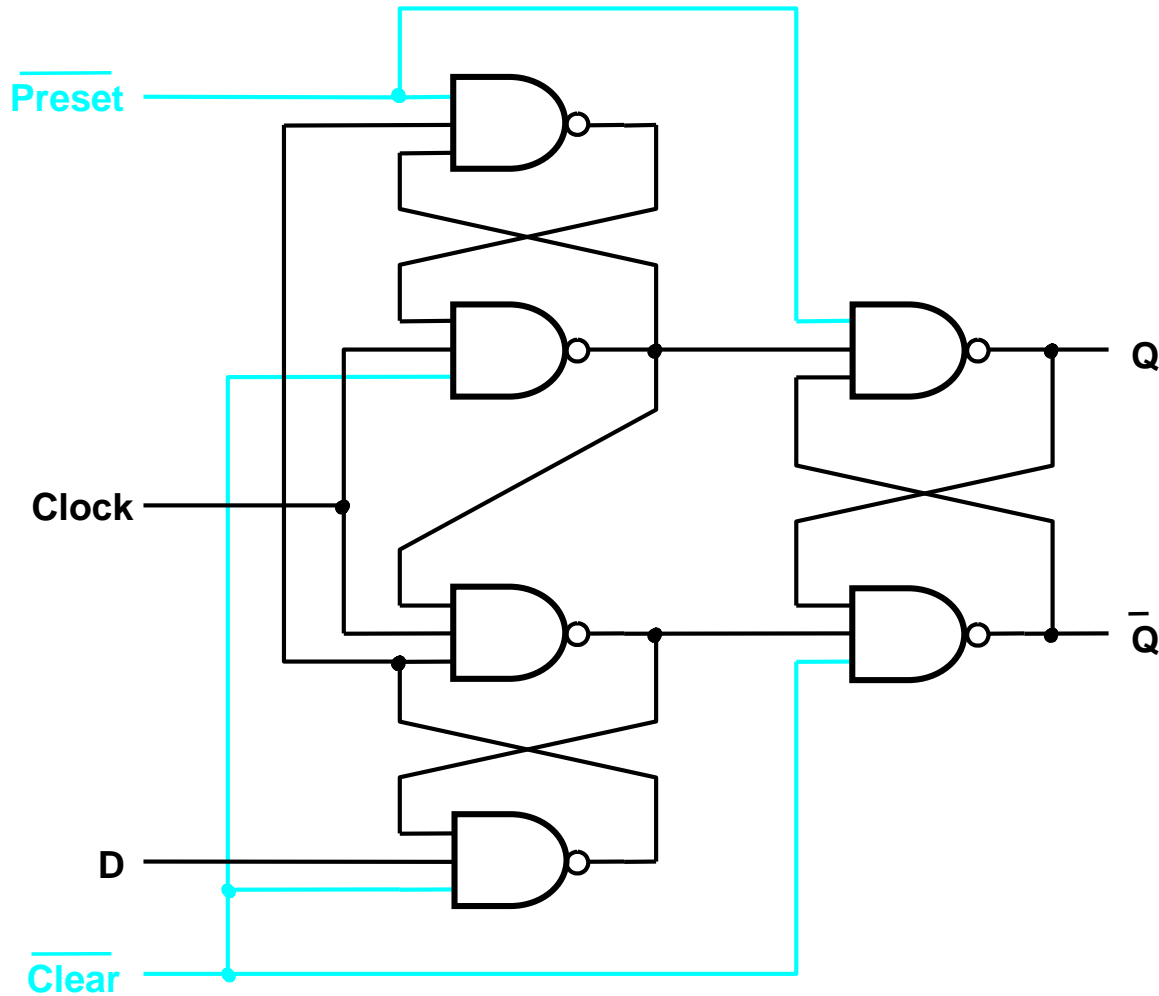
# Positive-edge-trigger D Flip-flop with Clear and Preset




Adding a synchronous clear



# Flip-Flop Timing Parameter

  

# T Flip-Flop

 


T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

  


# Configurable Flip-Flops

- In general purpose chips like PLDs, the flip-flops that are provided are sometimes *configurable*, which means that a flip-flop circuit can be configured to be either D, T, or some type.
- HOW?

# JK Flip-Flop

 

J	K	Q (t+1)
0	0	Q (t)
0	1	0
1	0	1
1	1	$\bar{Q} (t)$

 

# Summary of Terminology

- **Basic latch** is a feedback connection of two NOR gates or two NAND gates, which can store one bit of information. It can be set to 1 using S or 0 using R.
- **Gated latch** is a basic latch that includes input gating and a control input signal.
  - **Gated SR latch** uses the S and R inputs to set the latch to 1 or reset to 0 (do have  $R=S=0$  exception).
  - **Gated D latch** uses the D input to force the latch into a state that has the same logic value as the D input




- A **flip-flop** is a storage element based on the gated latch principle, which can have its output state changed only on the edge of the controlling clock signals.
  - **Edge-triggered flip-flop** is affected only by the input values present when the active edge of the clock occurs.
  - **Master-slave flip-flop** is built with two gated latches. The master stage is active during half of the clock cycle, and the slave stage is active during the other half. The output value of the flip-flop changes on the edge of the clock that activates the transfer into the slave stage. It can be edge-triggered or level sensitive. (Gated D latch=>edge-triggered; Gated SR latch=> level-sensitive)

# Registers

- A flip-flop stores one bit of information.
- When a **set** of  $n$  flip-flops is used to store  $n$  bits of information, such as an  $n$ -bit number, we refer to these flip-flops as a *register*.
- A common clock is used for each flip-flop in a register.

# Shift Register

 


	In	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub> = Out
$t_0$	1	0	0	0	0
$t_1$	0	1	0	0	0
$t_2$	1	0	1	0	0
$t_3$	1	1	0	1	0
$t_4$	1	1	1	0	1
$t_5$	0	1	1	1	0
$t_6$	0	0	1	1	1
$t_7$	0	0	0	1	1


# Parallel versus Serial

- Transmitting  $n$  bits at once using  $n$  separate wires. We say this scheme is **parallel transfer**.
- Transmitting  $n$  bits at once using a single wire, by performing the transfer one bit at a time, in  $n$  consecutive clock cycles. We say this scheme is **serial transfer**.


# Parallel-Access Shift Register

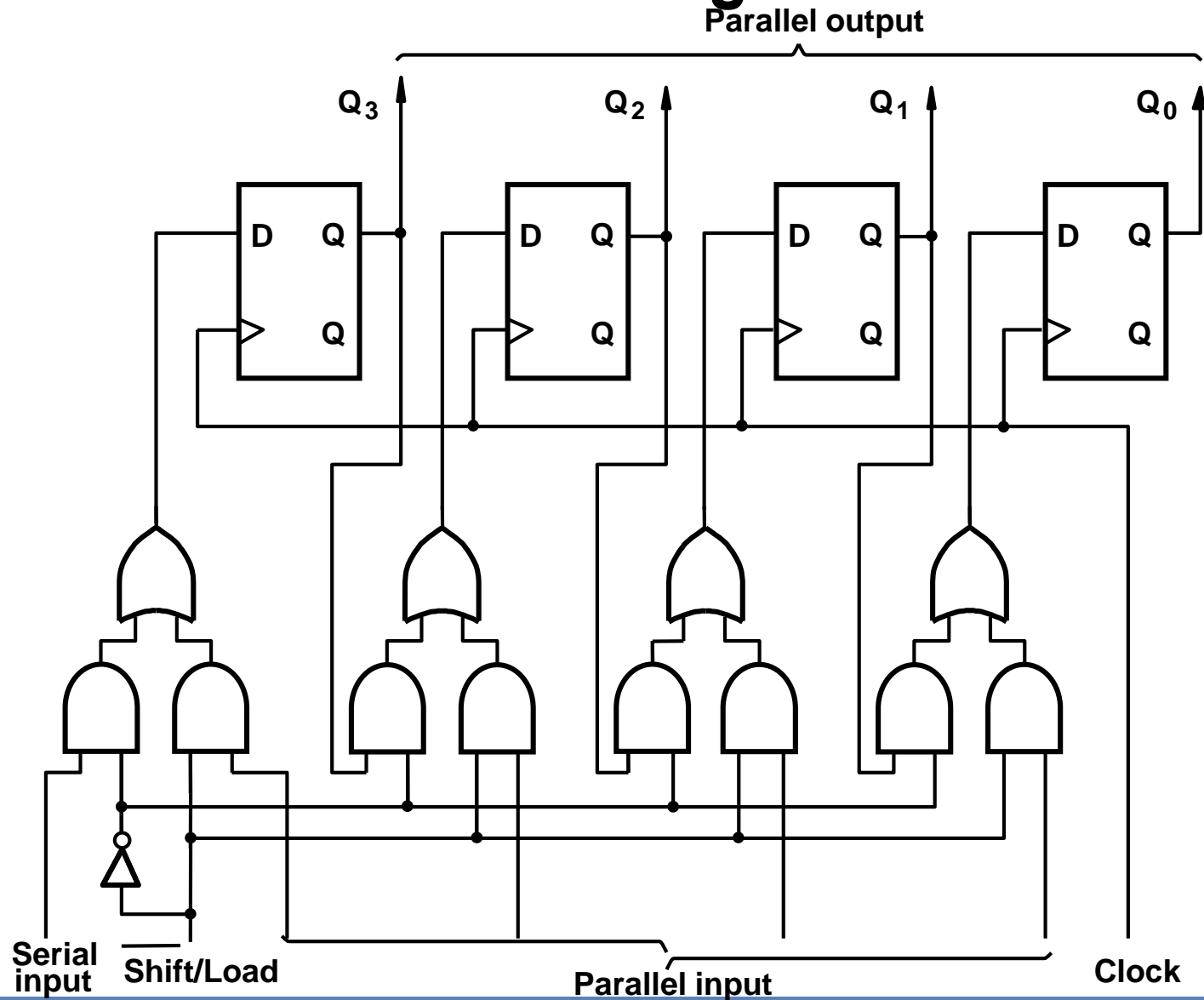
 
# Asynchronous Up-Counter with T Flip-flops


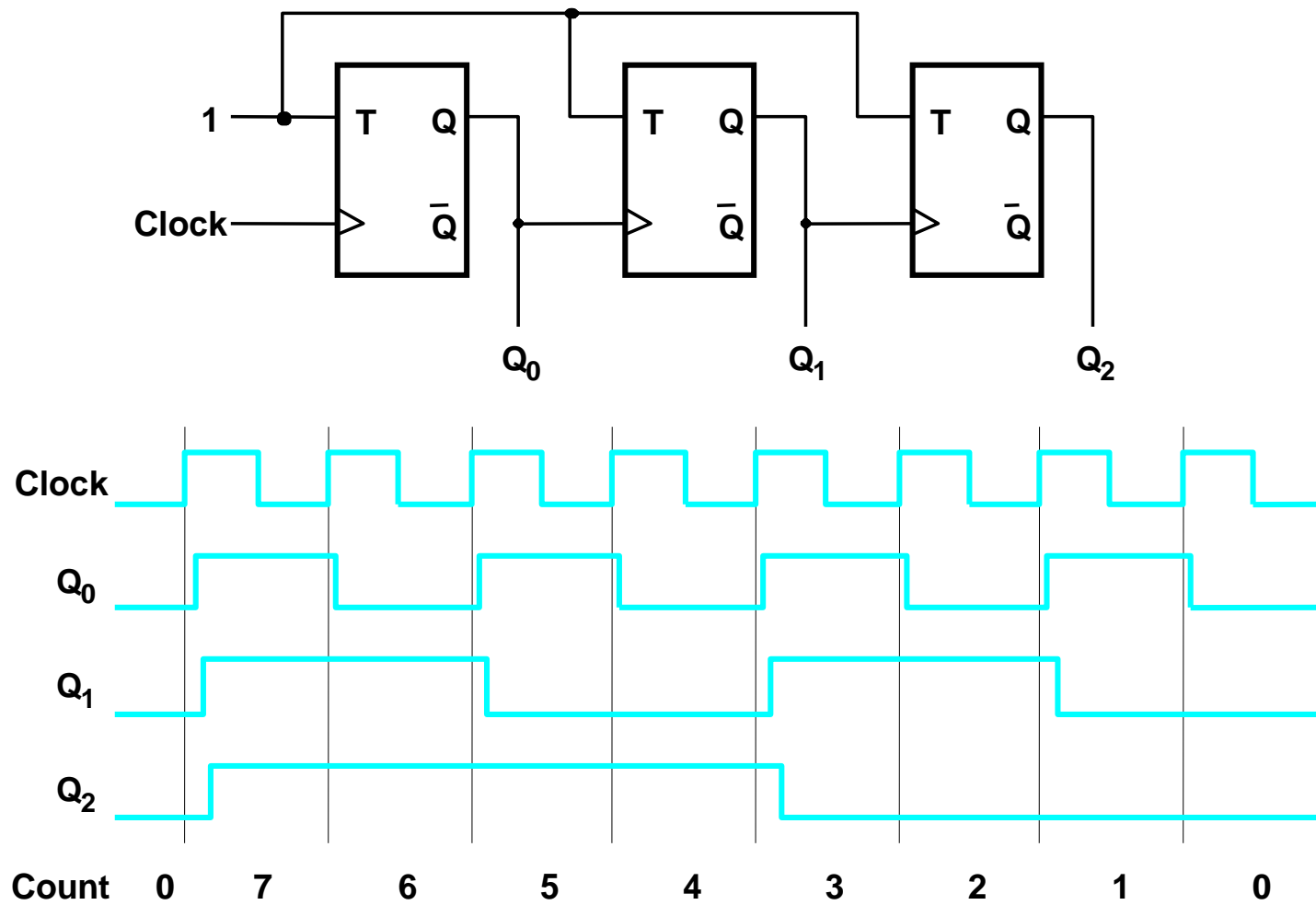
# Asynchronous Down-Counter with T Flip-flops



# Synchronous Counter with T Flip-flops



- $T_0 = 1$
- $T_1 = Q_0$
- $T_2 = Q_0 Q_1$
- $T_3 = Q_0 Q_1 Q_2$
- $T_n = Q_0 Q_1 \dots Q_{n-1}$

Clock cycle	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0


Q<sub>1</sub> changes  
Q<sub>2</sub> changes



# Synchronous Counter with T Flip-flops

  

# Enable and Clear

 


# Synchronous Counter with D Flip-flops

- $D_0 = \overline{Q_0} = 1 \oplus Q_0 (= Q_0 \oplus Enable)$
- $D_1 = Q_1 \oplus Q_0 (\cdot Enable)$
- $D_2 = Q_2 \oplus Q_1 Q_0 (\cdot Enable)$
- $D_3 = Q_3 \oplus Q_2 Q_1 Q_0 (\cdot Enable)$
- $D_i = Q_i \oplus Q_{i-1} Q_{i-2} \dots Q_1 Q_0 (\cdot Enable)$


- $$D = Q\bar{T} + \bar{Q}T$$

$$= Q \oplus T$$

# Synchronous Counter with D Flip-flops

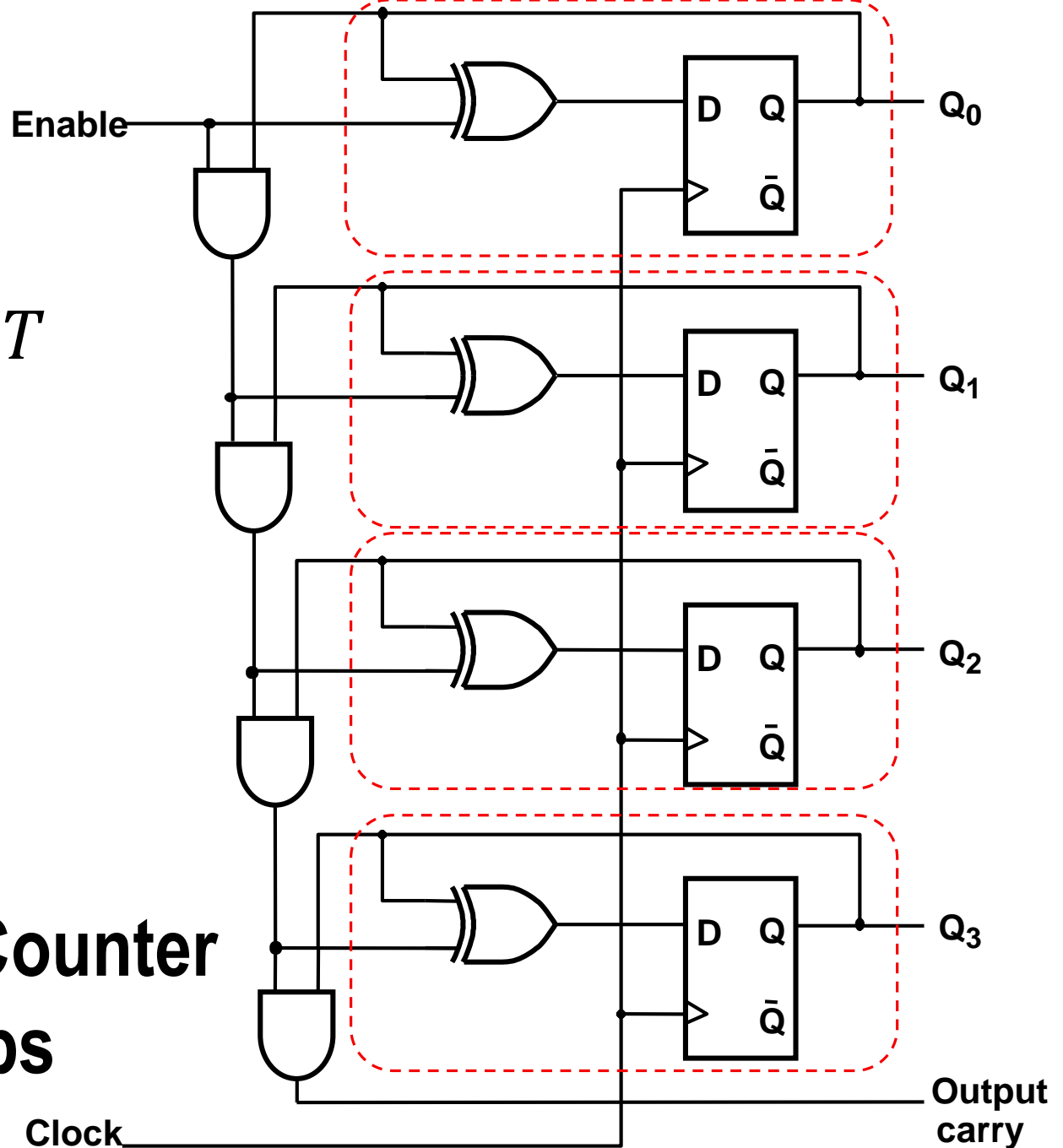


# Counter with Parallel-load

 

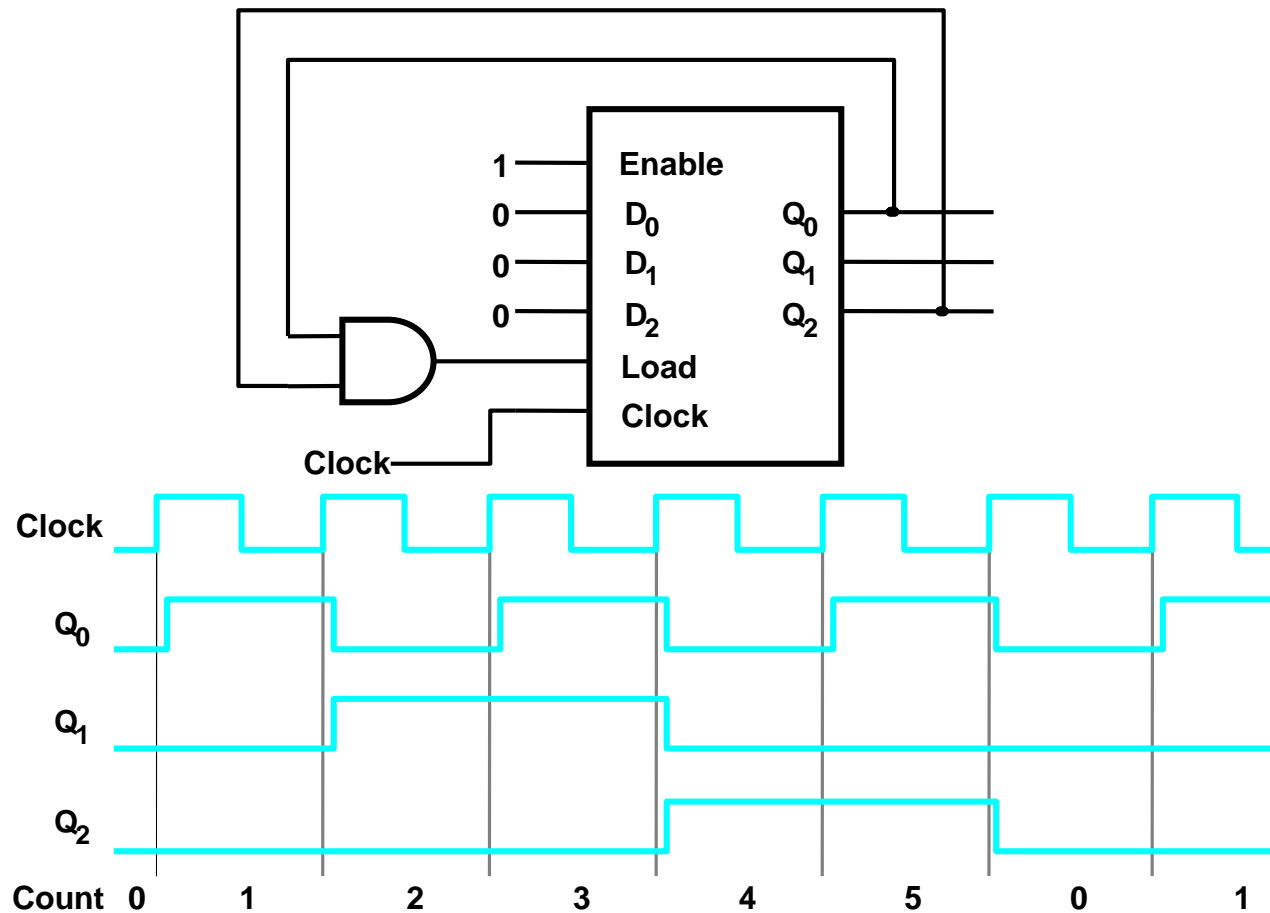
# A Modulo-6 Counter with Synchronous Reset

- Counting sequence: 0,1,2,3,4,5,0,1, and so on.




# A Modulo-6 Counter with Asynchronous Reset

- Modulo 5 or 6?

 


# BCD Counter

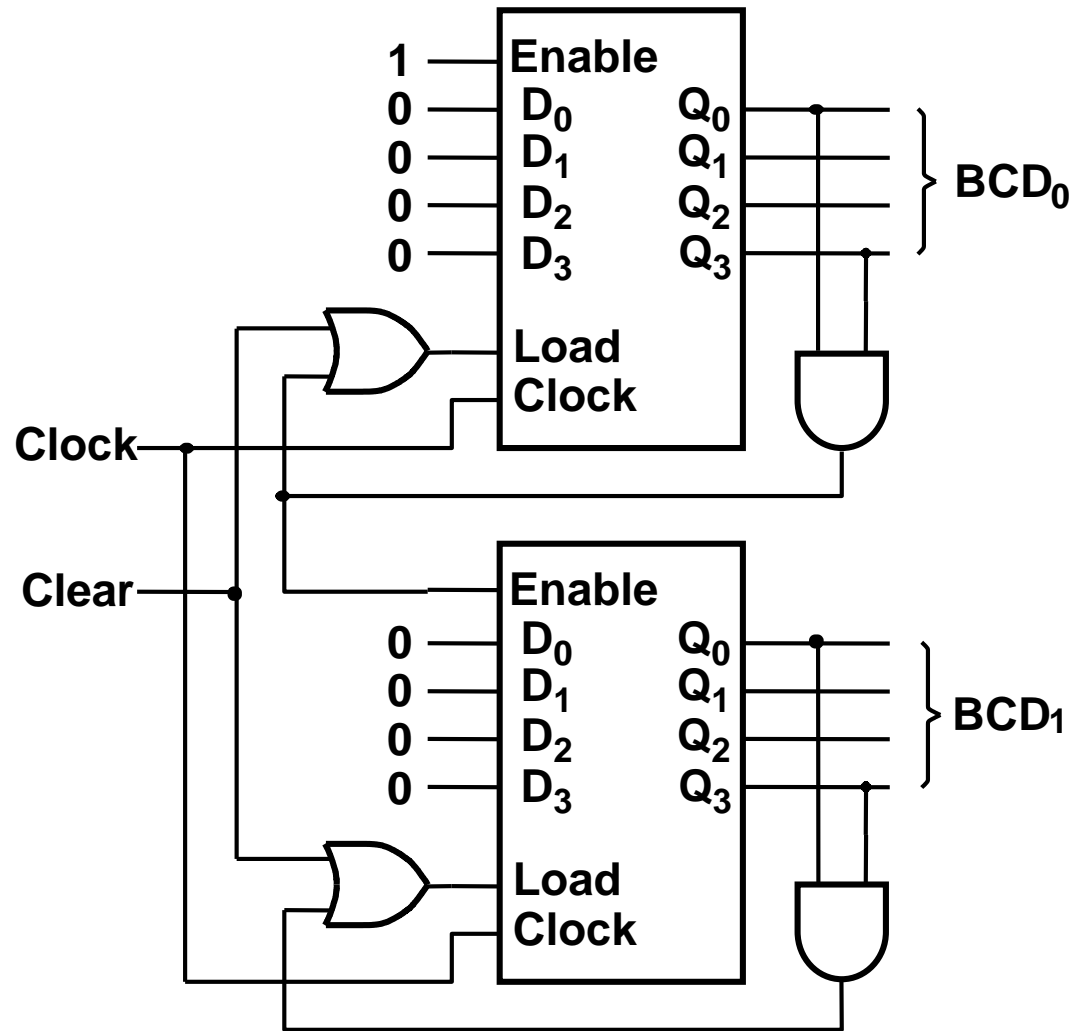





# Ring Counter

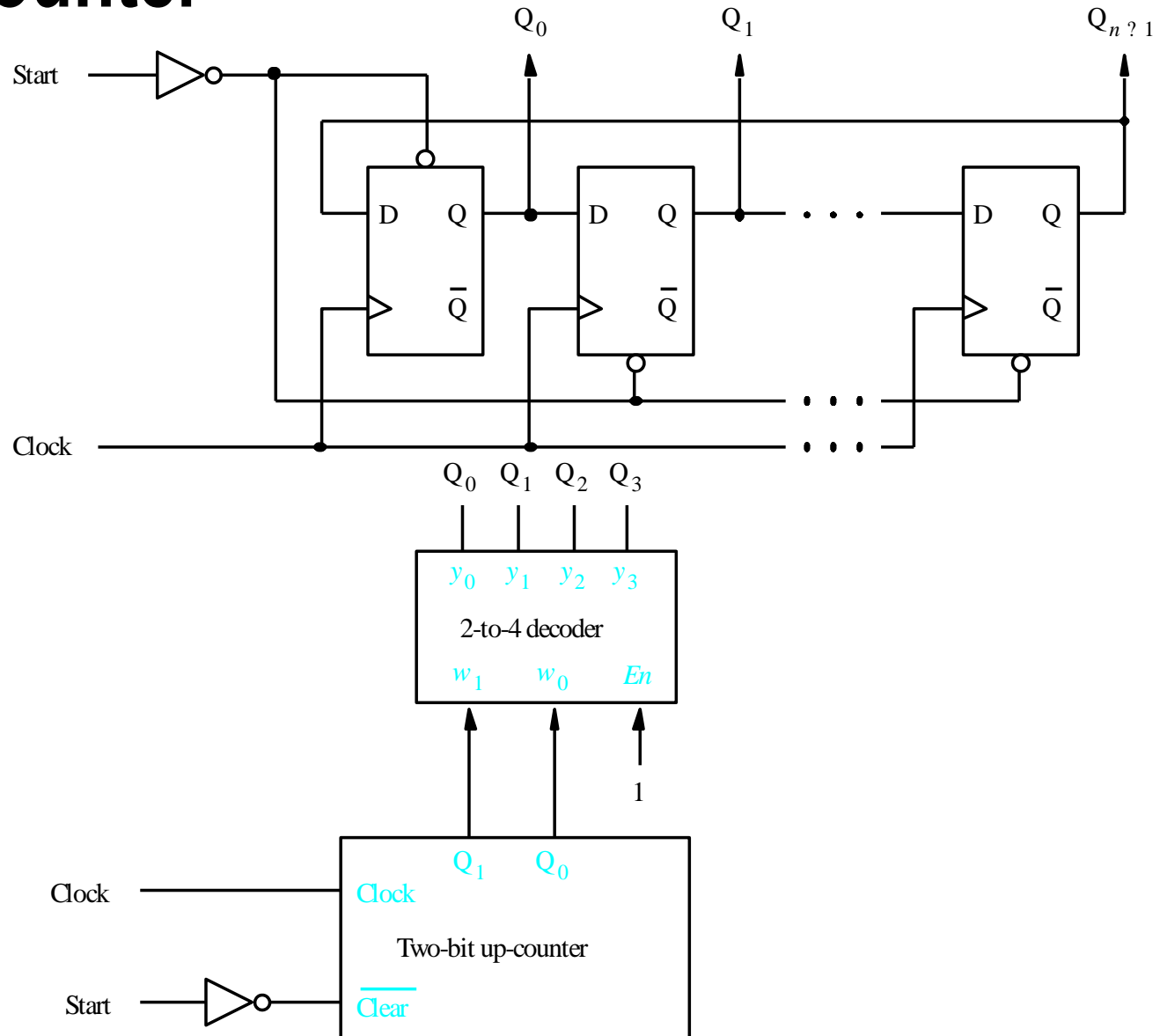


# Johnson Counter

 

# Design Example: Bus Structure

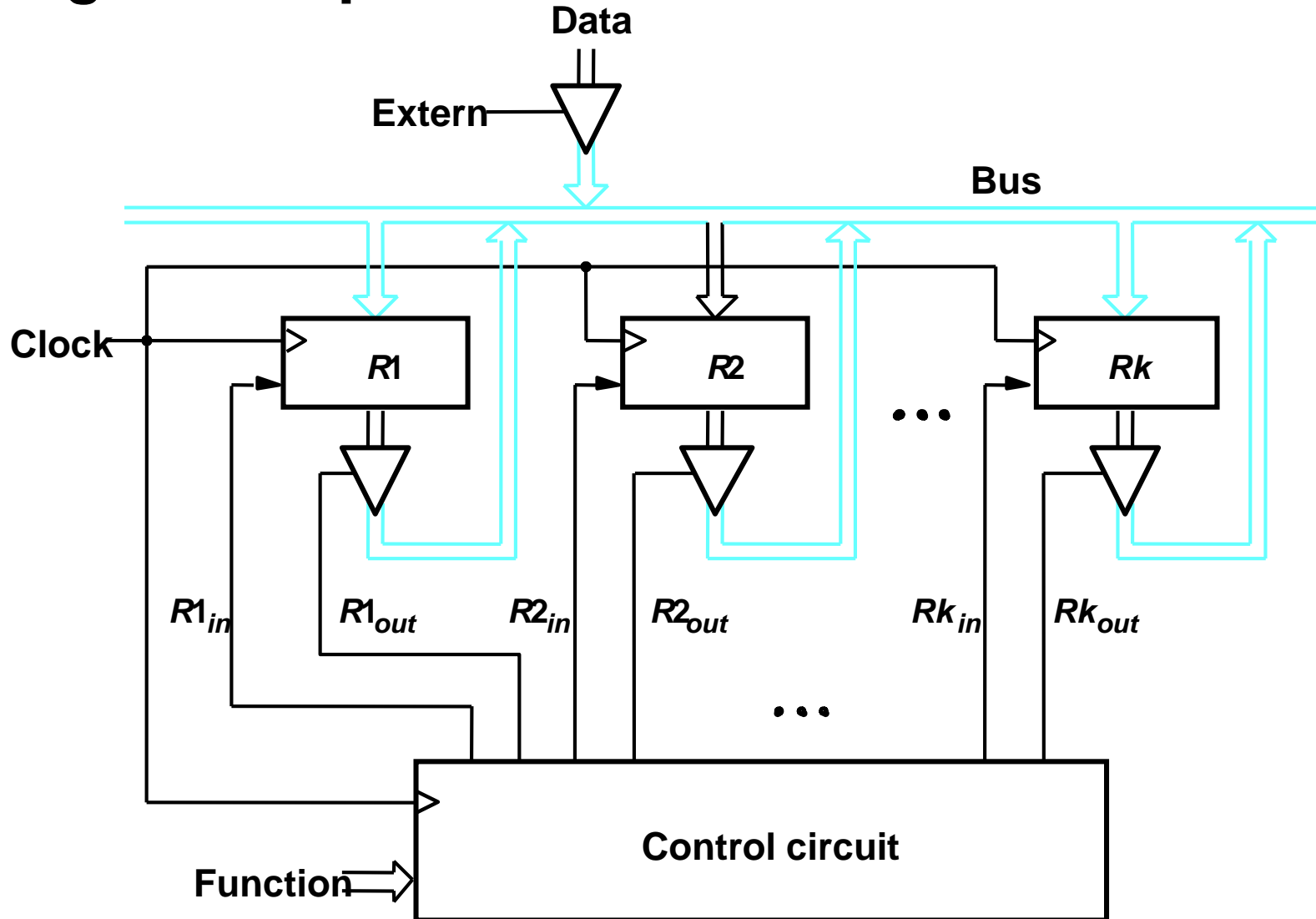


# Simple Processor

 

# Operation Performed in the Processor


Operation	Function performed
Load $Rx, Data$	$Rx \leftarrow Data$
Move $Rx, Ry$	$Rx \leftarrow [Ry]$
Add $Rx, Ry$	$Rx \leftarrow [Rx] + [Ry]$
Sub $Rx, Ry$	$Rx \leftarrow [Rx] - [Ry]$

# Control Circuit

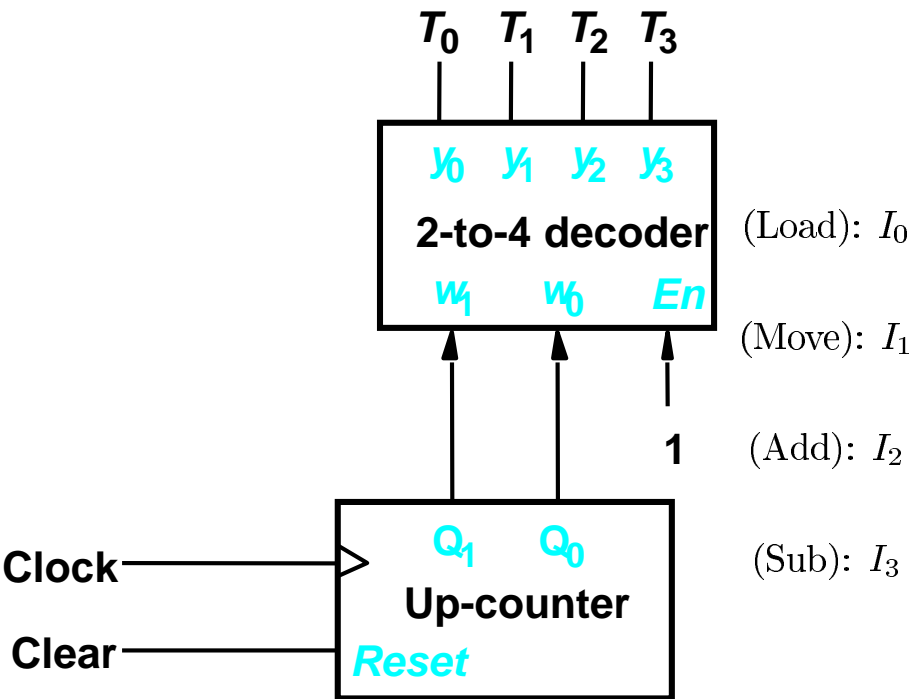


	$T_1$	$T_2$	$T_3$
(Load): $I_0$	$Extern, R_{in} = X,$ $Done$		
(Move): $I_1$	$R_{in} = X, R_{out} = Y,$ $Done$		
(Add): $I_2$	$R_{out} = X, A_{in}$	$R_{out} = Y, G_{in},$ $AddSub = 0$	$G_{out}, R_{in} = X,$ $Done$
(Sub): $I_3$	$R_{out} = X, A_{in}$	$R_{out} = Y, G_{in},$ $AddSub = 1$	$G_{out}, R_{in} = X,$ $Done$

# Control Circuit

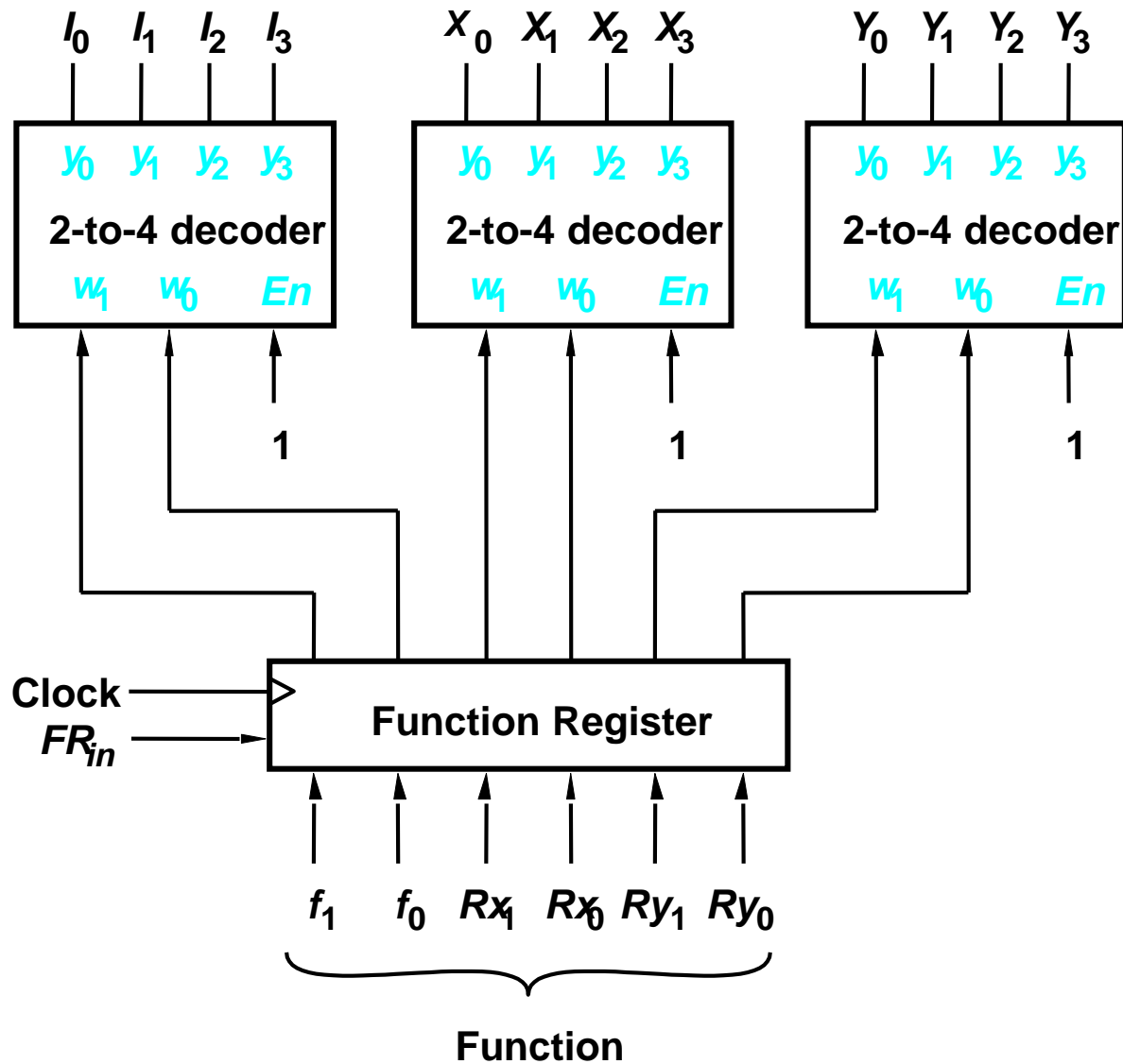


# Reaction Timer

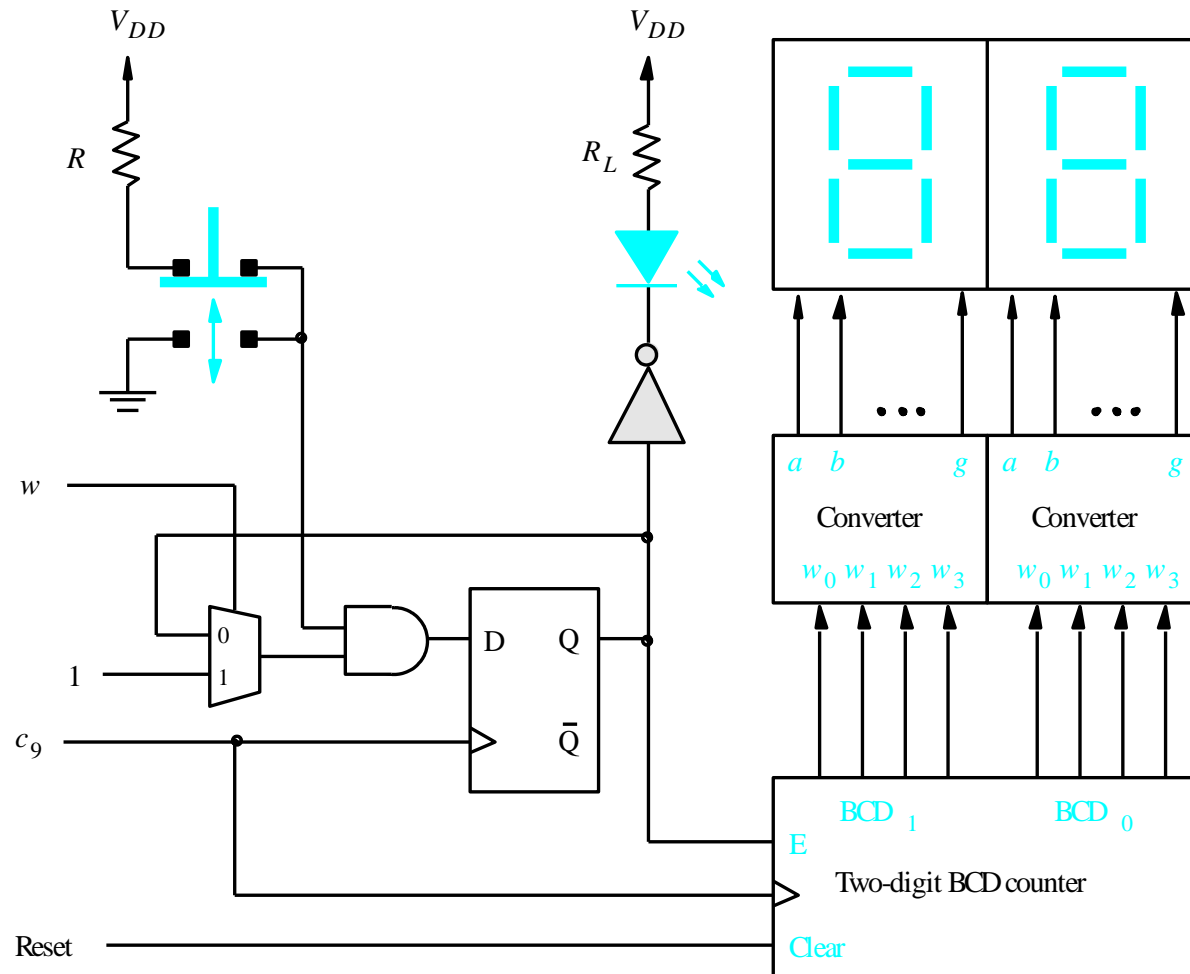


 
# Timing Analysis


- $T_{min} = t_{cQ} + t_{NOT} + t_{su}$
- $F_{max} = \frac{1}{T_{min}}$
- A simple flip-flop circuit
  - $T_{min} = 1.0 + 1.1 + 0.6 = 2.7ns$
  - $F_{max} = \frac{1}{2.7ns} = 370.37MHz$


 
# Timing Analysis for a 4-bit Counter

$$\begin{aligned} \bullet T_{min} &= t_{cQ} + 3(t_{AND}) \\ &\quad + t_{XOR} + t_{su} \\ &= 1.0 + 3(1.2) + 1.2 + 0.6 \\ &= 6.4ns \end{aligned}$$

$$\bullet F_{max} = \frac{1}{6.4ns} = 156.25 \text{ MHz}$$




# Clocked Synchronous State-Machine Analysis

- “Clocked” refers to the fact that their storage elements (flip-flops) employ a clock input.
- “Synchronous” means that all of the flip-flops use the same clock signal.
- “State-machine” or “finite state-machine” is a generic name given to sequential circuits with flip-flops.
- Such a state machine changes state only when a triggering edge or “tick” occurs on the clock signal.

 
# Mealy State-Machine

- The output depends on both state and input.
  - Next state =  $F$  (current state, input)
  - Output =  $G$  (current state, input)


 
# Moore State Machine

- Output only depends on the state alone.
  - Output =  $G$  (current state)
- Output-coded state machine: use state variables as output, no output logic  $G \Rightarrow$  no change during each




# Basic Design Steps

- 1. The circuit has one input,  $w$ , and one output  $Z$
- 2. All changes in the circuit occur on the positive edge of a clock signal
- 3. The output  $z$  is equal to 1 if during two immediately preceding clock cycles the input  $w$  was equal to 1. Otherwise the value of  $z$  is equal to 0.


# State Diagram and State Table

<b>Clockcycle:</b>	<b>t<sub>0</sub></b>	<b>t<sub>1</sub></b>	<b>t<sub>2</sub></b>	<b>t<sub>3</sub></b>	<b>t<sub>4</sub></b>	<b>t<sub>5</sub></b>	<b>t<sub>6</sub></b>	<b>t<sub>7</sub></b>	<b>t<sub>8</sub></b>	<b>t<sub>9</sub></b>	<b>t<sub>10</sub></b>
<b>w:</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>z:</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>

 

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

# State Assignment

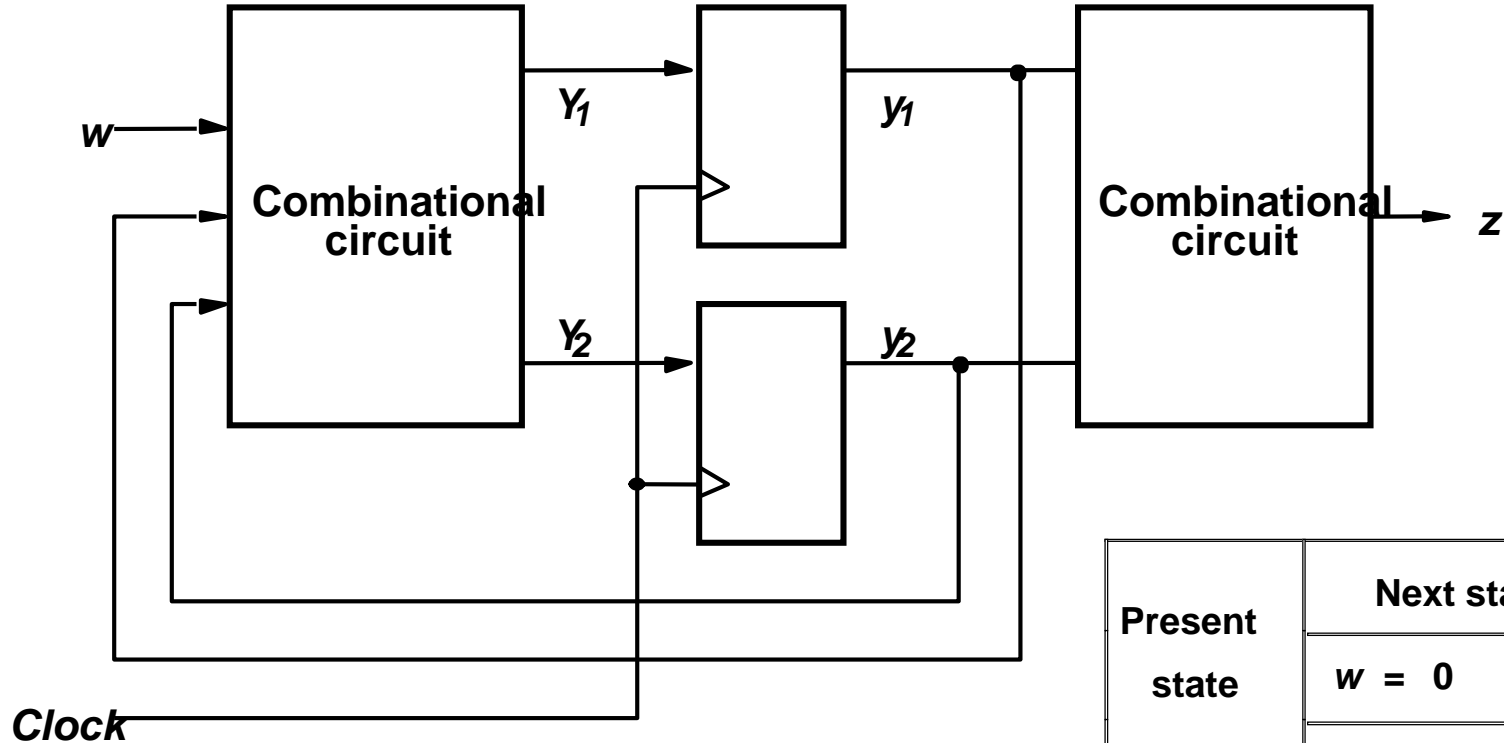

	Present state $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$



# Choice of Flip-flops and Derivation of Next-state and Output Expressions

- Simplest choice: D flip-flops
- Derive logic eq. from state table

		$y_2y_1$			
		00	01	11	10
$w$	0	0	0	d	0
	1	1	0	d	0

		$y_2y_1$			
		00	01	11	10
$w$	0	0	0	d	0
	1	0	1	d	1

$y_2$	$y_1$	
	0	1
0	0	0
1	1	d

Ignoring don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

$$Y_2 = wy_1\bar{y}_2 + w\bar{y}_1y_2$$

$$z = \bar{y}_1y_2$$


Using don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$


$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$

$$z = y_2$$

# Final Implementation

 

# Timing Diagram

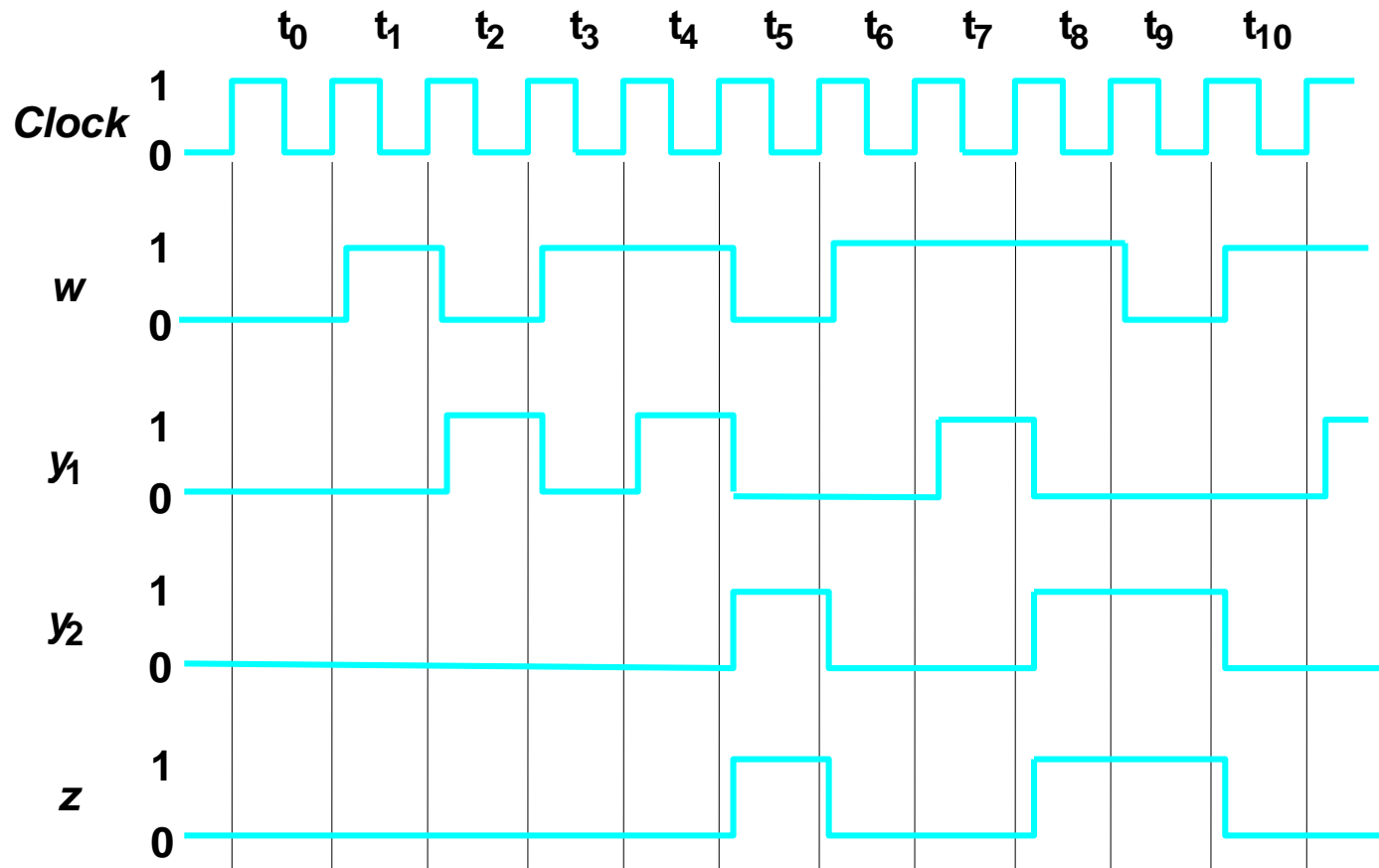


# Summary of Design Steps

- 1. Obtain the specification of the desired circuit
- 2. Derive the states for the machine by first selecting a starting state. Then, given the specification of the circuit, create new states as needed for the machine to respond to all inputs. Create a state diagram accordingly (optional).
- 3. Create a state table.
- 4. State minimization
- 5. Decide the state variables needed and do state assignment

- 6. Choose the type of flip-flops to be used in the circuit. Derive the next-state logic expressions to control the inputs to all flip-flops and then derive logic expressions for the output of the circuit.
- 7. Implement the circuit as indicated by the logic expressions.
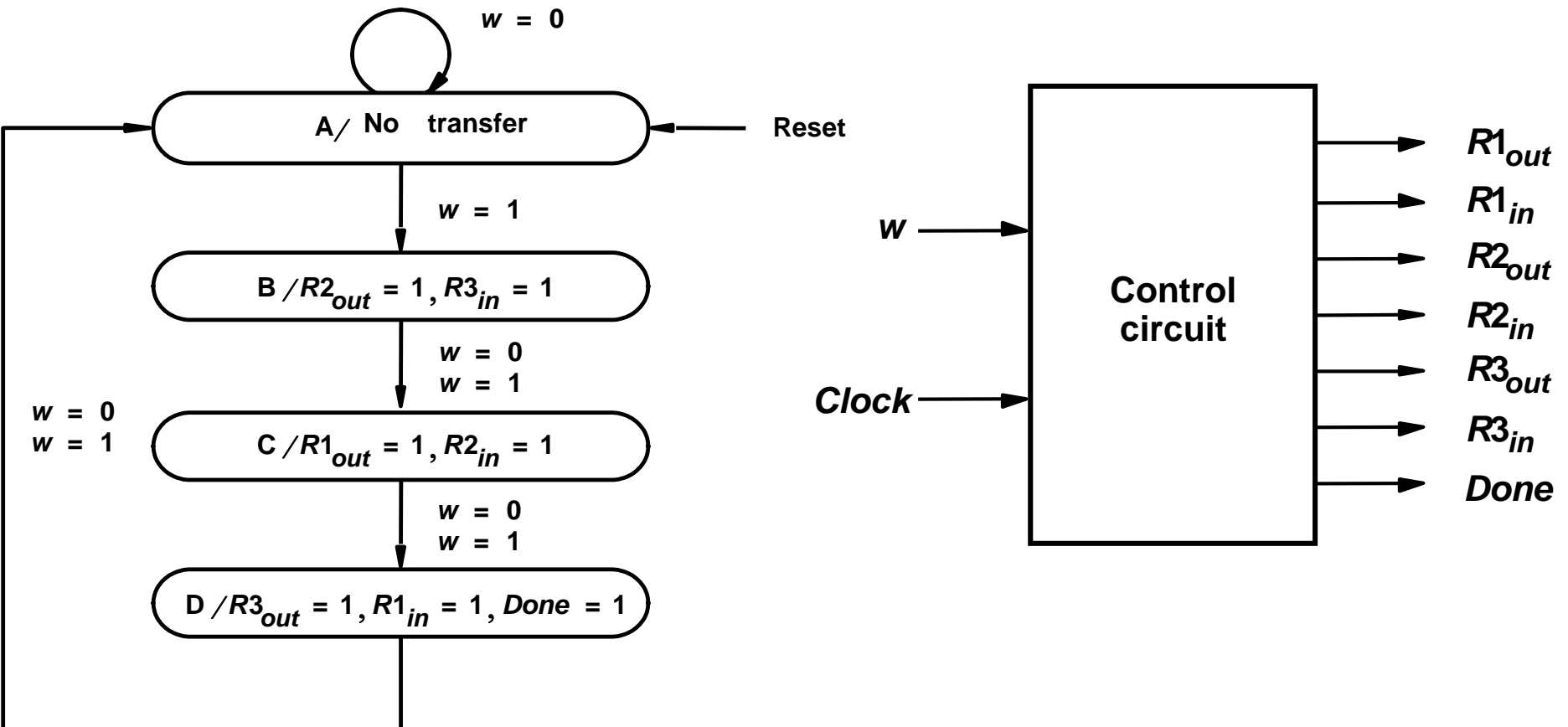
# Ex 8.1 Bus control

- Swap R1 and R2 using R3 as a temporary storage locations




# Ex 8.1 State table and state assignments


Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1
 
# Ex 8.1 Logic expression of Next-state and output Logic



$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$

 

$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$

- Output control signals are


- $R1_{out} = R2_{in} = \bar{y}_1y_2$

- $R1_{in} = R3_{out} = Done = y_1y_2$

- $R2_{out} = R3_{in} = y_1\bar{y}_2$




## Ex 8.1 Final Implementation

 

# Improved State Assignment

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Present state $y_2y_1$	Next state		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
A 00	00	01	0
B 01	00	11	0
C 11	00	11	1
	$dd$	$dd$	$d$

 

- $Y_1 = D_1 = w$
- $Y_2 = D_2 = wy_1$
- $z = y_2$

# Improved State Assignment

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	0 0	01	0	0	0	0	0	0	0
B	01	1 1	11	0	0	1	0	0	1	0
C	11	1 0	10	1	0	0	1	0	0	0
D	10	0 0	00	0	1	0	0	1	0	1

$y_2 y_1$		00	01	11	10
$w$	0		1		
	1	1	1		

$$Y_1 = w\bar{y}_2 + y_1\bar{y}_2$$

$y_2 y_1$		00	01	11	10
$w$	0		1	1	
	1		1	1	

$$Y_2 = y_1$$

- $R1_{out} = R2_{in} = y_1 y_2$
- $R1_{in} = R3_{out} =$   
 $Done = \bar{y}_1 y_2$
- $R2_{out} = R3_{in} = y_1 \bar{y}_2$

# One-Hot Encoding

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1


	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

- $Y_1 = \bar{w}y_1 + y_4$
- $Y_2 = wy_1$
- $Y_3 = y_2$
- $Y_4 = y_3$
- $R1_{out} = R2_{in} = y_3$
- $R1_{in} = R3_{out} = Done = \bar{y}_1y_2$
- $R2_{out} = R3_{in} = y_1\bar{y}_2$

# Mealy State Model

- Specification:  $z=1$  for two '1's and switch in the same cycle.

<b>Clock cycle:</b>	<b>t<sub>0</sub></b>	<b>t<sub>1</sub></b>	<b>t<sub>2</sub></b>	<b>t<sub>3</sub></b>	<b>t<sub>4</sub></b>	<b>t<sub>5</sub></b>	<b>t<sub>6</sub></b>	<b>t<sub>7</sub></b>	<b>t<sub>8</sub></b>	<b>t<sub>9</sub></b>	<b>t<sub>10</sub></b>
<b>w:</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>z:</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>

 

# State Table and State Assignment

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	A	B	0	0
B	A	B	0	1



- $Y=D=w$

- $z=wy$

	Present state	Next state		Output	
		w = 0	w = 1	w = 0	w = 1
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1




# Circuit and Timing Diagram

  


# Ex. 8.4


## • Moore type

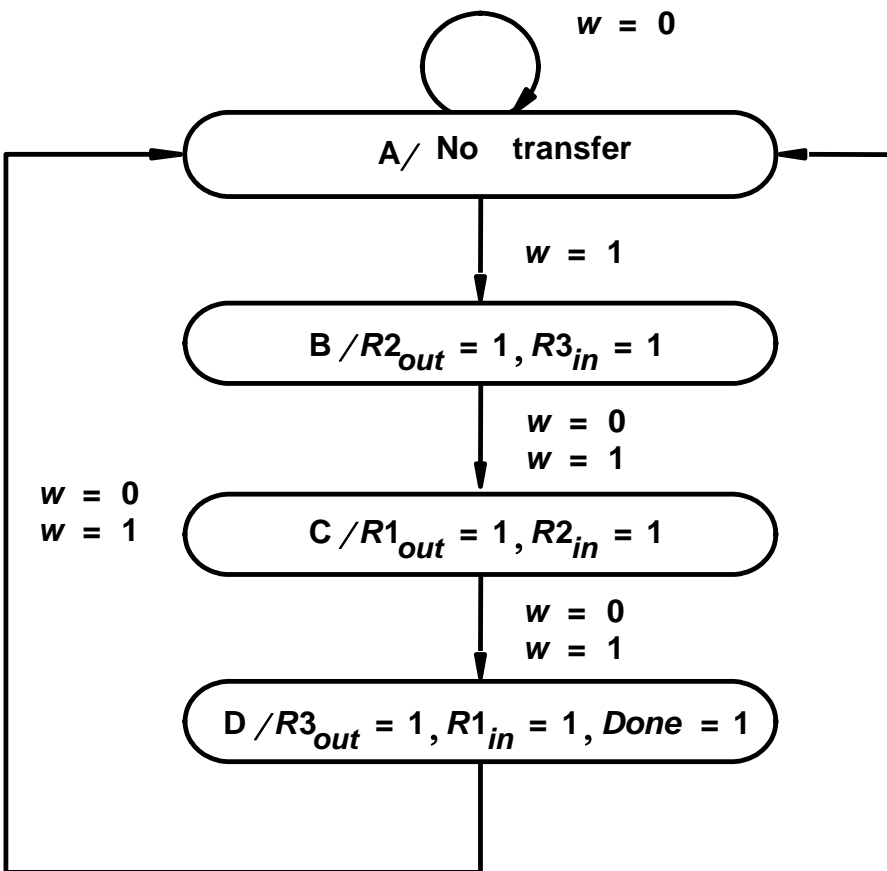

## Mealy type

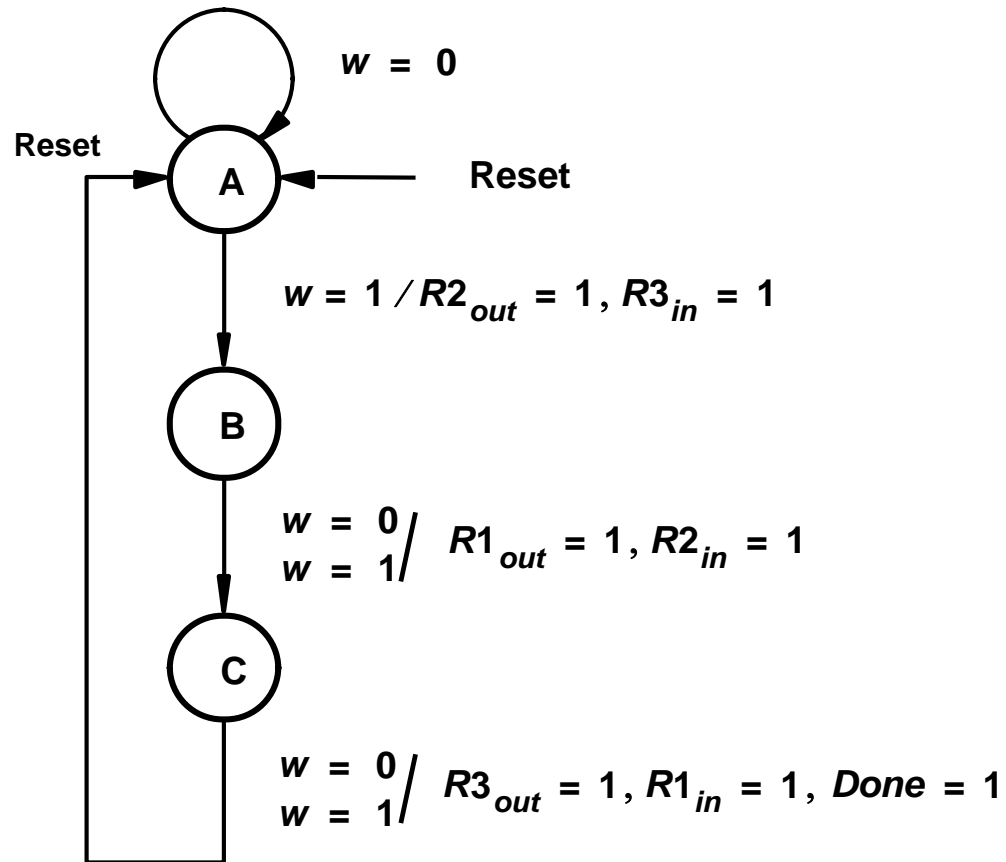

# Mealy-Type FSM for Serial Adder

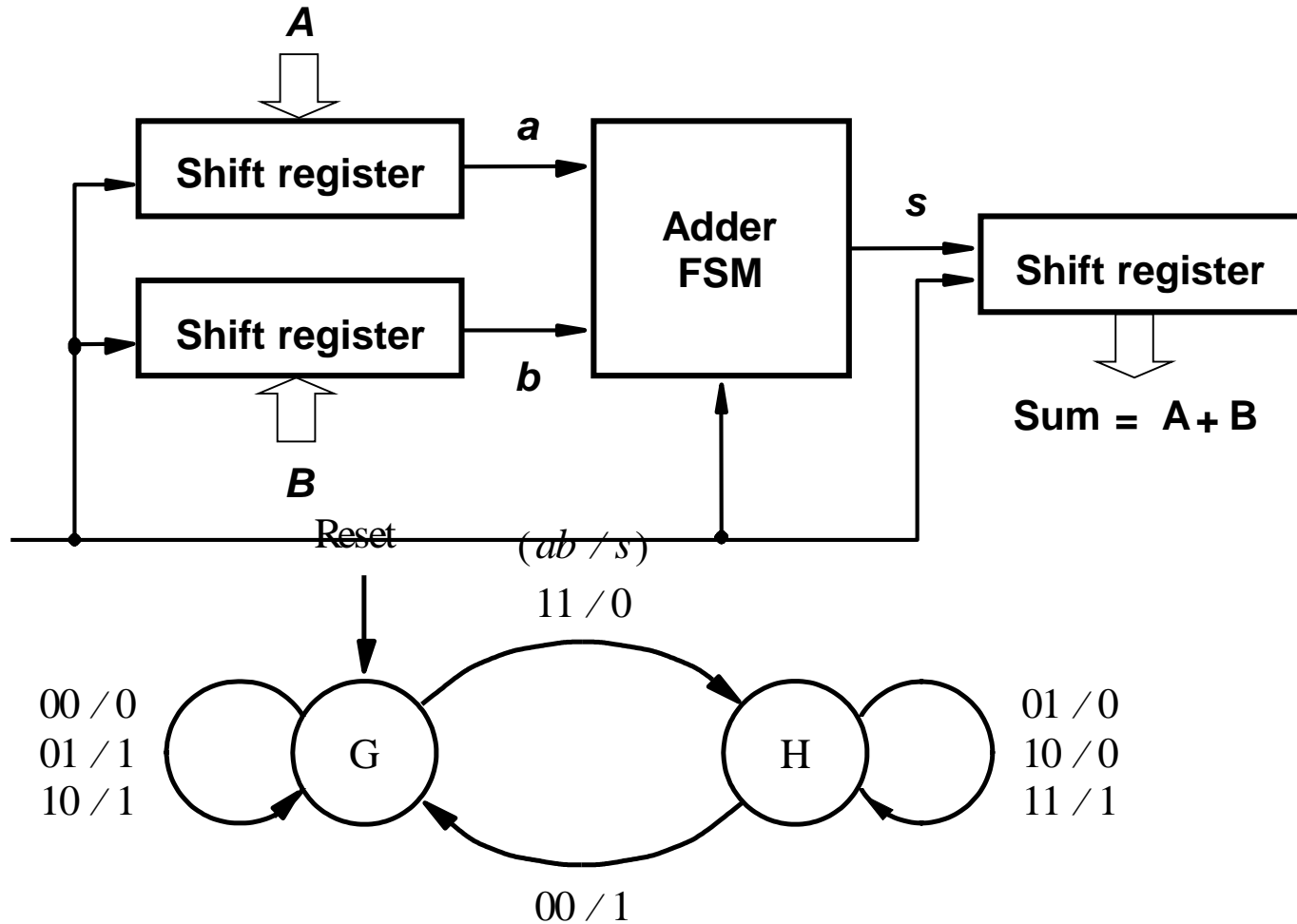

G: carry-in = 0


H: carry-in = 1

Present state	Next state				Outputs			
	<i>ab</i> =00	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1


Present state <i>y</i>	Next state				Output			
	<i>ab</i> =00	01	10	11	00	01	10	11
	<i>Y</i>				<i>s</i>			
0	0	0	0	1	0	1	1	0
1	0	1	1	1	1	0	0	1

- $Y = ab + ay + by$
- $s = a \oplus b \oplus y$

# Mealy-type Serial Adder Circuit

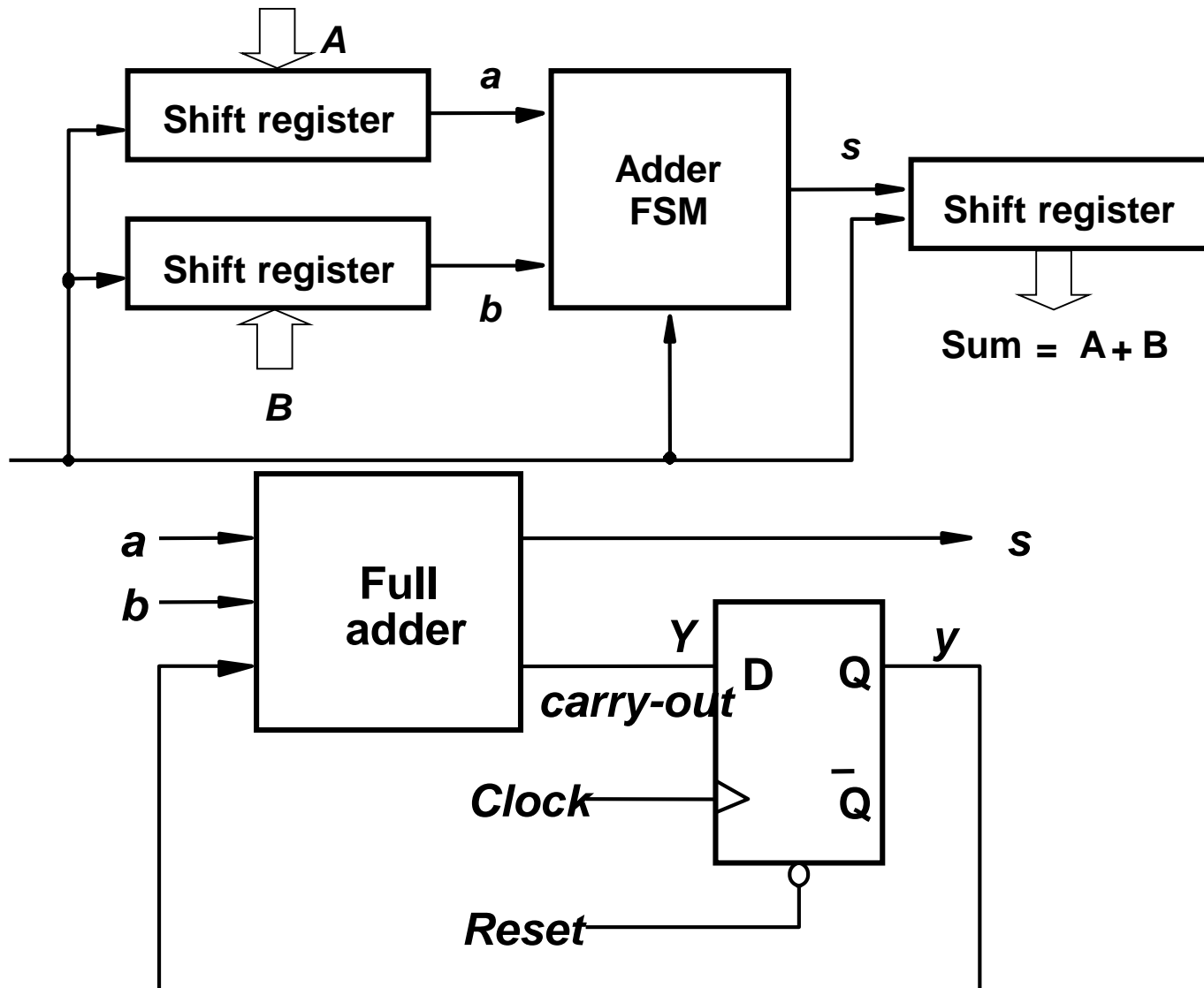

# Moore-type FSM for Serial Adder

 


Present state	Nextstate				Output <i>s</i>
	<i>ab</i> =00	01	10	11	
<b>G<sub>0</sub></b>	<b>G<sub>0</sub></b>	<b>G<sub>1</sub></b>	<b>G<sub>1</sub></b>	<b>H<sub>0</sub></b>	<b>0</b>
<b>G<sub>1</sub></b>	<b>G<sub>0</sub></b>	<b>G<sub>1</sub></b>	<b>G<sub>1</sub></b>	<b>H<sub>0</sub></b>	<b>1</b>
<b>H<sub>0</sub></b>	<b>G<sub>1</sub></b>	<b>H<sub>0</sub></b>	<b>H<sub>0</sub></b>	<b>H<sub>1</sub></b>	<b>0</b>
<b>H<sub>1</sub></b>	<b>G<sub>1</sub></b>	<b>H<sub>0</sub></b>	<b>H<sub>0</sub></b>	<b>H<sub>1</sub></b>	<b>1</b>

Present state $y_2y_1$	Nextstate				Output $s$
	$ab=00$	01	10	11	
	$Y_2Y_1$				
00	00	01	01	10	0
01	00	01	01	10	1
10	01	10	10	11	0
11	01	10	10	11	1

- $Y_1 = a \oplus b \oplus y_2$
- $Y_2 = ab + ay_2 + by_2$
- $s = y_1$

# Moore-type Serial Adder Circuit

 



# State Minimization

- Two state  $S_i$  and  $S_j$  are said to be equivalent if and only if for every possible input sequence, the same output sequence will be produced regardless of whether  $S_i$  and  $S_j$  is the initial state
- If a input combination  $k$  is applied in the state  $S_i$  and it causes the machine to move to state  $S_v$ ,  $S_v$  is defined as a *k-successor* of  $S_i$ .
- A partition consist of one or more blocks, where each block comprises a subset of states that maybe equivalent

## Ex 8.6

- Initial partition  
 $P_1 = (ABCDEFGG)$
- Next partition with diff. outputs  
 $P_2 = (ABD)(CEFG)$
- Check 0-successors and 1-successors  
 $P_3 = (ABD)(CEG)(F)$
- Again  
 $P_4 = (AD)(B)(CEG)(F)$   
 $P_5 = (AD)(B)(CEG)(F)$

Present state	Next state		Output z
	w = 0	w = 1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0


Present state	Nextstate		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

## Ex8.7 Vending Machine


- The machine accepts nickels (5cent) and dimes (10cents)
- It takes 15 cents for a piece of candy to be releases.
- If 20 cents is deposited, the machine will not return the change, but it will credit the buyer with 5 cents and wait for the buyer to make a second purchase
 
# Denounced Circuit

- Mechanical sensor outputs  $\text{sense}_N$  and  $\text{sense}_D$  are slow and may stay on for several ticks.



# State Diagram

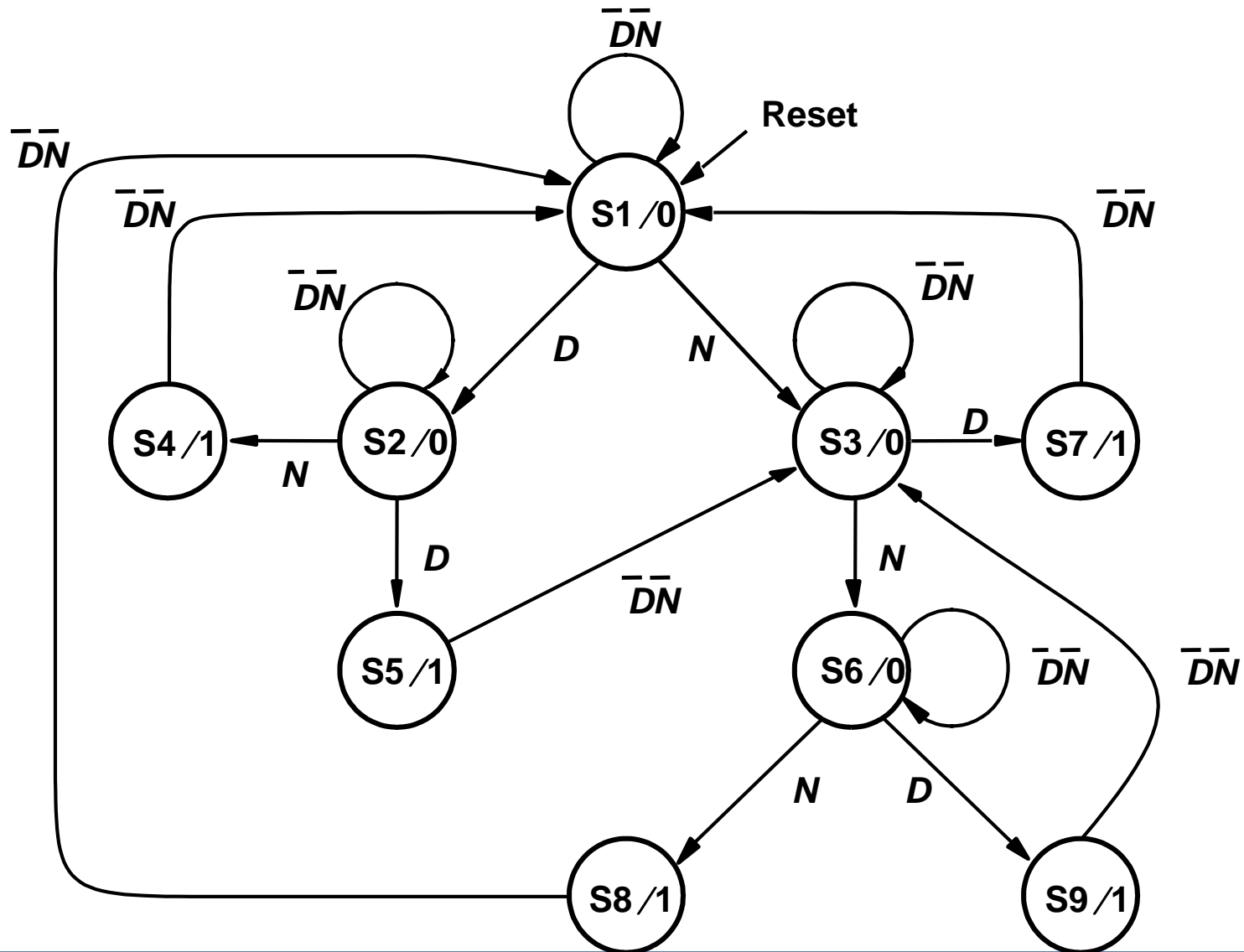

# State table and minimization

- $P_1 = (S1, S2, S3, S4, S5, S6, S7, S8, S9)$
- $P_2 = (S1, S2, S3, S6)(S4, S5, S7, S8, S9)$
- $P_3 = (S1)(S3)(S2, S6)(S4, S5, S7, S8, S9)$
- $P_4 = (S1)(S3)(S2, S6)(S4, S7, S8)(S5, S9)$
- $P_5 = (S1)(S3)(S2, S6)(S4, S7, S8)(S5, S9)$


Present state	Next state				Output $z$
	$DN = 00$	01	10	11	
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S6	S7	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1
S6	S6	S8	S9	—	0
S7	S1	—	—	—	1
S8	S1	—	—	—	1
S9	S3	—	—	—	1

# Minimized State Table


Present state	Next state				Output $z$
	$DN = 00$	01	10	11	
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S2	S4	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1

# State Diagram

- Moore

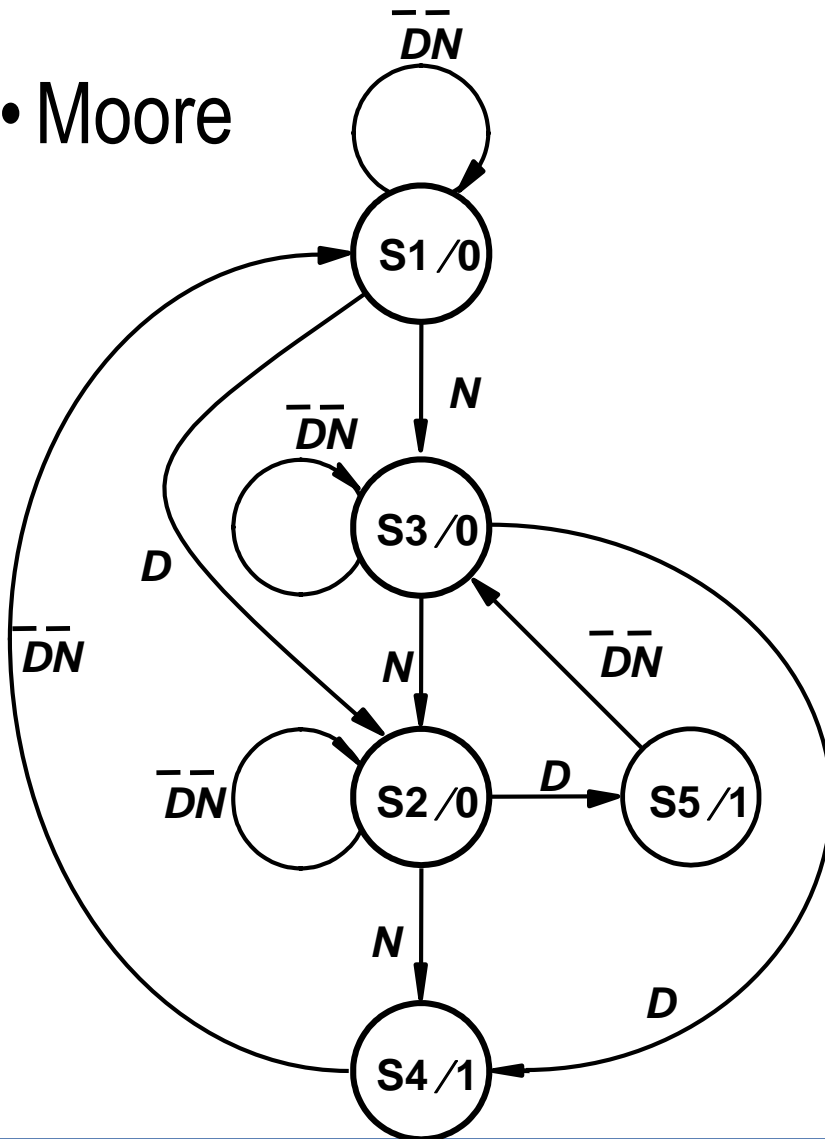

Mealy

 



# Ex. 8.8 Incompletely Specified State Table

- $P_1 = (ABCDEFGG)$

- Assume  $- = 0$

$P_2 = (ABDG)(CEF)$

- Check k-successors

$P_3 = (AB)(D)(G)(CE)(F)$

$P_4 = (A)(B)(D)(G)(CE)(F)$

$P_5 = P_4$


- Assume  $- = 1$

$P_2 = (AD)(BCEFG)$

$P_3 = (AD)(B)(CEFG)$   $P_4 = (AD)(B)(CEG)(F)$   $P_5 = P_4$

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

# State Diagram for A Modulo-8 Counter

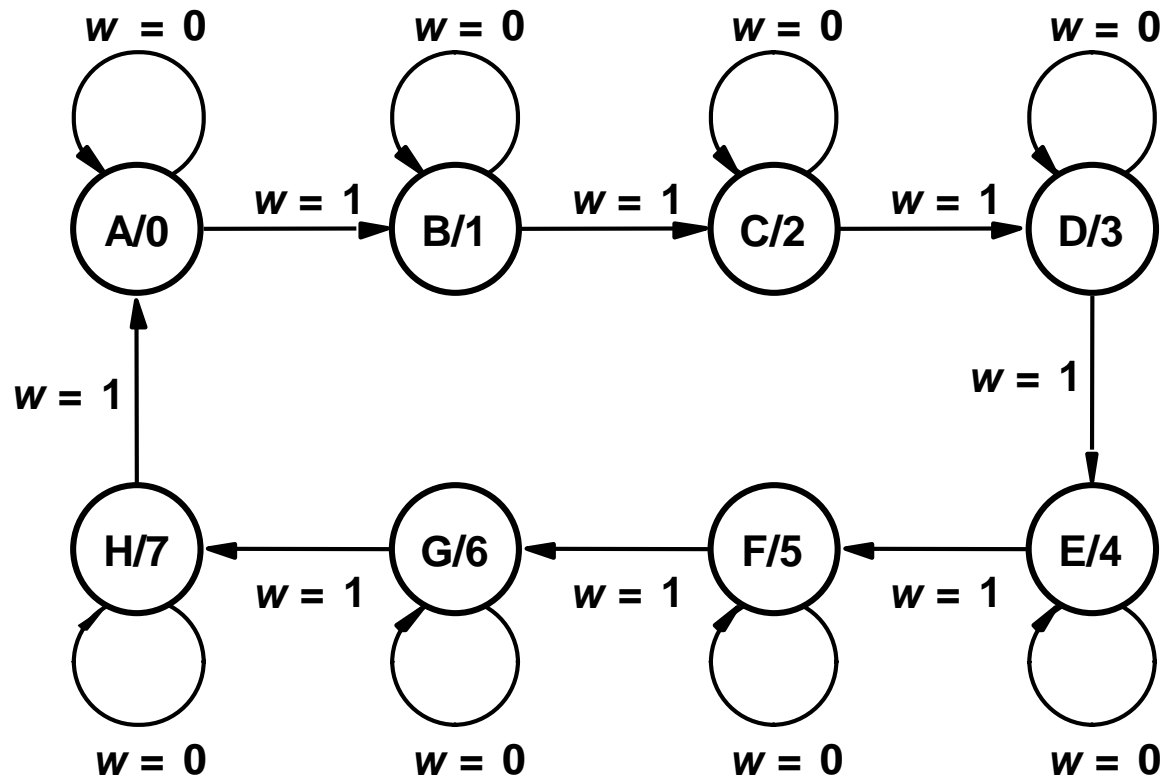

# State Table for A Modulo-8 Counter

Present state	Next state		Output	
	w = 0	w = 1		
A	A	B	0	A
B	B	C	1	B
C	C	D	2	C
D	D	E	3	D
E	E	F	4	E
F	F	G	5	F
G	G	H	6	G
H	H	A	7	H

Present state $y_2 y_1 y_0$	Next state		Count $z_2 z_1 z_0$
	w = 0	w = 1	
	$Y_2 Y_1 Y_0$	$Y_2 Y_1 Y_0$	
000	000	001	000
001	001	010	001
010	010	011	010
011	011	100	011
100	100	101	100
101	101	110	101
110	110	111	110
111	111	000	111

# Implementation Using D-type Flip-Flops

- $$D_0 = Y_0$$

$$= \bar{w}y_0 + w\bar{y}_0$$

$$= w \oplus y_0$$

		$y_1y_0$			
		00	01	11	10
$wy_2$	00	0	1	1	0
	01	0	1	1	0
	11	1	0	0	1
	10	1	0	0	1

$$Y_0 = \bar{w}y_0 + w\bar{y}_0$$

		$y_1y_0$			
		00	01	11	10
$wy_2$	00	0	0	1	1
	01	0	0	1	1
	11	0	1	0	1
	10	0	1	0	1

$$Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1$$

- $$D_1 = Y_1$$

$$= \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1$$

$$= wy_0 \oplus y_1$$

		$y_1y_0$			
		00	01	11	10
$wy_2$	00	0	0	0	0
	01	1	1	1	1
	11	1	1	0	1
	10	0	0	1	0

$$Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2$$


- $$D_2 = Y_2$$

$$= \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2$$

$$+ wy_0y_1\bar{y}_2$$

$$= wy_0y_1 \oplus y_2$$

# Circuit of the Counter<sub>w</sub>

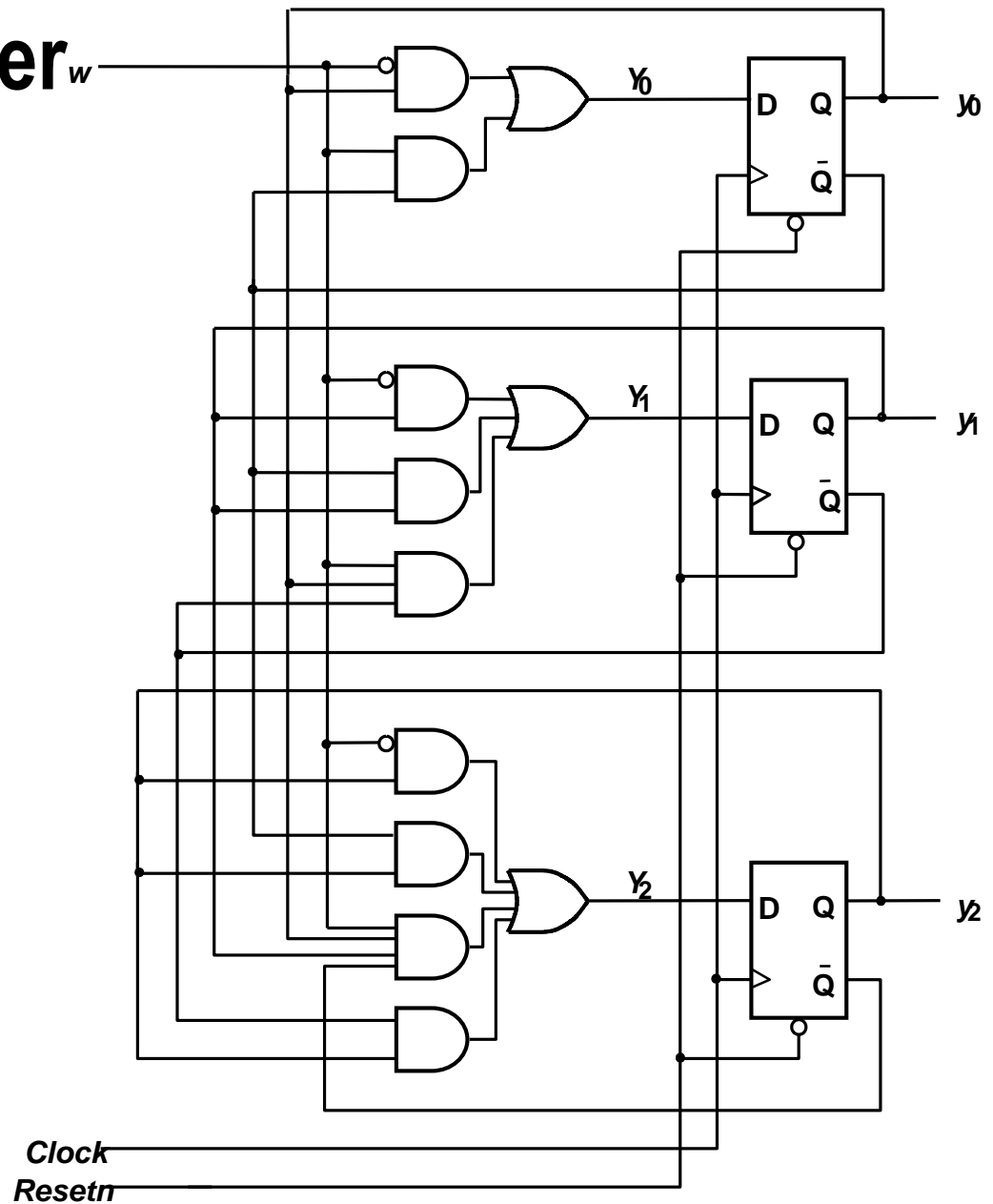

# Counting 0,4,2,6,1,5,3,7,0,4 ...


$$D_2 = Y_2 = \overline{y_2}$$

$$D_1 = Y_1 = y_1 \oplus y_2$$



Present state	Next state	Output $z_2 z_1 z_0$
A	B	000
B	C	100
C	D	010
D	E	110
E	F	001
F	G	101
G	H	011
H	A	111

Present state $y_2 y_1 y_0$	Next state $Y_2 Y_1 Y_0$	Output $z_2 z_1 z_0$
000	100	000
100	010	100
010	110	010
110	001	110
001	101	001
101	011	101
011	111	011
111	000	111

# Different Counter Circuit Diagram

 


# Arbiter for a 3 Device System

  


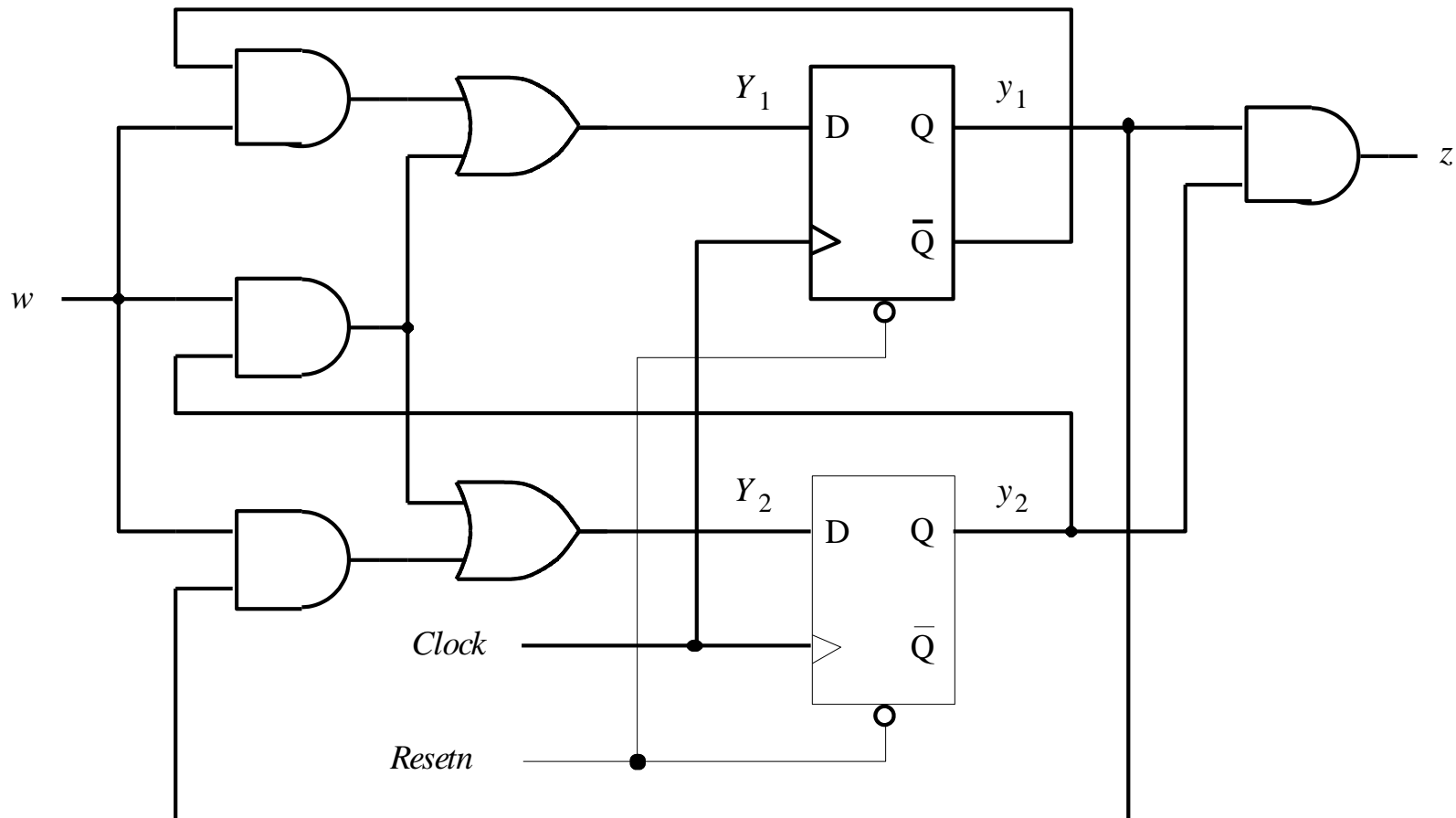
## Ex. 8.9 Analyze the FSM

•  $Y_1 = w\overline{y_1} + wy_2$     $Y_2 = wy_1 + wy_2$     $z = y_1y_2$




# State Table

•  $Y_1 = w\overline{y_1} + wy_2$     $Y_2 = wy_1 + wy_2$     $z = y_1y_2$


Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
0 0	0 0	0 1	0
0 1	0 0	1 0	0
1 0	0 0	1 1	0
1 1	0 0	1 1	1

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1


# Algorithmic State Machine (ASM) Charts

 

(a) State box


 


(b) Decision box


 


(c) Conditional output box

# ASM Style State Diagram

  

# ASM Style

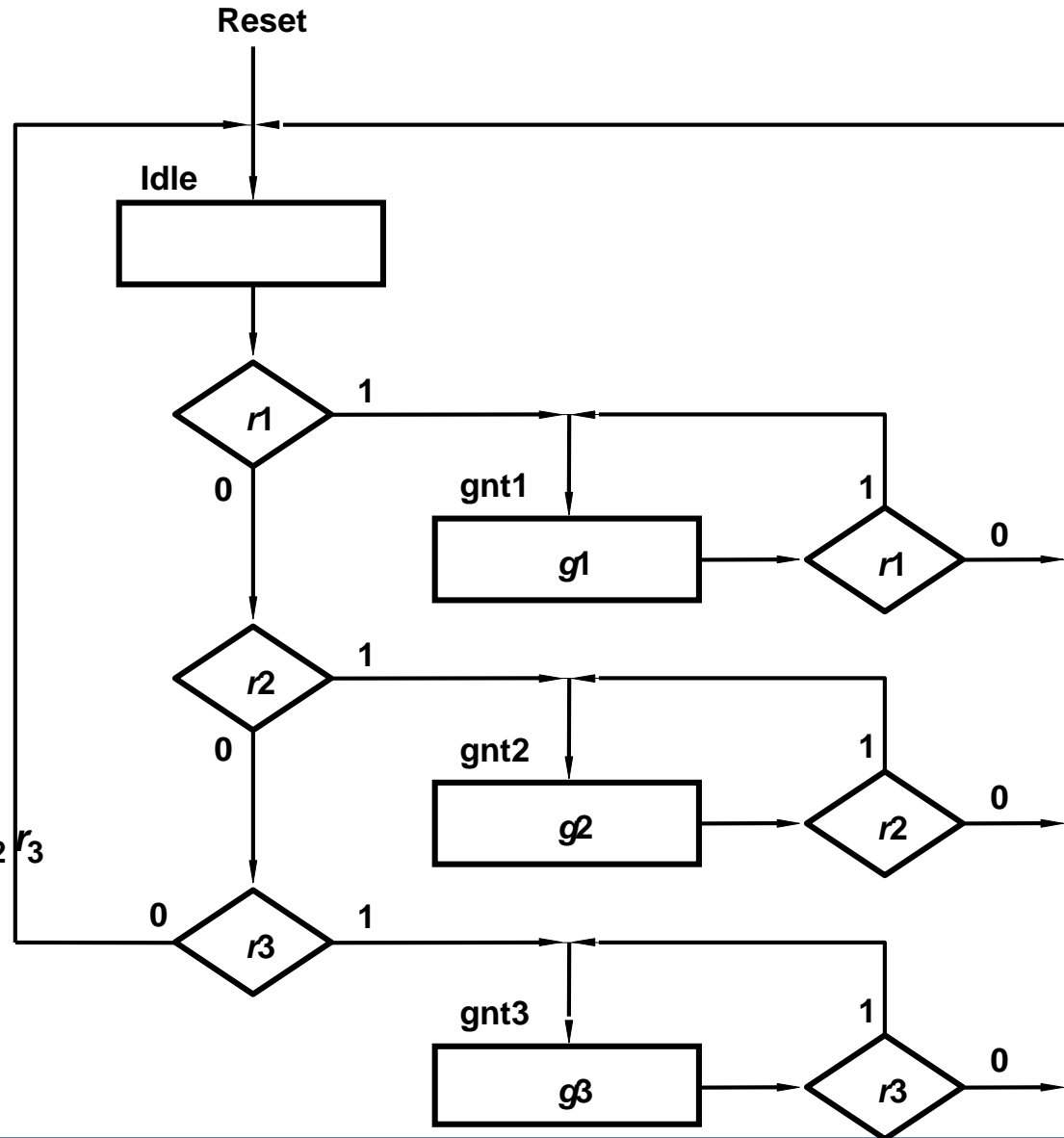 


# Mutual Exclusion and All Inclusion

- The transition expressions on arcs leaving a particular state must be mutually exclusive and all inclusive:
- Mutually exclusive: No two transition expressions can equal 1 for the same input combination, since a machine can't have two next states for one input combination.
- All inclusive: For every possible input combination, some transition expression must equal 1, so that all next states are defined.

# More Examples (not on our textbook)
 
# A State-Table Design Example

- Design a clocked synchronous state machine with two inputs, A and B, and a single output Z that is 1 if:
  - A had the same value at each of the two previous clock ticks, *or*
  - B has been 1 since the last time that the first condition was





# Evolution of State Table

(a)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT					0
...	...					
...	...					
...	...					

S\*

(b)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0					0
Got a 1 on A	A1					0

S\*

(c)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK	OK	A1	A1	0
Got a 1 on A	A1					0
Got two equal A inputs	OK					1

S\*

(d)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK	OK	A1	A1	0
Got a 1 on A	A1	A0	A0	OK	OK	0
Got two equal A inputs	OK					1

S\*

# Evolution of State Table (Cont')

(a)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK	OK	A1	A1	0
Got a 1 on A	A1	A0	A0	OK	OK	0
Got two equal A inputs	OK	?	OK	OK	?	1
S*						

(b)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK0	OK0	A1	A1	0
Got a 1 on A	A1	A0	A0	OK1	OK1	0
Two equal, A=0 last	OK0					1
Two equal, A=1 last	OK1					1
S*						


(c)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK0	OK0	A1	A1	0
Got a 1 on A	A1	A0	A0	OK1	OK1	0
Two equal, A=0 last	OK0	OK0	OK0	OK1	A1	1
Two equal, A=1 last	OK1					1
S*						

(d)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK0	OK0	A1	A1	0
Got a 1 on A	A1	A0	A0	OK1	OK1	0
Two equal, A=0 last	OK0	OK0	OK0	OK1	A1	1
Two equal, A=1 last	OK1	A0	OK0	OK1	OK1	1
S*						

# Timing Diagram with States

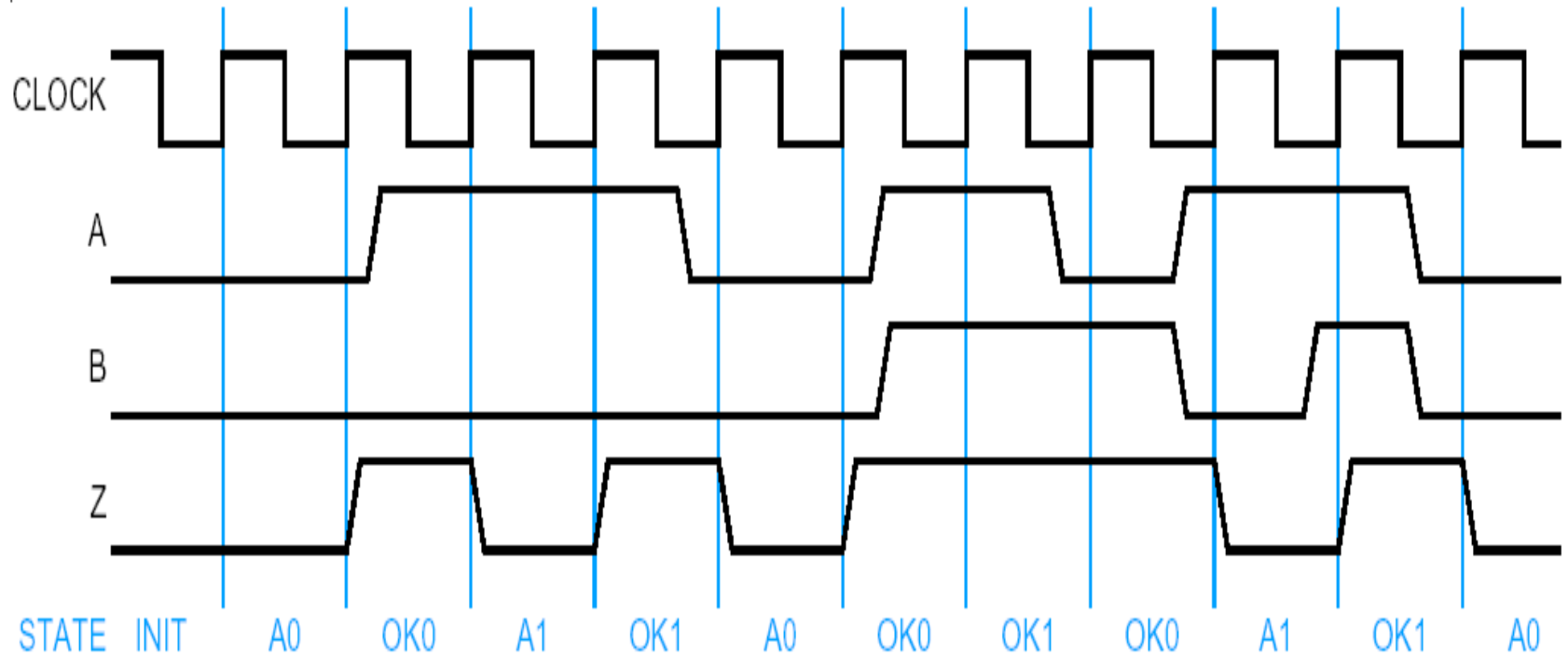

# State Minimization

- Two states S1 and S2 are equivalent if two conditions are true.
  - First, S1 and S2 must produce the same values at the state-machine output(s); in the Mealy machine, this must be true for all input combinations.
  - Second, for each input combination, S1 and S2 must have either the same next state or equivalent next states.

(a)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK00	OK00	A1	A1	0
Got a 1 on A	A1	A0	A0	OK11	OK11	0
Got 00 on A	OK00	OK00	OK00	OKA1	A1	1
Got 11 on A	OK11	A0	OKA0	OK11	OK11	1
OK, got a 0 on A	OKA0	OK00	OK00	OKA1	A1	1
OK, got a 1 on A	OKA1	A0	OKA0	OK11	OK11	1

S\*

(b)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK00	OK00	A1	A1	0
Got a 1 on A	A1	A0	A0	OK11	OK11	0
Got 00 on A	OK00	OK00	OK00	A001	A1	1
Got 11 on A	OK11	A0	A110	OK11	OK11	1
Got 001 on A, B=1	A001	A0	AE10	OK11	OK11	1
Got 110 on A, B=1	A110	OK00	OK00	AE01	A1	1
Got bb...10 on A, B=1	AE10	OK00	OK00	AE01	A1	1
Got bb...01 on A, B=1	AE01	A0	AE10	OK11	OK11	1

S\*

# State Assignment Example

S	A B				Z
	00	01	11	10	
INIT	A0	A0	A1	A1	0
A0	OK0	OK0	A1	A1	0
A1	A0	A0	OK1	OK1	0
OK0	OK0	OK0	OK1	A1	1
OK1	A0	OK0	OK1	OK1	1

$S^*$

State name	Assignment			
	Simplest Q1–Q3	Decomposed Q1–Q3	One-hot Q1–Q5	Almost one-hot Q1–Q4
INIT	000	000	00001	0000
A0	001	100	00010	0001
A1	010	101	00100	0010
OK0	011	110	01000	0100
OK1	100	111	10000	1000

# Unused States

- *Minimal risk* : Assumes that it is possible for the state machine somehow to get into one of the unused (or “illegal”) states, perhaps because of a hardware failure, an unexpected input, or a design error. Therefore, all of the unused state-variable combinations are identified and explicit next-state entries are made so that, for any input combination, the unused states go to the “initial” state, the “idle” state, or some other “safe” state.
- *Minimal cost* : Assumes that the machine will never enter an unused state. Therefore, in the transition and excitation tables, the next-state entries of the unused states can be marked as “don’t-cares.” In most cases this simplifies the excitation logic. However, the machine’s behavior may be weird if it ever does enter an unused state.

# Transition/ Excitation Table

- Transition/Output table.

			A B				Z
Q1	Q2	Q3	00	01	11	10	
000			100	100	101	101	0
100			110	110	101	101	0
101			100	100	111	111	0
110			110	110	111	101	1
111			100	110	111	111	1
			Q1* Q2* Q3*				


- Excitation/Output table.

			A B				Z
Q1	Q2	Q3	00	01	11	10	
000			100	100	101	101	0
100			110	110	101	101	0
101			100	100	111	111	0
110			110	110	111	101	1
111			100	110	111	111	1
			D1 D2 D3				



# Minimal Risk Excitation Maps

Minimal risk: Assume unused states go to state 000

			A B				
Q1	Q2	Q3	00	01	11	10	Z
000			100	100	101	101	0
100			110	110	101	101	0
101			100	100	111	111	0
110			110	110	111	101	1
111			100	110	111	111	1
			D1 D2 D3				

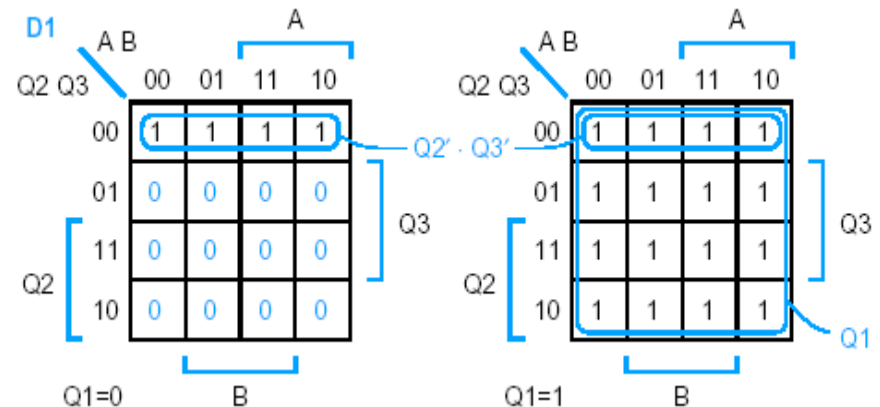

$$D1 = Q1 + Q2' \cdot Q3'$$

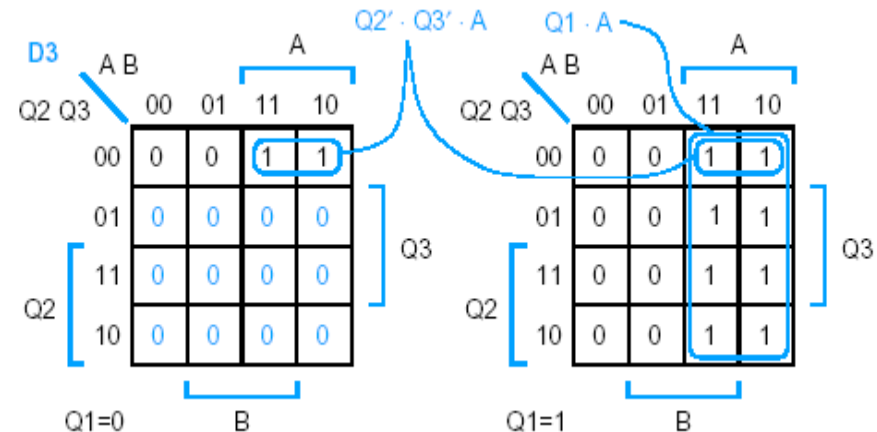 

$$D2 = Q1 \cdot Q3' \cdot A' + Q1 \cdot Q3 \cdot A + Q1 \cdot Q2 \cdot B \quad D3 = Q1 \cdot A + Q2' \cdot Q3' \cdot A$$




# Minimal Risk Logic Equation

- Excitation equations
  - $D1 = Q1 + Q2' \cdot Q3'$
  - $D2 = Q1 \cdot Q3' \cdot A' + Q1 \cdot Q3 \cdot A + Q1 \cdot Q2 \cdot B$
  - $D3 = Q1 \cdot A + Q2' \cdot Q3' \cdot A$
- Output Equations ( $Z = 1$  for 110 and 111)
  - $Z = Q1 \cdot Q2 \cdot Q3' + Q1 \cdot Q2 \cdot Q3$   
 $= Q1 \cdot Q2$


# Minimal Cost Excitation Map

- Next-state of unused states are “don't care”.
- Output equation  $Z = Q2$ .

			A B				
Q1	Q2	Q3	00	01	11	10	Z
000			100	100	101	101	0
100			110	110	101	101	0
101			100	100	111	111	0
110			110	110	111	101	1
111			100	110	111	111	1
			D1 D2 D3				

 

$$D1 = 1$$

 

$$D2 = Q1 \cdot Q3' \cdot A' + Q3 \cdot A + Q2 \cdot B$$