


Lecture 3

Implementation Technology





吳文中

Representation of logic values by voltage levels

 - Positive logic : 0 and 1 referred to low and high.
- Negative logic : 1 and 0 referred to low and high.
- $V_{dd} = 5V$ conventionally, 3.3V->2.5V->1.8V->1.3V->~1V evolutionally.




NMOS and PMOS Transistors as Switches

    


(a) A simple switch controlled by the input x

 
(a) A switch with the opposite behavior to left




(b) NMOS transistor

 

(b) PMOS transistor

 



 
(c) Simplified symbol for an NMOS transistor



(c) Simplified symbol for a PMOS transistor

NMOS and PMOS Transistors in Logic Circuits




- NMOS

   

Closed switch
when $V_G = V_{DD}$

Open switch
when $V_G = 0\text{ V}$

- PMOS


 
 
 


Open switch
when $V_G = V_{DD}$


Closed switch
when $V_G = 0\text{ V}$

A NOT Gate Built with NMOS Tehcnology

   
 
- Power consumption: V_{DD}^2/R when $V_x = V_{DD}$




NMOS Realization of a NAND gate

 



x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

  



NMOS Realization of a NOR Gate

 

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0

  


NMOS Realization of AND and OR Gates

  


Structure of NMOS and CMOS Circuits

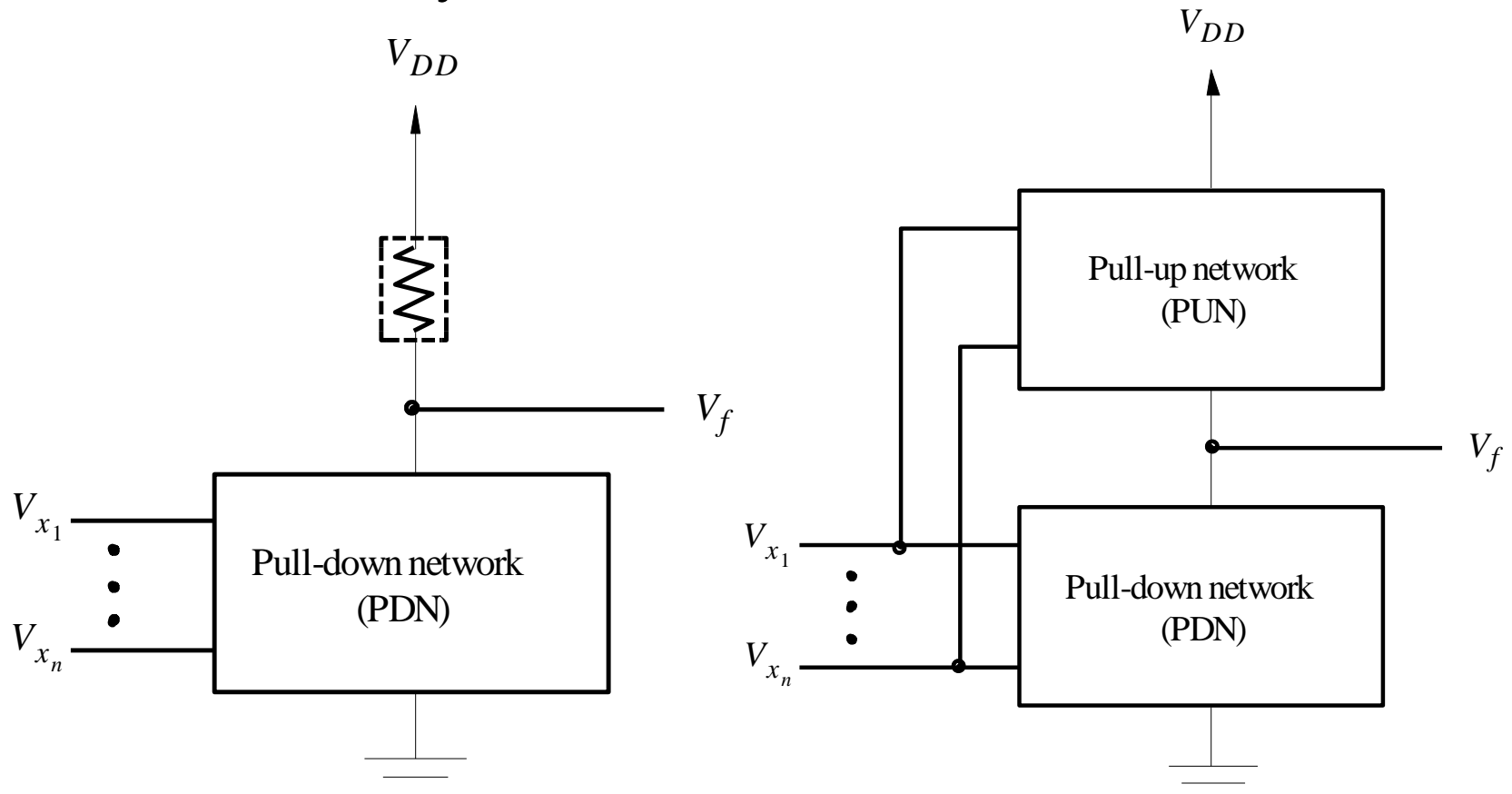- Resistors are replaced as PMOS transistors, and thus $P=0$ theoretically.




CMOS Realization of a NOT Gate

 

X	T_1	T_2	f
0	on	off	1
1	off	on	0


CMOS Realization of a NAND Gate

 

- PUN: $f = \overline{x_1 x_2} = \overline{x_1} + \overline{x_2}$
- PDN: $\bar{f} = x_1 x_2$

x_1	x_2	T_1	T_2	T_3	T_4	f
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

CMOS Realization of an NOR Gate

 


- PUN: $f = \overline{x_1 + x_2} = \overline{x_1 x_2}$
- PDN: $\bar{f} = x_1 + x_2$

x_1	x_2	T_1	T_2	T_3	T_4	f
0	0	on	on	off	off	1
0	1	on	off	off	on	0
1	0	off	on	on	off	0
1	1	off	off	on	on	0

CMOS Realization of an AND Gate

- NAND + NOT

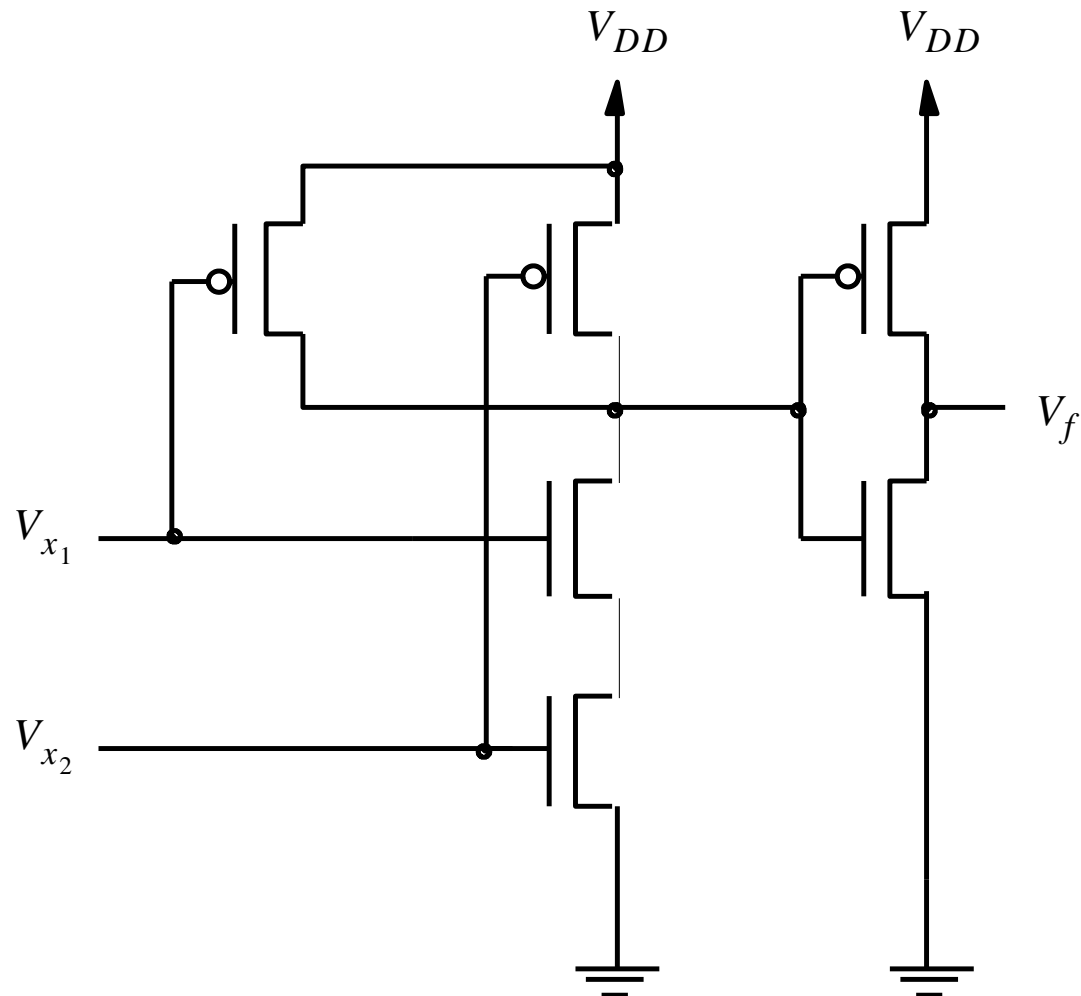

Negative Logic System - NAND

- Voltage level



V_{x_1}	V_{x_2}	V_f
L	L	H
L	H	H
H	L	H
H	H	L

Positive logic

x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

Negative logic



x_1	x_2	f
1	1	0
1	0	0
0	1	0
0	0	1

  


Negative Logic System - AND

- Voltage level Positive logic Negative logic


V_{x_1}	V_{x_2}	V_f	x_1	x_2	f	x_1	x_2	f
L	L	L	0	0	0	1	1	1
L	H	L	0	1	0	1	0	1
H	L	L	1	0	0	0	1	1
H	H	H	1	1	1	0	0	0

  

7400-Series Standard Chips

 



Dual-inline package

 


Structure of 7404 chip

Implementation with 74xx

 


 


Programmable Logic Array (PLA)

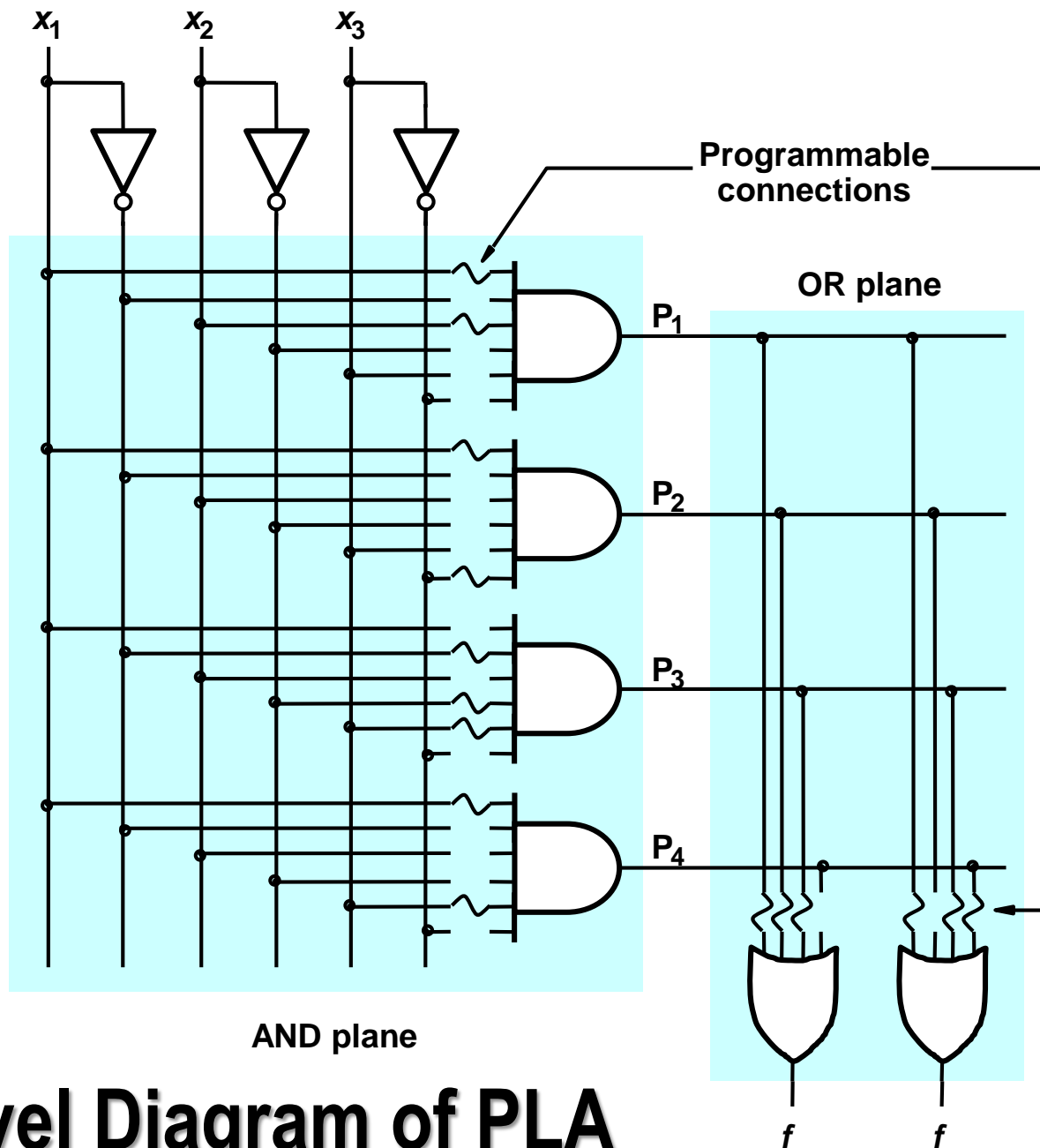

Gate-level Diagram of PLA

 

Customary Schematic for the PLA

 


AND plane


(Programmable Array Logic) PAL Example

Programming of PLD

 
- Old Fashion: Programmer
- Current technology: Field programming




Complex Programmable Logic Device (CPLD)

 


CPLD

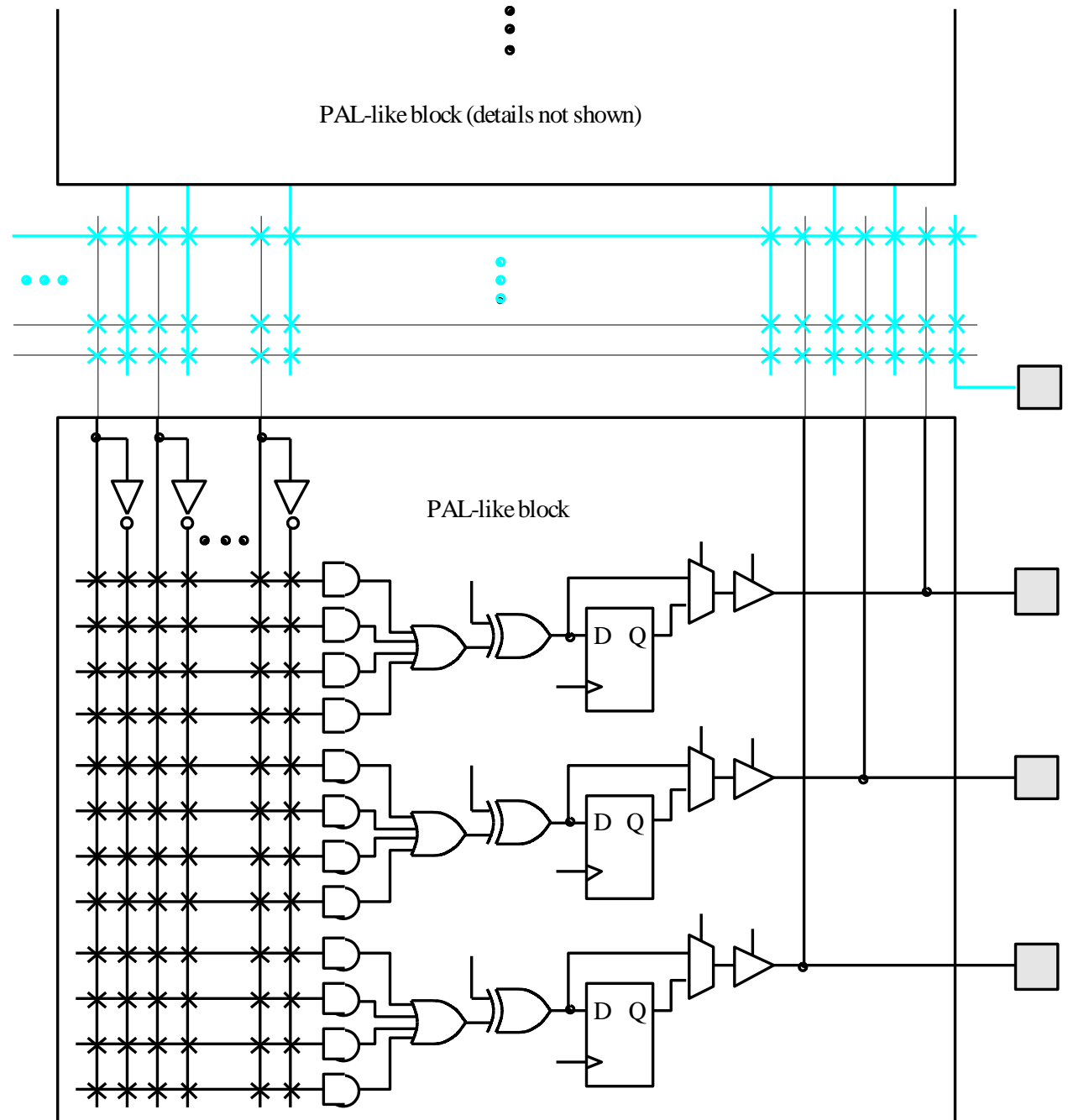


JTAG Programming

 


Field-Programmable Gate Arrays (FPGA)

 

Two-Input LUT (Look-up Table)

 

x_1	x_2	f_1
0	0	1
0	1	0
1	0	0
1	1	1

 

A Section of FPGA

