



# **Lecture 2**

## **Introduction to Logic Circuits**


吳文中
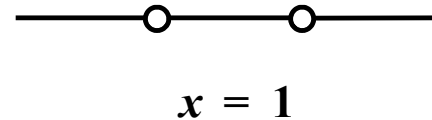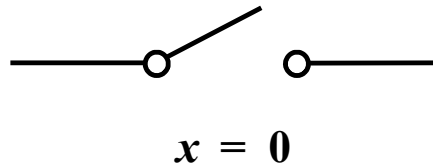
# One Variable Logic Function

- Simplest binary logic, a switch with two states.




- Symbol of a switch.

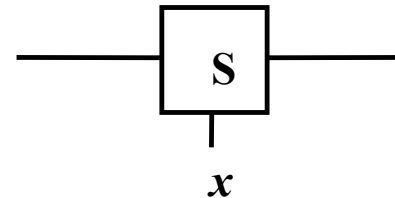

- Light control switch,  $L(x) = x$ , a one variable logic function.

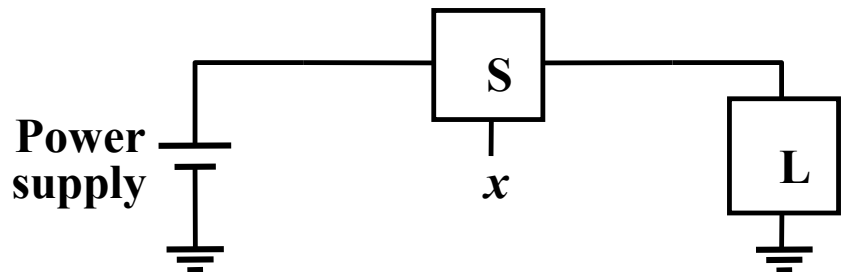- $- L = 1$  if  $x = 1$ .
- $- L = 0$  if  $x = 0$ .



# Two Variable Logic Function

- Two switches to control a lamp.


- And logic(series):

$$L(x_1) = x_1 \cdot x_2$$

$$-L = 1$$

if  $x_1 = 1$  and  $x_2 = 1$

$$-L = 0 \text{ otherwise.}$$

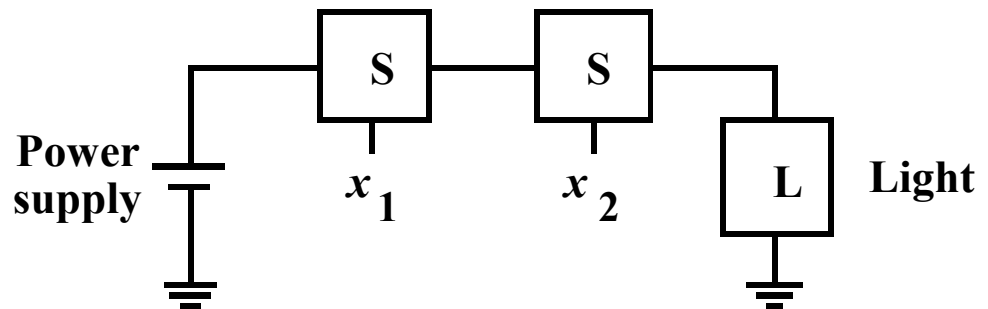


- Or logic(parallel):

$$L(x_1) = x_1 + x_2$$

$$-L = 1$$

if  $x_1 = 1$  or  $x_2 = 1$

$$-L = 0 \text{ otherwise}$$

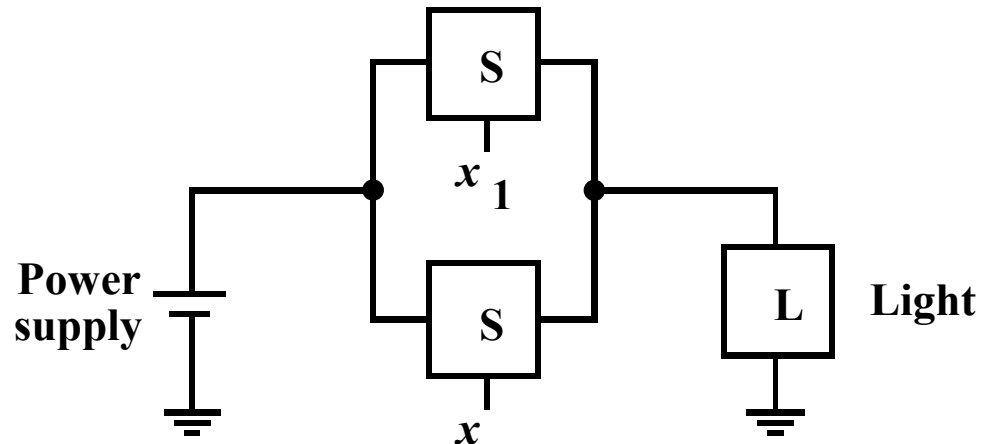


# Three Variable Logic Function

- $L(x_1) = (x_1 + x_2) \cdot x_3$

- $L = 1$  if  $x_3 = 1$  and, at the same time either  $x_1 = 1$  or  $x_2 = 1$

- $L = 0$  otherwise.

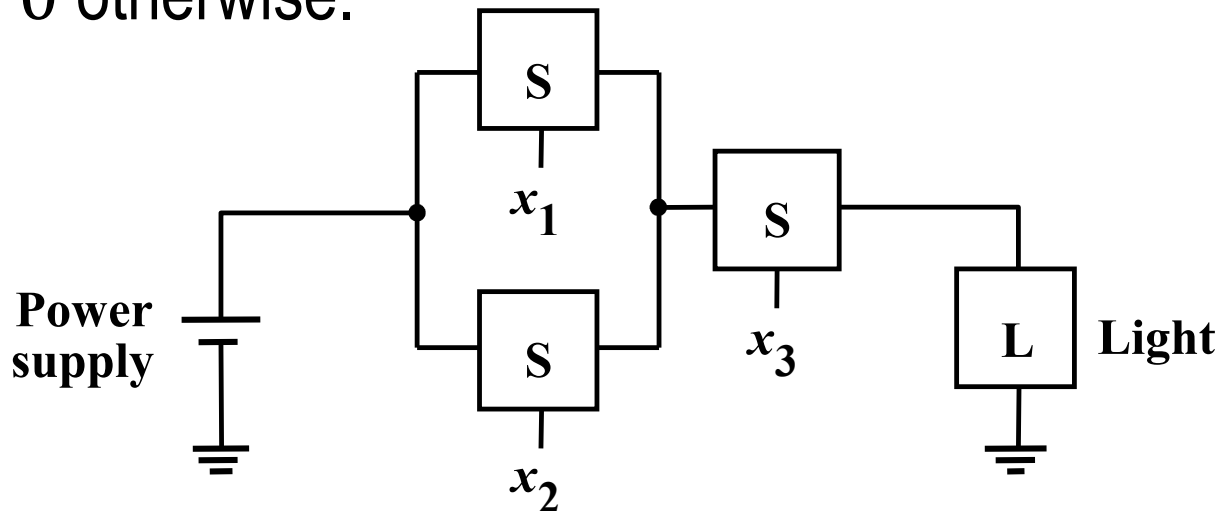


# Inversion Logic (One Variable)

- The light will be turned on when the switch is opened.

$$-L(x) = \bar{x}$$

$$-L = 1 \text{ if } x = 0$$

$$-L = 0 \text{ if } x = 1$$

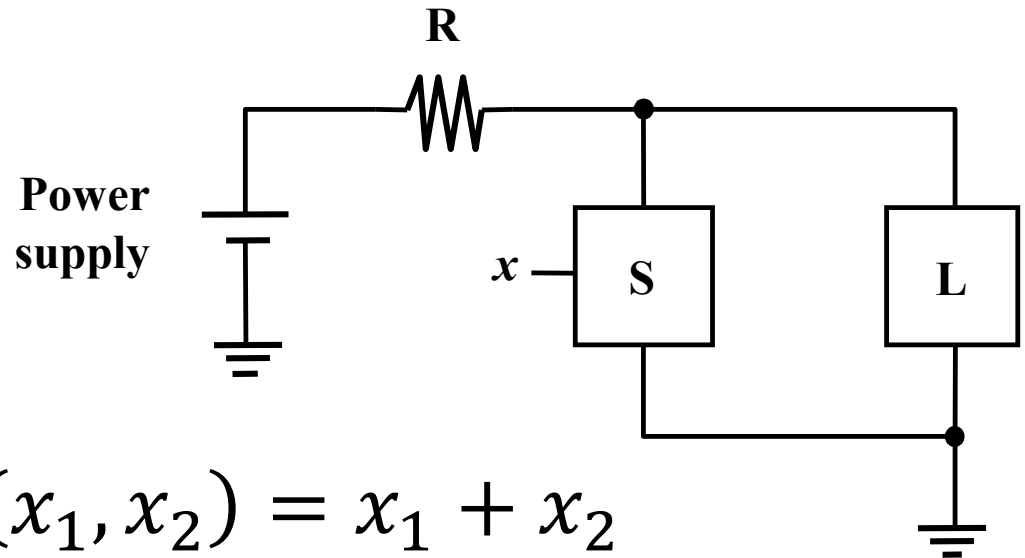

- $\bar{x} = x' = !x = \sim x$
- Complex operator:  $f(x_1, x_2) = x_1 + x_2$
- Complement function:  $\bar{f}(x_1, x_2) = \overline{x_1 + x_2}$
- $\overline{x_1 + x_2} = (x_1 + x_2)' = !(x_1 + x_2) = \sim(x_1 + x_2)$




# Truth Table

- A truth table for AND and OR operations.

$x_1$	$x_2$	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND



OR

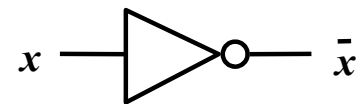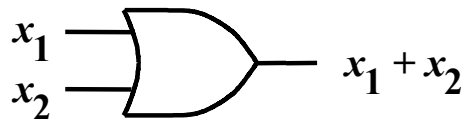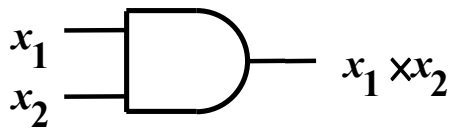

# Three-input to Multiple input AND, OR


- Truth table for 3 input AND, OR

$x_1$	$x_2$	$x_3$	$x_1 \cdot x_2 \cdot x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

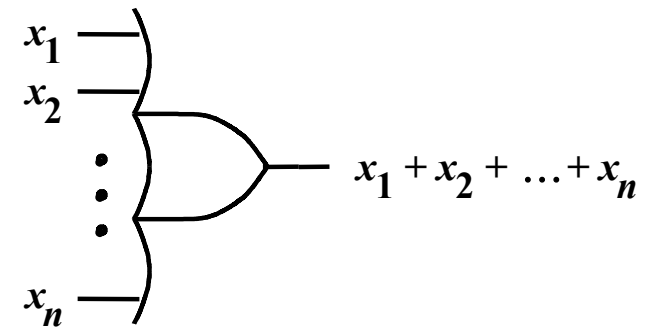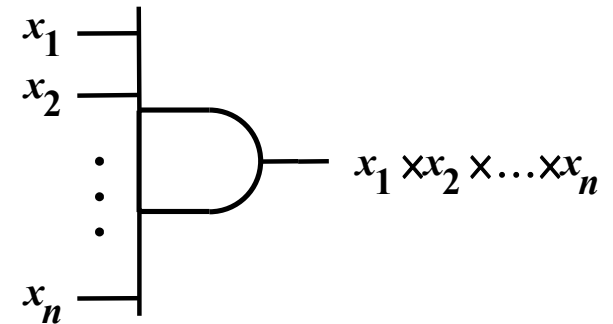

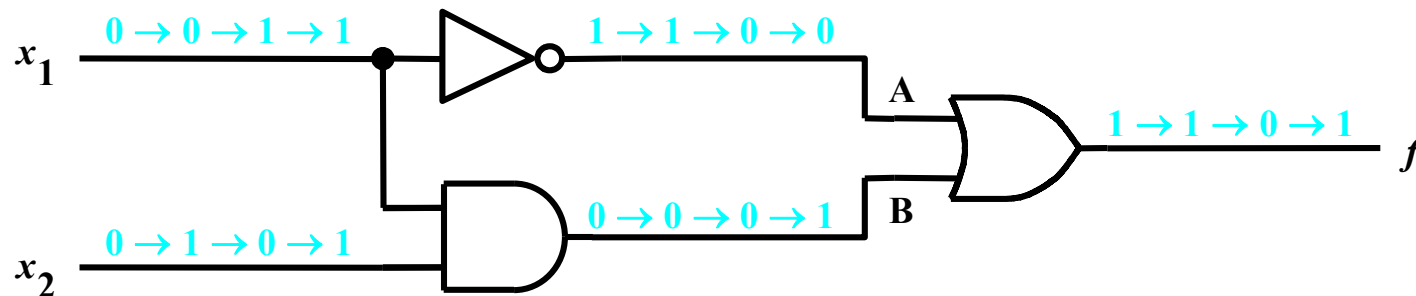
# Logic Network Analysis

- Network implements  $f = \bar{x}_1 + x_1 \cdot x_2$



- Truth table, Timing Diagram

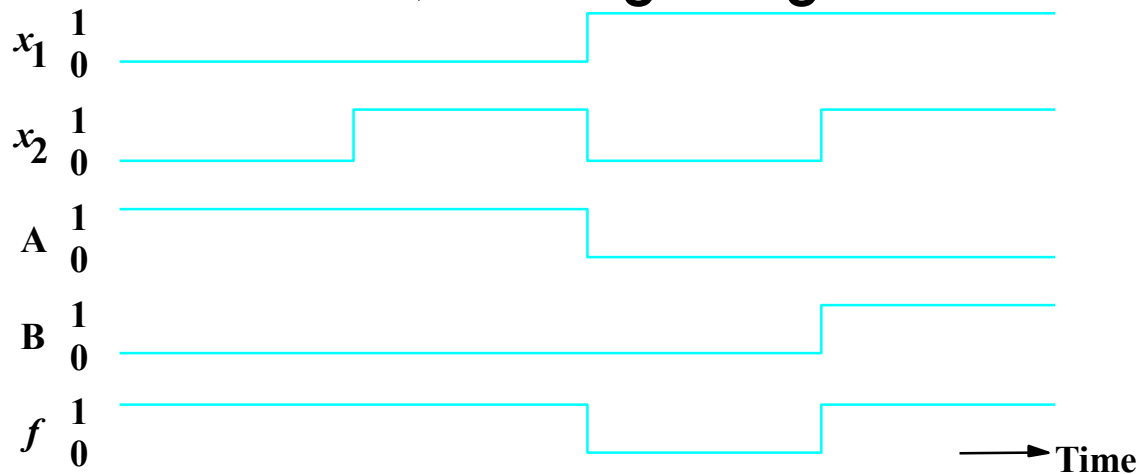

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

(b) Truth table for  $f$



# Switching Algebra

- In 1854, George Boole invented a 2-value algebraic system, now called Boolean algebra.
- In 1904, E. V. Huntington formulate the postulates as the formal definitions
- In 1938, Bell Labs researcher Claude E. Shannon showed how to adapt Boolean algebra to analyze and describe the behavior of circuits built from relays with his *switching algebra*.

# Basic Definition

- Boolean Algebra:
  - A deductive mathematical system
  - Defined with
    - A set of elements
      - ex:  $B = \{0, 1\}$
    - A set of operators
      - ex:  $+$ ,  $\cdot$ ,  $\square$
  - A number of unproved axioms or postulates

# Two-Valued Boolean Algebra

- A two-valued Boolean algebra is
- Defined on a set of two elements  $B = \{0, 1\}$
- With rules for the binary operators  $+$  and  $\cdot$

$x$	$y$	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

$x$	$y$	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

$x$	$x'$
0	1
1	0

- Called “switching algebra”, “binary logic”

# Axioms of Boolean Algebra

- 1a.  $0 \cdot 0 = 0$
- 1b.  $1 + 1 = 1$
- 2a.  $1 \cdot 1 = 1$
- 2b.  $0 + 0 = 0$
- 3a.  $0 \cdot 1 = 1 \cdot 0 = 0$
- 3b.  $1 + 0 = 0 + 1 = 1$
- 4a. If  $x = 0$ , then  $\bar{x} = 1$  (inverse)
- 4b. If  $x = 1$ , then  $\bar{x} = 0$

# Single-Variable Theorems

- 5a.  $x \cdot 0 = 0$
- 5b.  $x + 1 = 1$
- 6a.  $x \cdot 1 = x$  (identity)
- 6b.  $x + 0 = x$
- 7a.  $x \cdot x = x$
- 7b.  $x + x = x$
- 8a.  $x \cdot \bar{x} = 0$
- 8b.  $x + \bar{x} = 1$
- 9.  $\bar{\bar{x}} = x$

# Duality Principle

- Every Boolean algebraic expression remains valid if the operators and identity elements are interchanged
- Part (a) and part (b) are dual
- For one-variable Boolean algebra:
  - Interchange OR and AND operators and replace 1's by 0's and 0's by 1's
  - Ex:  $X + 1 = 1 \rightarrow X \cdot 0 = 0$


# Two- and Three- Variable Properties

- 10a.  $x \cdot y = y \cdot x$  (Commutative 交換率)
- 10b.  $x + y = y + x$
- 11a.  $x \cdot (y \cdot z) = (x \cdot y) \cdot z$  (Associative 結合率)
- 11b.  $x + (y + z) = (x + y) + z$
- 12a.  $x \cdot (y + z) = x \cdot y + x \cdot z$  (Distributive 分配率)
- 12b.  $x + y \cdot z = (x + y) \cdot (x + z)$
- 13a.  $x + x \cdot y = x$  (Absorption)
- 13b.  $x \cdot (x + y) = x$


# Two- and Three- Variable Properties

- 14a.  $x \cdot y + x \cdot \bar{y} = x$  (combining)
- 14b.  $(x + y) \cdot (x + \bar{y}) = x$
- 15a.  $\overline{x \cdot y} = \bar{x} + \bar{y}$  (DeMorgan's Theorem)
- 15b.  $\overline{x + y} = \bar{x} \cdot \bar{y}$

$x$	$y$	$x \cdot y$	$\overline{x \cdot y}$	$\bar{x}$	$\bar{y}$	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0



LHS



RHS



# Two- and Three- Variable Properties


- 16a.  $x + \bar{x} \cdot y = x + y$
- 16b.  $x \cdot (\bar{x} + y) = x \cdot y$
- 17a.  $x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$   
(consensus)
- 17b.  $(x + y) \cdot (y + z) \cdot (\bar{x} + z) =$   
 $(x + y) \cdot (\bar{x} + z)$

## Example 2.1

- Prove  $(x_1 + x_3) \cdot (\overline{x_1} + \overline{x_3}) = x_1 \cdot \overline{x_3} + \overline{x_1} \cdot x_3$
- LHS =  $(x_1 + x_3) \cdot \overline{x_1} + (x_1 + x_3) \cdot \overline{x_3}$  (12a.)
  - =  $x_1 \cdot \overline{x_1} + x_3 \cdot \overline{x_1} + x_1 \cdot \overline{x_3} + x_3 \cdot \overline{x_3}$  (12a.)
  - =  $0 + x_3 \cdot \overline{x_1} + x_1 \cdot \overline{x_3} + 0$  (8a.)
  - =  $x_3 \cdot \overline{x_1} + x_1 \cdot \overline{x_3}$  (6a.)
  - =  $x_1 \cdot \overline{x_3} + \overline{x_1} \cdot x_3$  (10a. and 10b.)
  - = RHS

•


# The Venn Diagram

 


(a) Constant 1




(b) Constant 0

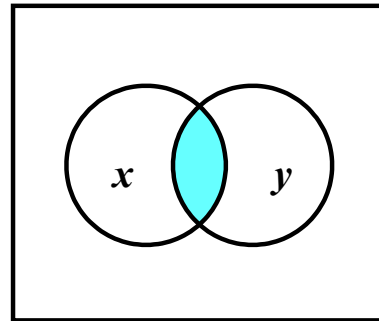


(e)  $x \times y$

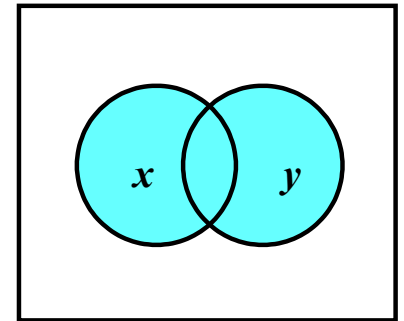


(f)  $x + y$

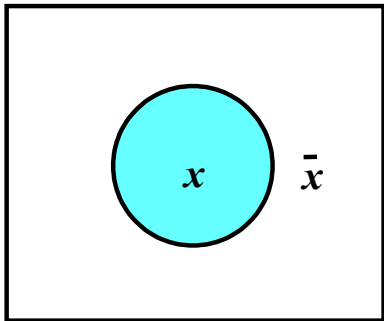


(c) Variable  $x$

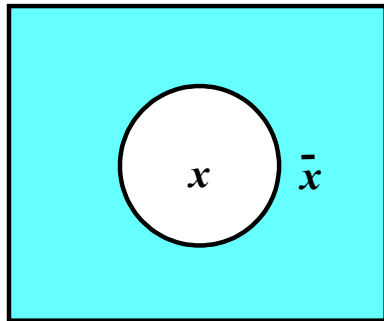

(d)  $\bar{x}$

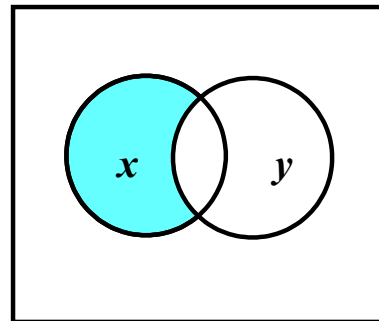


(g)  $x \times \bar{y}$

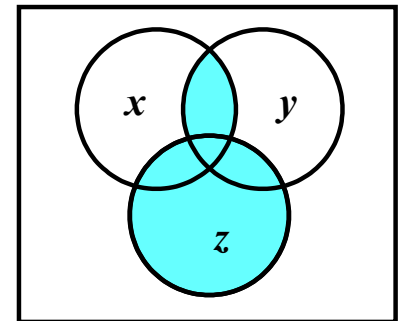


(h)  $x \times y + z$
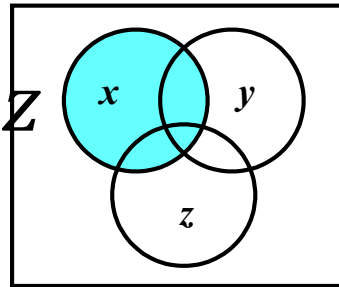
# Verification of Distributive Property


$$\bullet x \cdot (y + z) = x \cdot y + x \cdot z$$




(a)  $x$

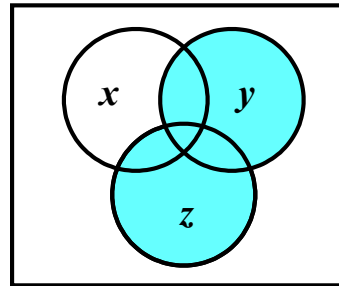


(b)  $y + z$

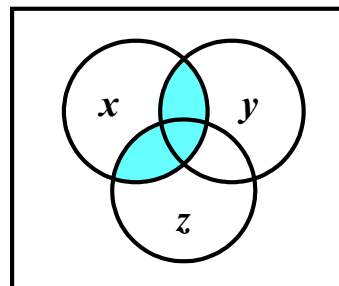


(c)  $x \times (y + z)$

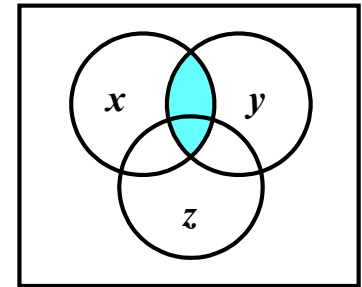

(d)  $x \times y$

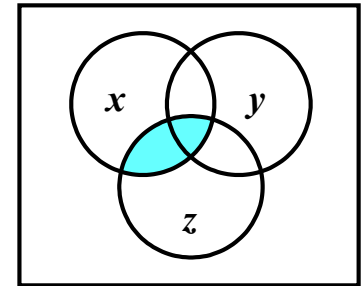

(e)  $x \times z$

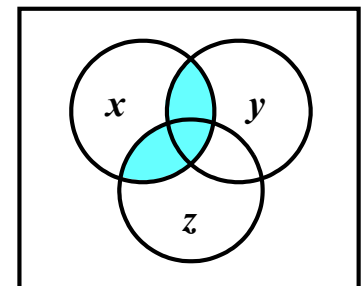

(f)  $x \times y + x \times z$

# Boolean v.s. Ordinary

## Boolean Algebra

- Associate law not included (but still valid)
- Distributive law is valid
- No additive or multiplicative inverses
- Define complement in axiom 4
- No. of elements is not clearly defined
  - 2 for two-valued Boolean algebra

## Ordinary Algebra

- Associate law included
- Distributive law may not valid
- Have additive and multiplicative inverses
- No complement operator
- Deal with real numbers
  - Infinite set of elements

# Notation and Terminology

- Boolean algebra is based on the AND and OR operations. We have adopted the symbols  $\cdot$  and  $+$  to denote these operations.
- Because of the similarity with the arithmetic addition and multiplication operation, the OR and AND operations are often called the *logical sum* and *logical product* operations, or to say simply *sum* and *product*.
- $x_1 \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_4 + x_2 \cdot x_3 \cdot \overline{x_4}$  : *sum* of three product terms.
- $(\overline{x_1} + x_3) \cdot (x_1 + \overline{x_3}) \cdot (\overline{x_2} + x_3 + x_4)$ : *product* of three sum terms.

# Minterms and Maxterms

			Minterms		Maxterms	
x	y	z	Term	Name	Term	Name
0	0	0	$x'y'z'$	$m_0$	$x+y+z$	$M_0$
0	0	1	$x'y'z$	$m_1$	$x+y+z'$	$M_1$
0	1	0	$x'yz'$	$m_2$	$x+y'+z$	$M_2$
0	1	1	$x'yz$	$m_3$	$x+y'+z'$	$M_3$
1	0	0	$xy'z'$	$m_4$	$x'+y+z$	$M_4$
1	0	1	$xy'z$	$m_5$	$x'+y+z'$	$M_5$
1	1	0	$xyz'$	$m_6$	$x'+y'+z$	$M_6$
1	1	1	$xyz$	$m_7$	$x'+y'+z'$	$M_7$

# Canonical Form

- $F_1 = x'y'z + xy'z' + xyz = m_1 + m_4 + m_7$

- $F_1' = x'y'z' + x'yz' + x'yz + xy'z + xyz'$

$$\rightarrow F_1 = (x+y+z)(x+y'+z)(x+y'+z')$$

$$(x'+y+z')(x'+y'+z)$$

$$= M_0 M_2 M_3 M_5 M_6$$

- Similarly:

$$F_2 = x'yz + xy'z + xyz' + xyz = m_3 + m_5 + m_6 + m_7$$

$$= (x+y+z)(x+y+z')(x+y'+z)(x'+y+z) = M_0 M_1 M_2 M_4$$

- Boolean functions expressed as a sum of minterms or product of maxterms are said to be in **canonical form**

$x$	$y$	$z$	$F_1$	$F_2$
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Notation for Sum of Minterms

- $F = A+B'C = ABC+ABC'+AB'C+AB'C'+A'B'C$   
 $= m_1+m_4+m_5+m_6+m_7$

- $F(A, B, C) = \Sigma(1,4,5,6,7)$

- $\Sigma$ : ORing of terms

- Can be derived directly from the truth table

$x$	$y$	$z$	$F_1$		
0	0	0	0		
0	0	1	1	$\rightarrow$	$m_1$
0	1	0	0		
0	1	1	0		
1	0	0	1	$\rightarrow$	$m_4$
1	0	1	1	$\rightarrow$	$m_5$
1	1	0	1	$\rightarrow$	$m_6$
1	1	1	1	$\rightarrow$	$m_7$

$\Sigma(1,4,5,6,7)$

# Conversion between Canonical Forms

- The complement of a function = the sum of minterms missing from the original function
- $F(A,B,C) = \Sigma(1,4,5,6,7)$
- $F'(A,B,C) = \Sigma(0,2,3) = m_0 + m_2 + m_3$
- From DeMorgan's theorem:
  - $F = (m_0 + m_2 + m_3)' = m_0' m_2' m_3' = M_0 M_2 M_3 = \Pi(0,2,3)$ 
    - $m_j' = M_j$  are shown in Table 2-3
- To convert from one canonical form to another:
  - Interchange the symbol  $\Sigma$  and  $\Pi$
  - List those numbers missing from the original form

# Conversion of Canonical Form

- $F = xy + x'z = x'y'z + x'yz + xyz' + xyz$

$x$	$y$	$z$	$F_1$		
0	0	0	0		
0	0	1	1	$\rightarrow$	$m_1$
0	1	0	0		
0	1	1	1	$\rightarrow$	$m_3$
1	0	0	0		
1	0	1	0		
1	1	0	1	$\rightarrow$	$m_6$
1	1	1	1	$\rightarrow$	$m_7$

$\left. \begin{array}{l} m_1 \\ m_3 \\ m_6 \\ m_7 \end{array} \right\} \Sigma(1,3,6,7)$

- The missing numbers are 0, 2, 4, 5  
 $-F = \Pi(0,2,4,5)$

# Standard Forms


- The canonical forms are basic forms obtained from the truth table
  - Very seldom to have the least number of literals
- Standard forms : not required to have all variables in each term
  - **Sum of products** [ex:  $F_1 = y' + xy + x'yz'$  ]
  - **Product of sums** [ex:  $F_2 = x(y' + z)(x' + y + z')$  ]
- Results in a two-level gating structure

# A Two-Variable Function to be Synthesized


- $f(x_1, x_2) = m_0 + m_1 + m_3$   
 $= x_1 x_2 + \overline{x_1} \overline{x_2} + \overline{x_1} x_2$   
 $= x_1 x_2 + \overline{x_1} \overline{x_2} + \overline{x_1} x_2 + \overline{x_1} x_2 \quad (7a)$   
 $= (x_1 + \overline{x_1}) x_2 + \overline{x_1} (\overline{x_2} + x_2) \quad (12a)$   
 $= 1 \cdot x_2 + \overline{x_1} \cdot 1 \quad (8b)$   
 $= x_2 + \overline{x_1} \quad (6a)$

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

# Synthesized Schematic

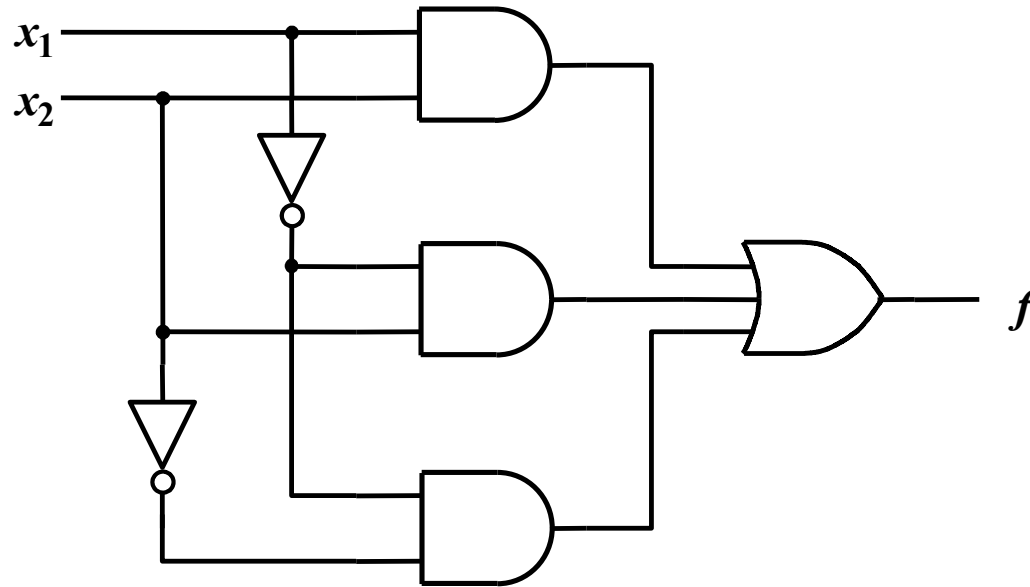

(a) Canonical sum-of-products

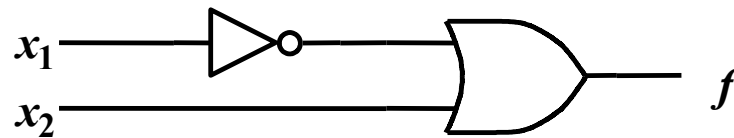


(b) Minimal-cost realization


## Example 2.3

- $f(x_1, x_2, x_3) = \sum m(2,3,4,6,7)$
- $f = m_2 + m_3 + m_4 + m_6 + m_7$   
 $= \overline{x_1}x_2\overline{x_3} + \overline{x_1}x_2x_3 + x_1\overline{x_2}\overline{x_3} + x_1x_2\overline{x_3} + x_1x_2x_3$   
 $= \overline{x_1}x_2(\overline{x_3} + x_3) + x_1(\overline{x_2} + x_2)\overline{x_3} + x_1x_2(\overline{x_3} + x_3)$   
 $= \overline{x_1}x_2 + x_1\overline{x_3} + x_1x_2$   
 $= (\overline{x_1} + x_1)\overline{x_2} + x_1\overline{x_3}$   
 $= \overline{x_2} + x_1\overline{x_3}$

# NAND and NOR Gates

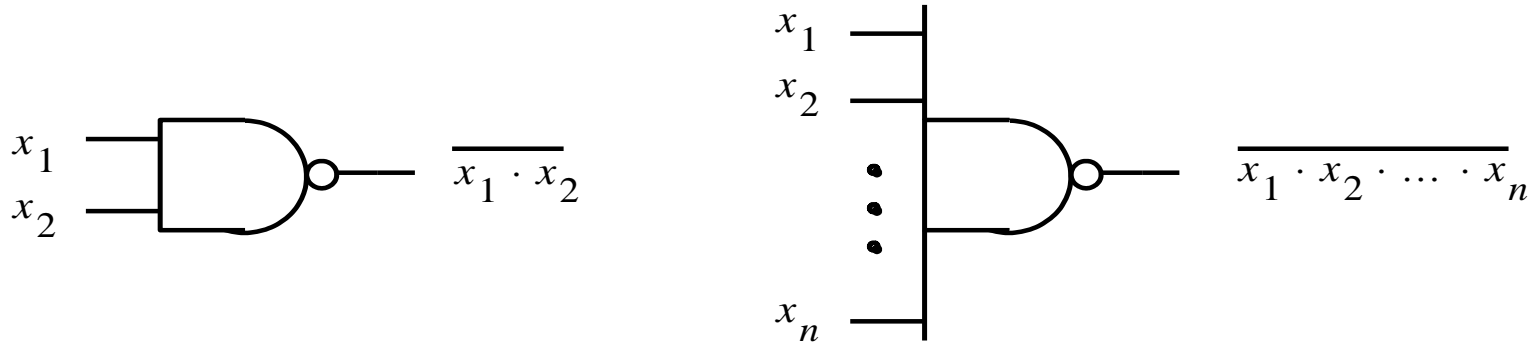


(a) NAND gates

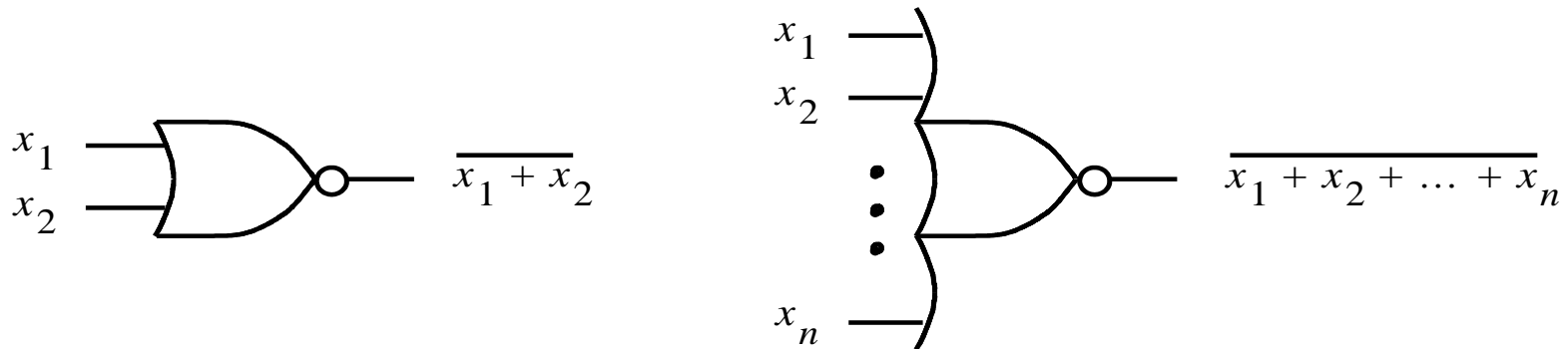


(b) NOR gates



# Derivation with DeMorgan's Theorem

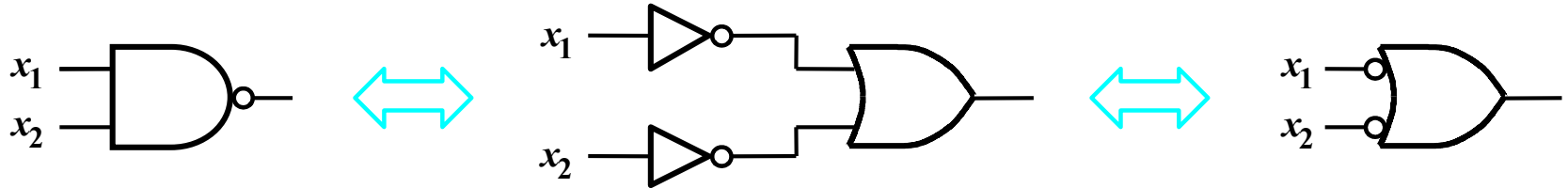

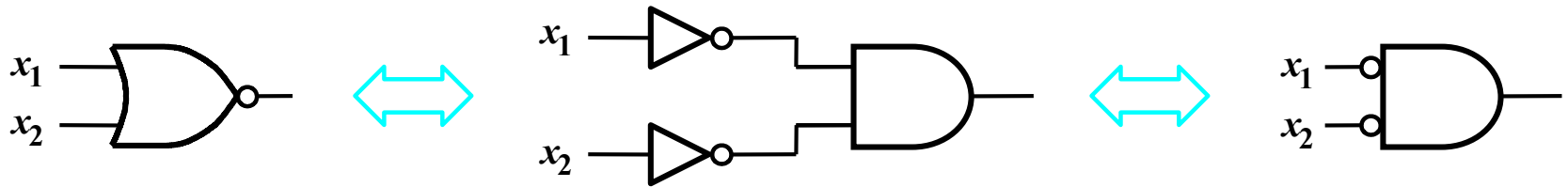
$$(a) \overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$$







$$(b) \overline{x_1 + x_2} = \bar{x}_1 \bar{x}_2$$
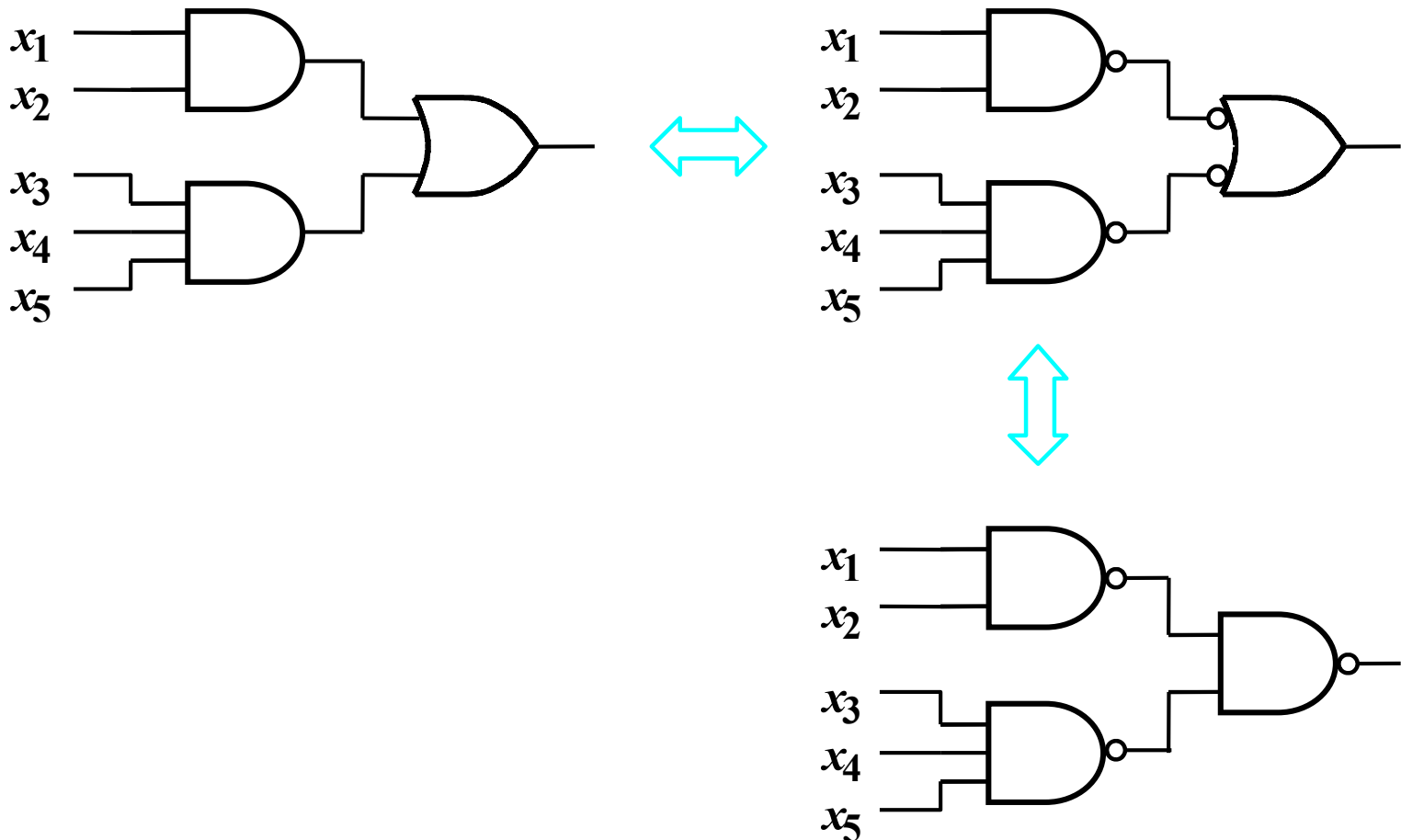
# Sum of Product Realization with NAND Gates


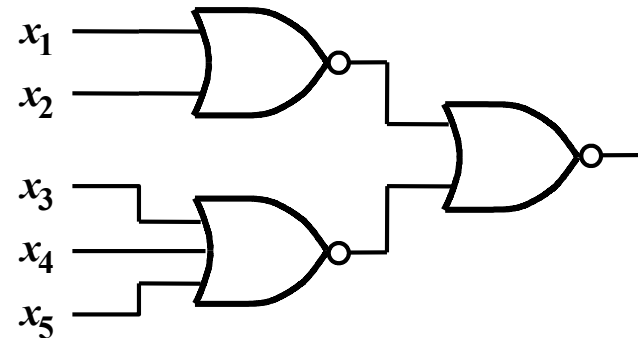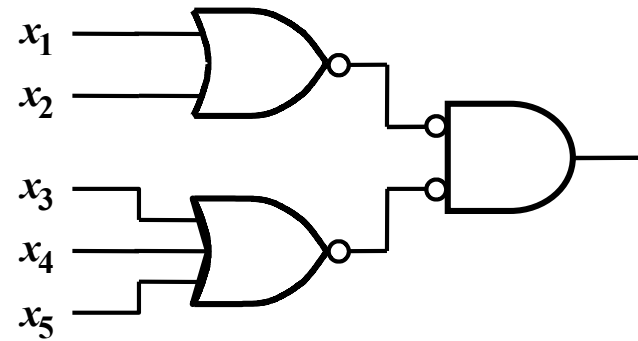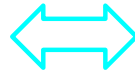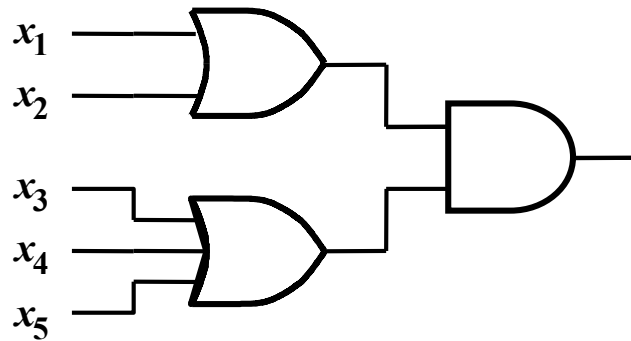
# Product of Sum Realization with NOR Gates




# Three Way Light Switch Control

$$\begin{aligned} \bullet f &= m_1 + m_2 + m_4 + m_7 \\ &= \overline{x_1}x_2x_3 + \overline{x_1}x_2\overline{x_3} + x_1\overline{x_2}x_3 + x_1x_2x_3 \end{aligned}$$


$$\begin{aligned} \bullet f &= M_0 \cdot M_3 \cdot M_5 \cdot M_6 \\ &= (x_1 + x_2 + x_3)(x_1 + \overline{x_2} + \overline{x_3}) \\ &\quad (\overline{x_1} + x_2 + \overline{x_3})(\overline{x_1} + \overline{x_2} + x_3) \end{aligned}$$

$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# SOP Realization

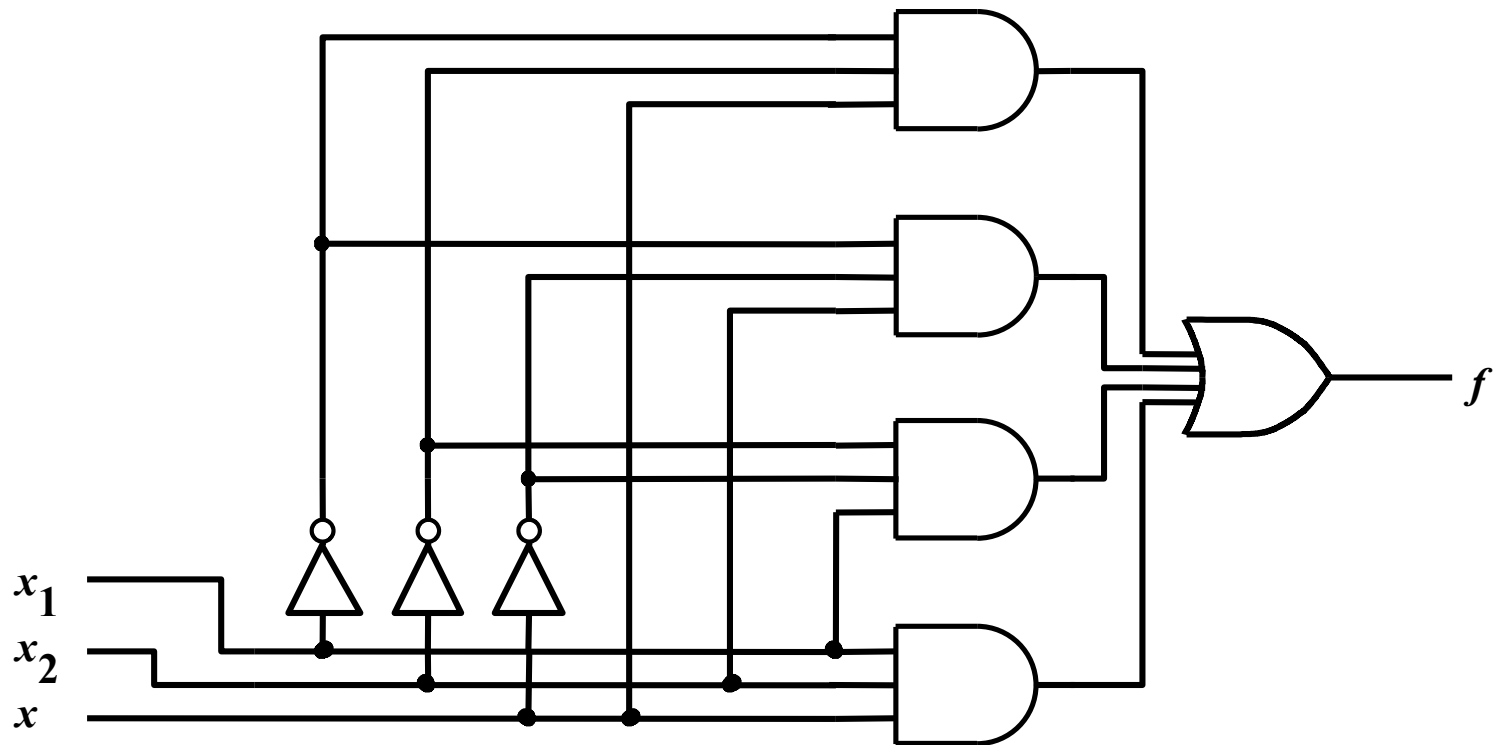


# POS Realization

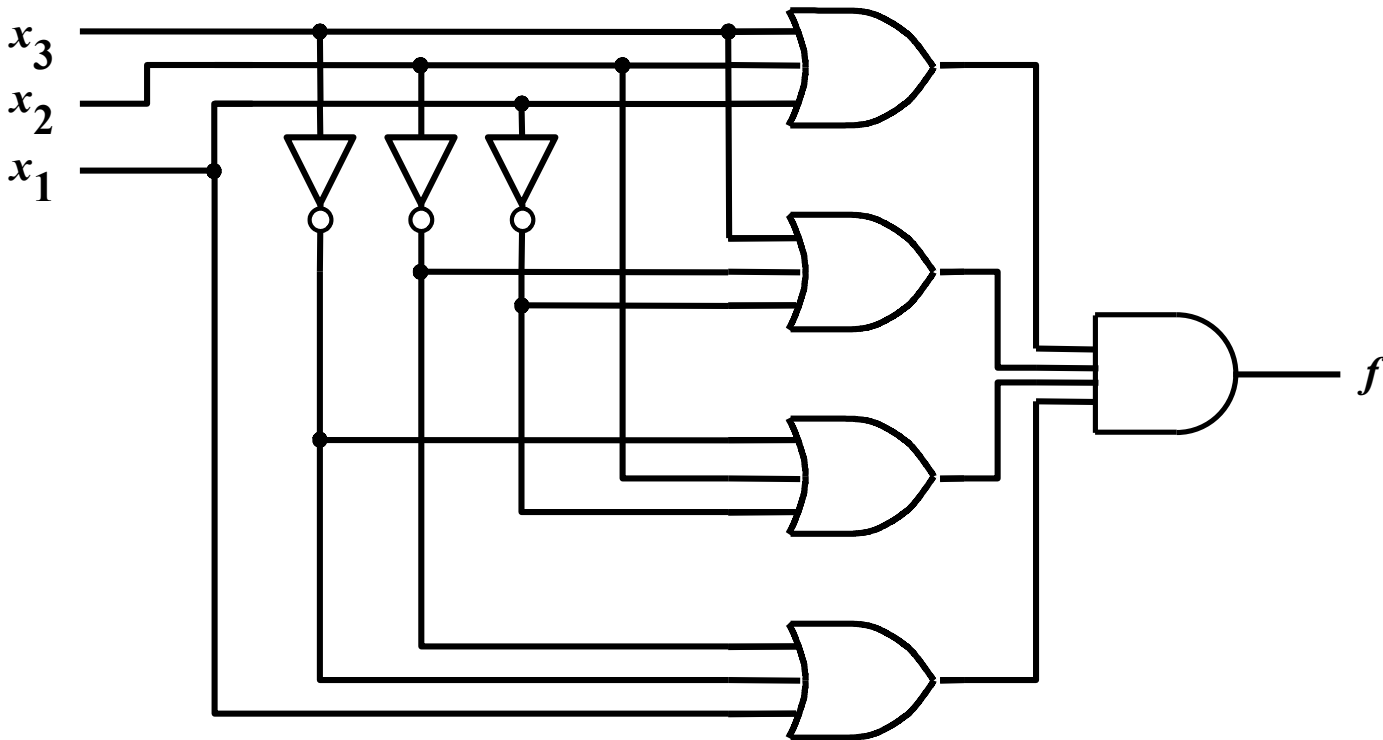

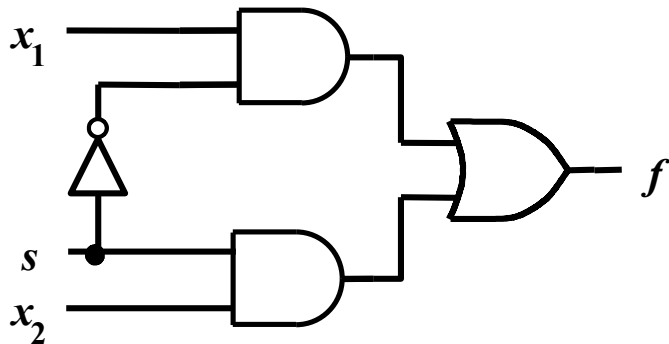
# Multiplexer Circuit

$$\begin{aligned}
 \bullet f(s, x_1, x_2) &= \bar{s}x_1\bar{x}_2 + \bar{s}x_1x_2 \\
 &\quad + s\bar{x}_1x_2 + sx_1x_2 \\
 &= \bar{s}x_1(\bar{x}_2 + x_2) + s(\bar{x}_1 + x_1)x_2 \\
 &= \bar{s}x_1 \cdot 1 + s \cdot 1 \cdot x_2 \quad (8b) \\
 &= \bar{s}x_1 + sx_2 \quad (6a)
 \end{aligned}$$



$s$	$f(s, x_1, x_2)$
0	$x_1$
1	$x_2$

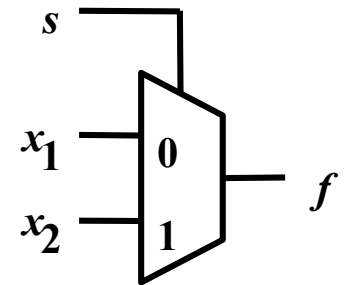

$s x_1 x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1