

Lecture 4

Optimized Implementation of Logic Functions

吳文中

Karnaugh Map

- $f = m_0 + m_2 + m_4 + m_5 + m_6$

- $= \overline{x_1} \overline{x_2} \overline{x_3} + \overline{x_1} x_2 \overline{x_3} + x_1 \overline{x_2} \overline{x_3} + x_1 \overline{x_2} x_3 + x_1 x_2 \overline{x_3}$

- $= \overline{x_1} \overline{x_2} \overline{x_3} + \overline{x_1} x_2 \overline{x_3} + x_1 \overline{x_2} \overline{x_3} + x_1 \overline{x_2} x_3 + x_1 x_2 \overline{x_3}$

- $= \overline{x_1} (\overline{x_2} + x_2) \overline{x_3} + x_1 (\overline{x_2} + x_2) \overline{x_3} + x_1 \overline{x_2} (x_3 + \overline{x_3})$

- $= \overline{x_1} \overline{x_3} + x_1 \overline{x_3} + x_1 \overline{x_2}$

- $= \overline{x_3} + x_1 \overline{x_2}$

Row number	x_1	x_2	x_3	f
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Karnaugh Map

	x_1	x_2	x_3
m_0	0	0	0
m_2	0	1	0
m_4	1	0	0
m_6	1	1	0

$$\overline{x_1 x_3}$$

$$x_1 \overline{x_3}$$



	x_1	x_2	x_3
m_4	1	0	0
m_5	1	0	1

$$x_1 \overline{x_2}$$

Two-variable Karnaugh Map

- $m_2 + m_3 = x_1\bar{x}_2 + x_1x_2$
- $= x_1(\bar{x}_2 + x_2)$
- $= x_1$

x_1	x_2	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

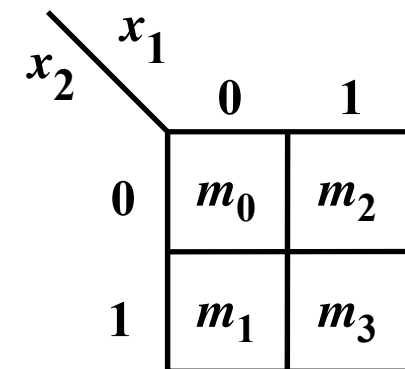
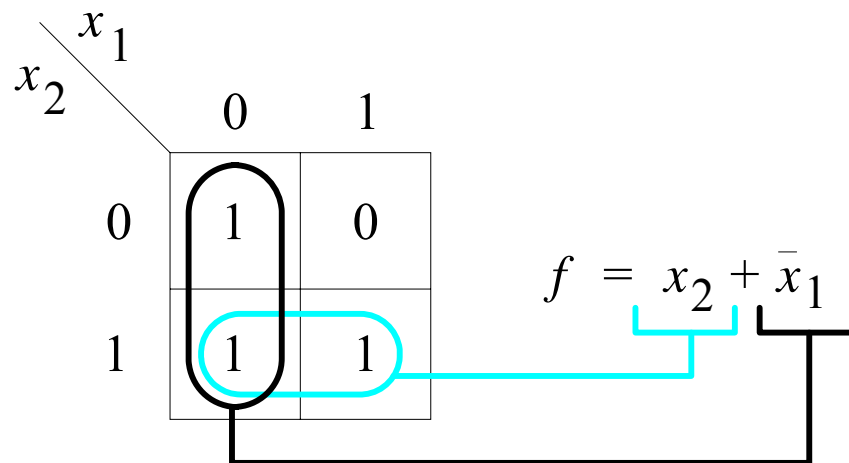


Three-Variable Karnaugh Map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

Three-Variable Example

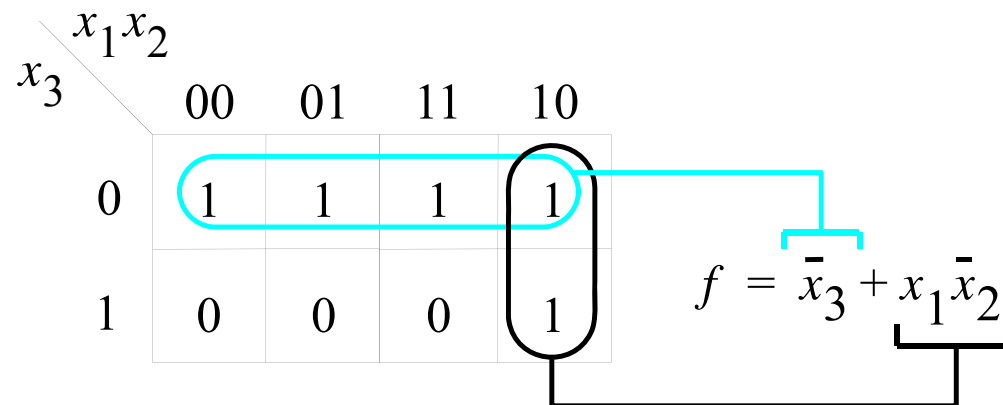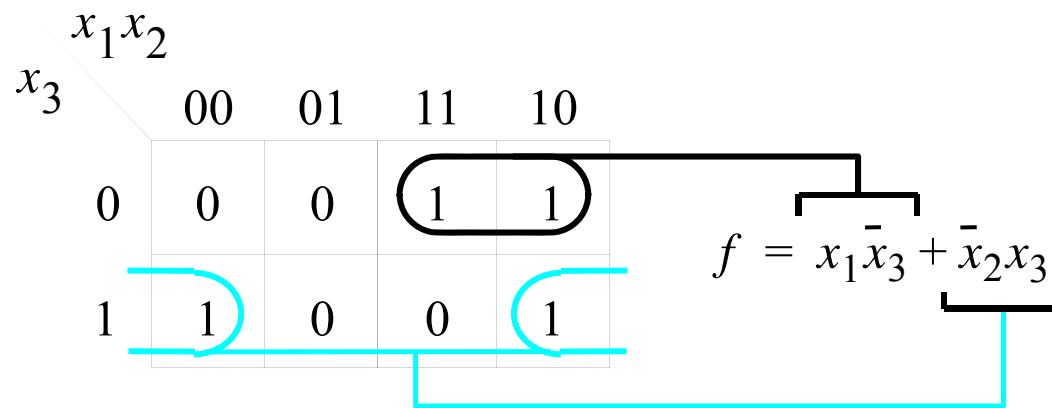






Four Variable Karnaugh Map

A 4x4 Karnaugh Map for four variables x_1, x_2, x_3, x_4 . The map is a grid of 16 cells, each labeled with a minterm m_i . The columns are labeled with x_1x_2 values (00, 01, 11, 10) and the rows with x_3x_4 values (00, 01, 11, 10). Four cyan brackets indicate groupings: x_1 groups the top two columns (11, 10), x_2 groups the bottom two columns (01, 11), x_3 groups the left two rows (00, 01), and x_4 groups the right two rows (11, 10).

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	m_0	m_4	m_{12}	m_8
01	m_1	m_5	m_{13}	m_9
11	m_3	m_7	m_{15}	m_{11}
10	m_2	m_6	m_{14}	m_{10}


Five-Variable Map

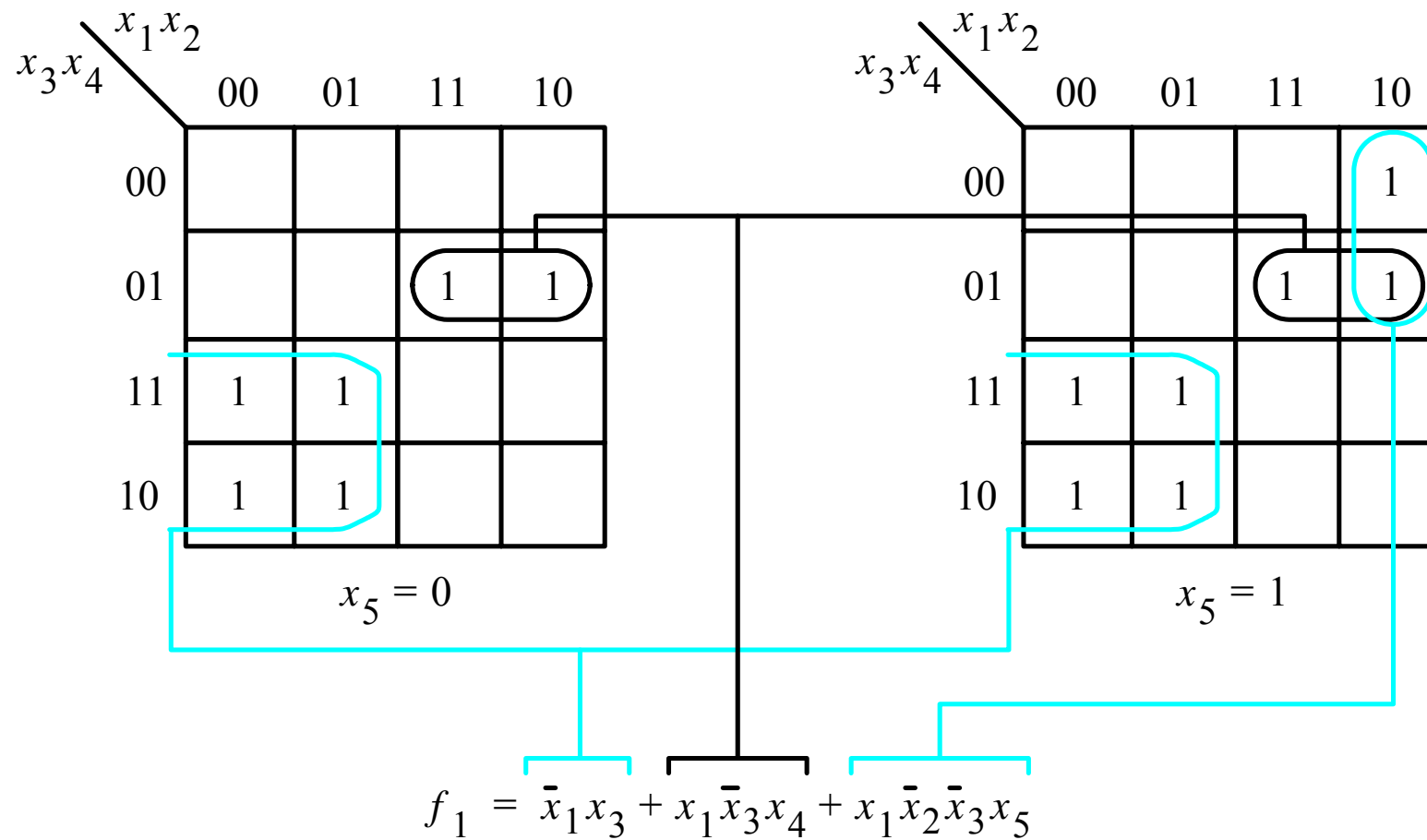

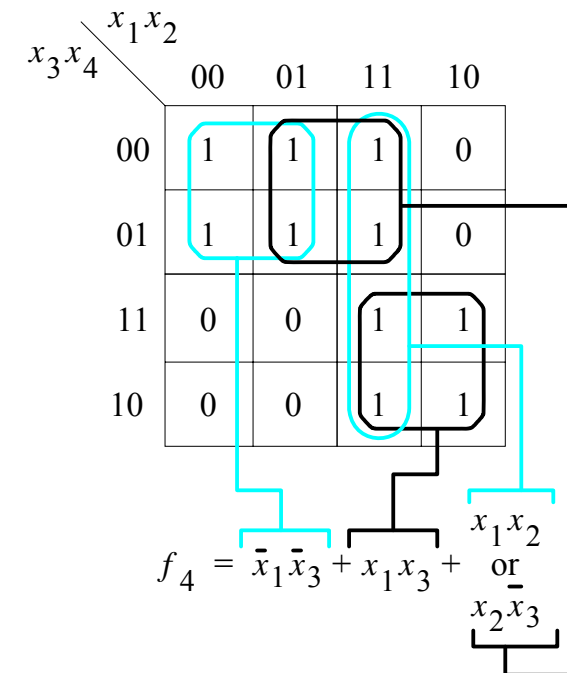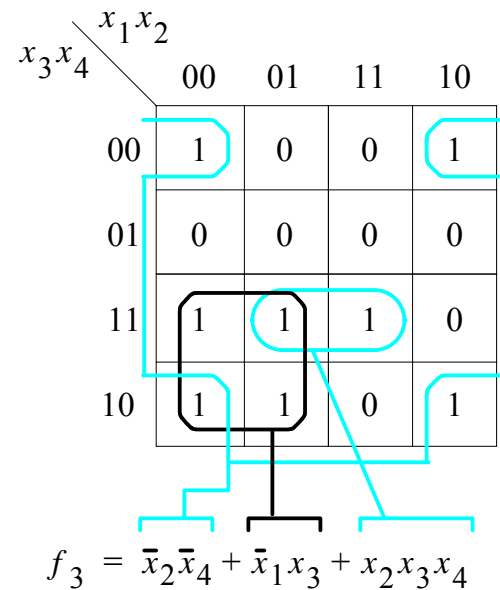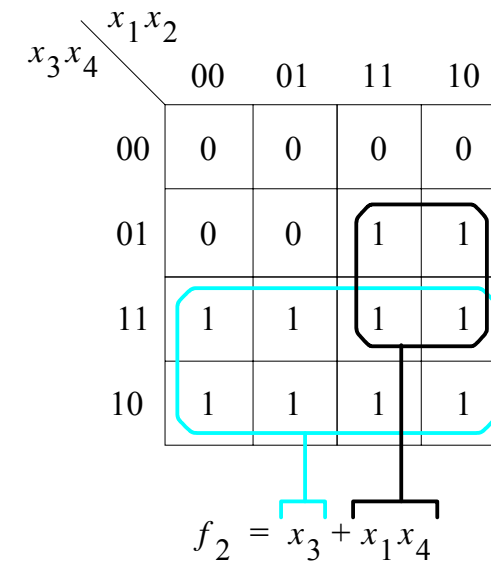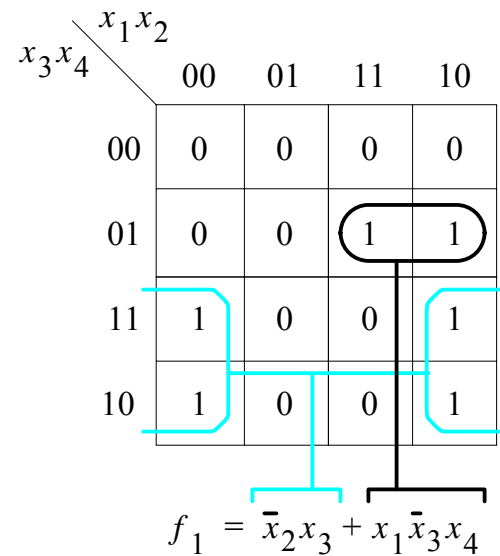

Examples of Four-Variable Map

Prime-Number Detector (again)

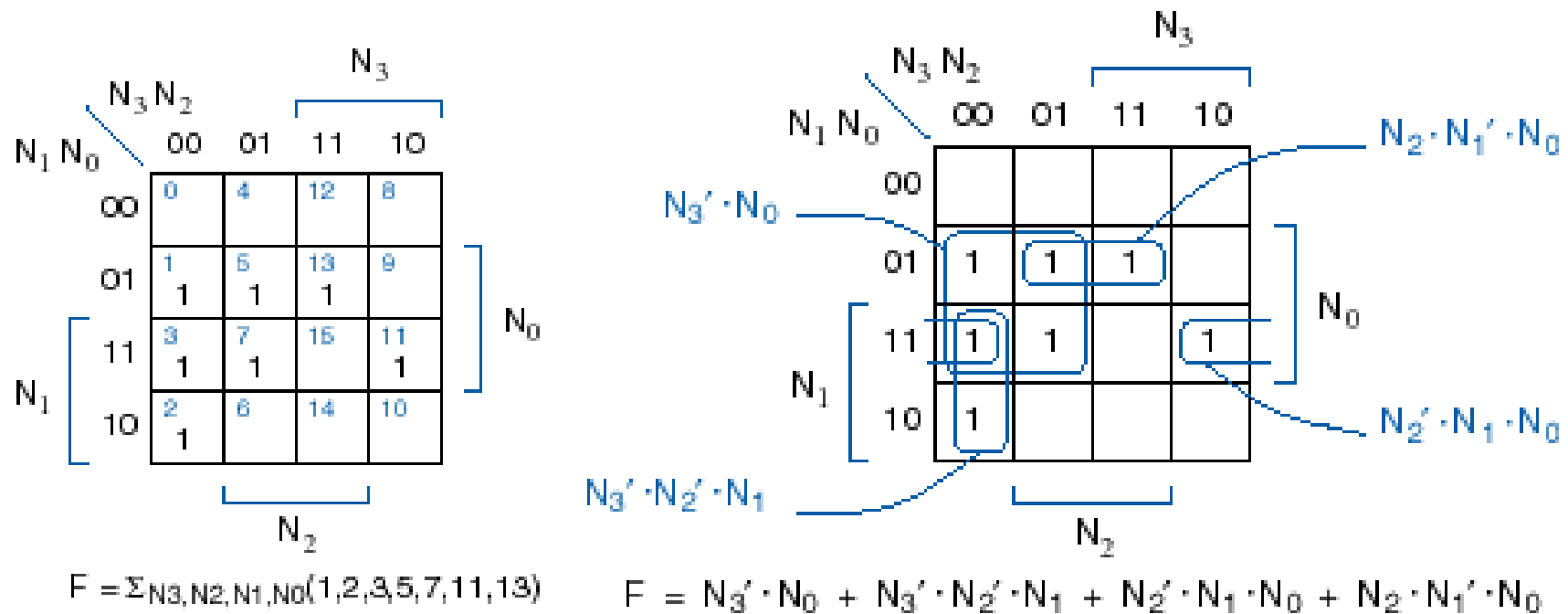


Terminology

- Literal : A given product term consists of some number of variables, each of which may appear either in uncomplemented or complemented form. e.g. $x_1\overline{x_2}x_3$ has three literals
- Implicant: A product term that indicates the input valuations(s) for which is given function is equal to 1 is called an implicant of the function. The most basic implicants are the minterms, and the terms combining pairs of minterms with consensus theorem are also implicants.

Terminology

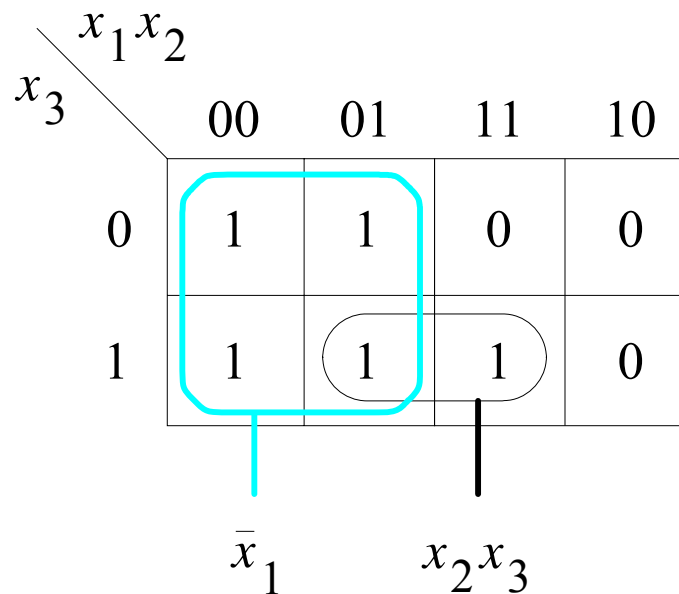- Prime Implicant: An implicant is called a prime implicant if it cannot be combined into another implicant that has fewer literals.



Terminology


- Cover: A collection of implicants that account for which a given function is equal to 1 is called a cover of that function, e.g.
- $f = \overline{x_1 x_2 x_3} + \overline{x_1 x_2 \overline{x_3}} + \overline{x_1 \overline{x_2} x_3} + \overline{x_1 \overline{x_2} \overline{x_3}} + \overline{x_1 x_2 \overline{x_3}}$
- $= \overline{x_1 x_3} + \overline{x_1 \overline{x_3}} + \overline{x_1 \overline{x_2}}$
- $= \overline{x_3} + \overline{x_1 \overline{x_2}}$

Terminology

- Cost: The cost of a logic circuit is the number of gates plus the total number of inputs to all gates in the circuit.
- $f = x_1\overline{x_2} + x_3\overline{x_4}$ has a cost of 9 because it can be implemented using two AND gates and one OR gate with six inputs to the AND and OR gates.
- If an inversion is needed inside a circuit, then the corresponding NOT gate and its input are included in the cost. Ex. $g = \overline{x_1\overline{x_2} + x_3(\overline{x_4} + x_5)}$ has cost of 14.

Essential Prime Implicants


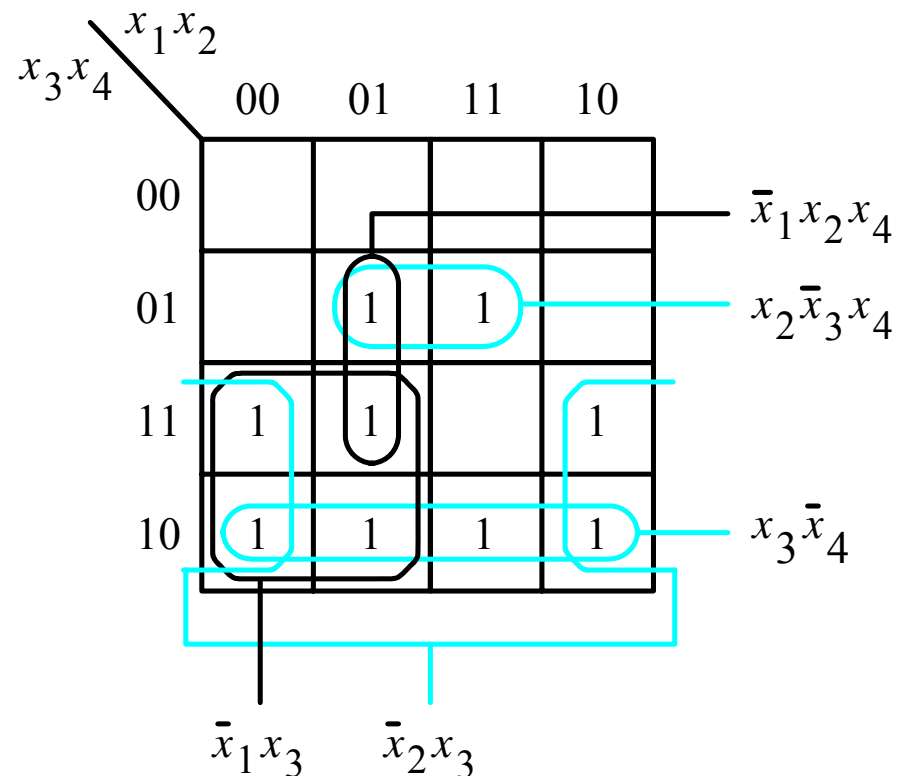
- If a prime implicant includes a minterm for which $f=1$ that is not included in any other prime implicant, then it must be included in the cover and is called an essential prime implicants.




Minimized Procedure for Minimum Cost

- 1. Generate all prime implicants for the given function f .
- 2. Find the set of essential prime implicants.
- 3 If the set of essential prime implicants covers all valuations for which $f=1$, then this set is the desired cover of f . Otherwise, determine the nonessential prime implicants that should be added to form a complete minimum-cost cover.


Examples

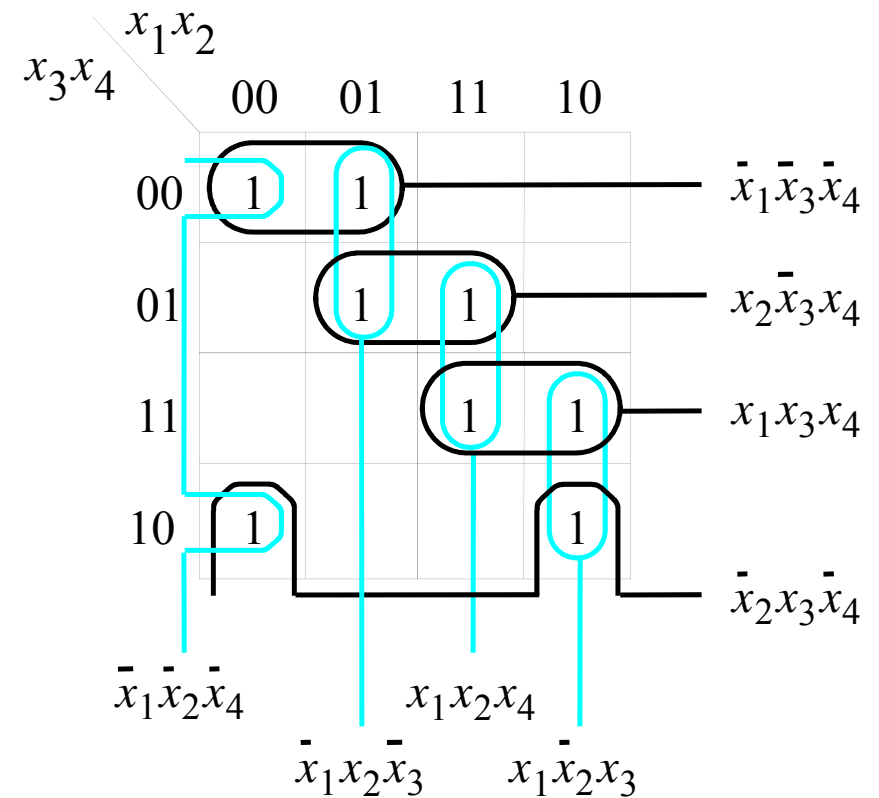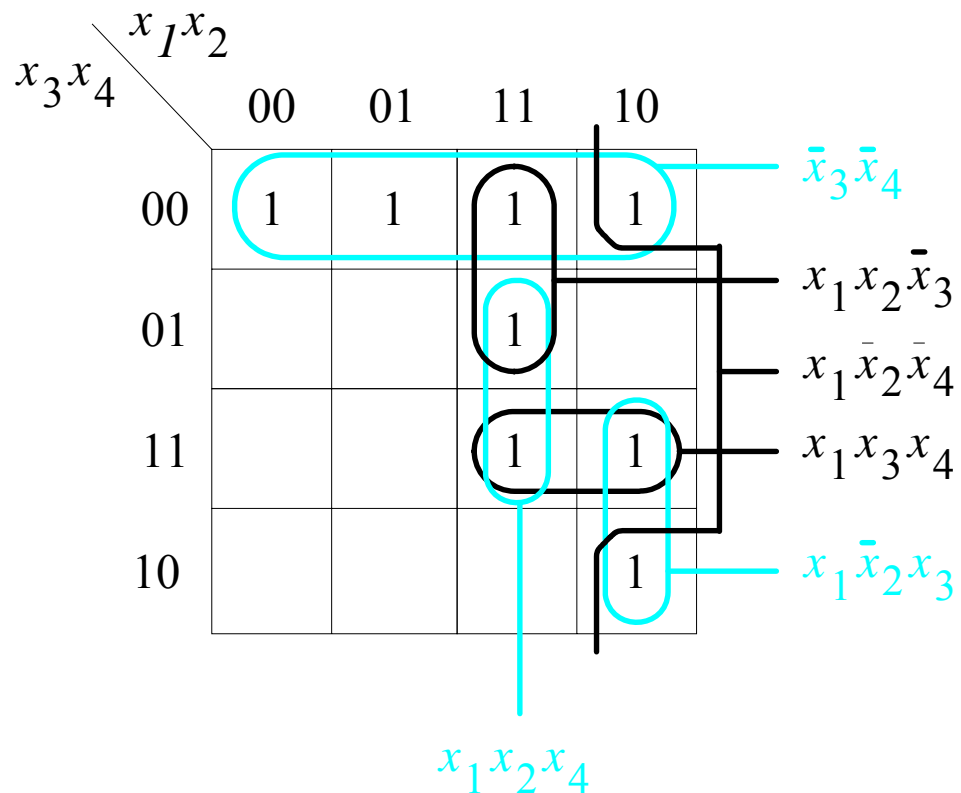

All Prime-Implicants are Essential

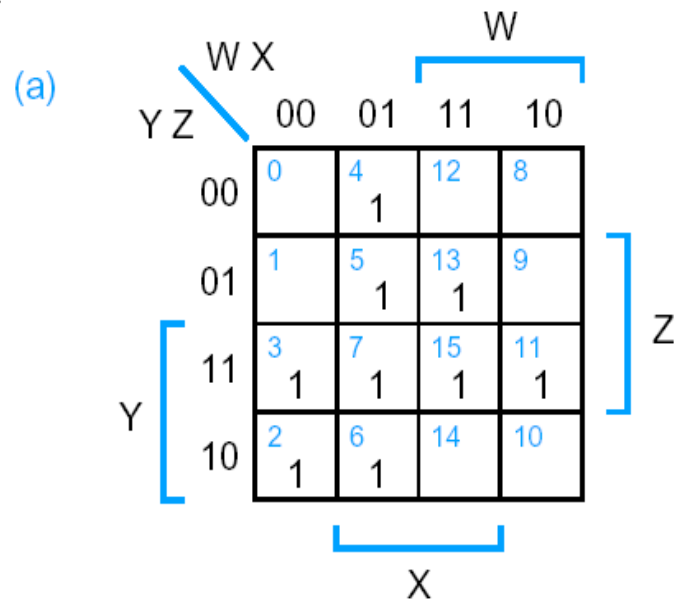

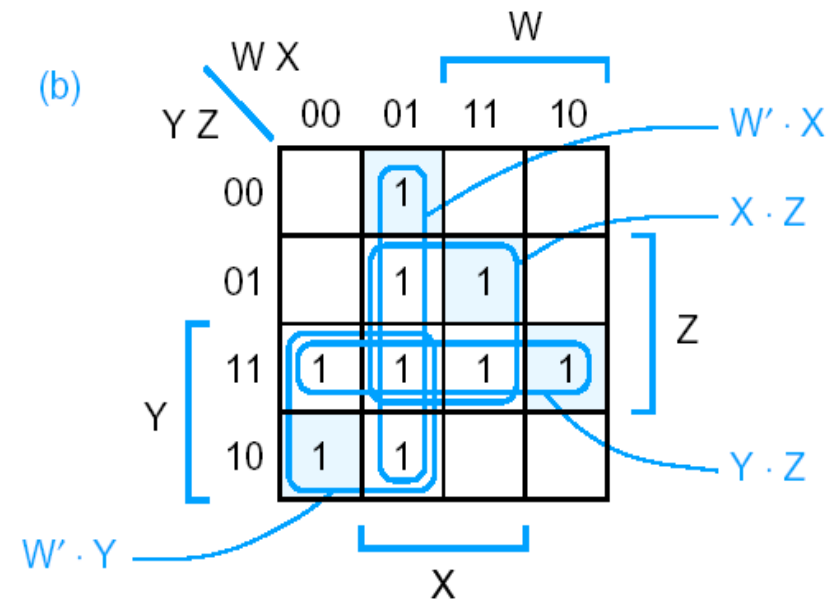
$$F = \sum_{W,X,Y,Z}(2,3,4,5,6,7,11,13,15)$$




$$F = W' \cdot Y + W' \cdot X + X \cdot Z + Y \cdot Z$$

Another Example

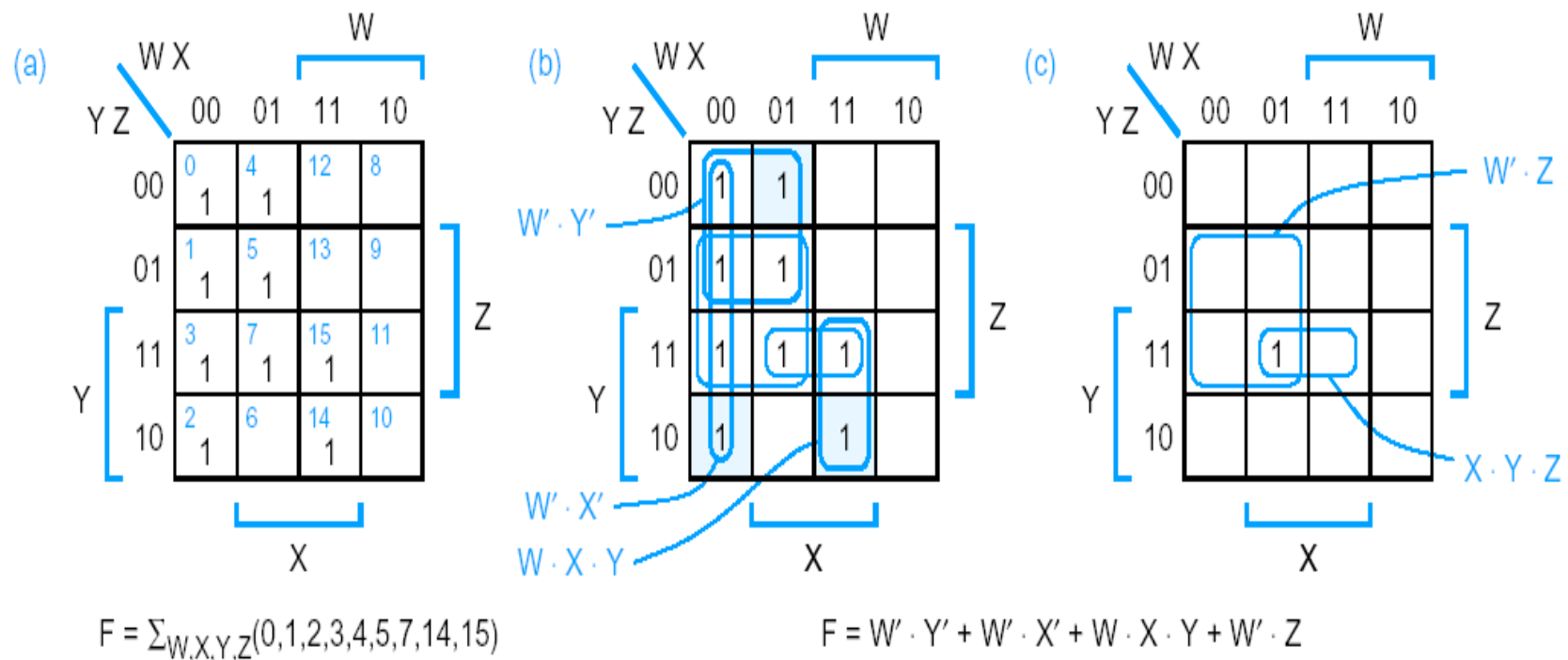

Minimization of Product-of-Sums

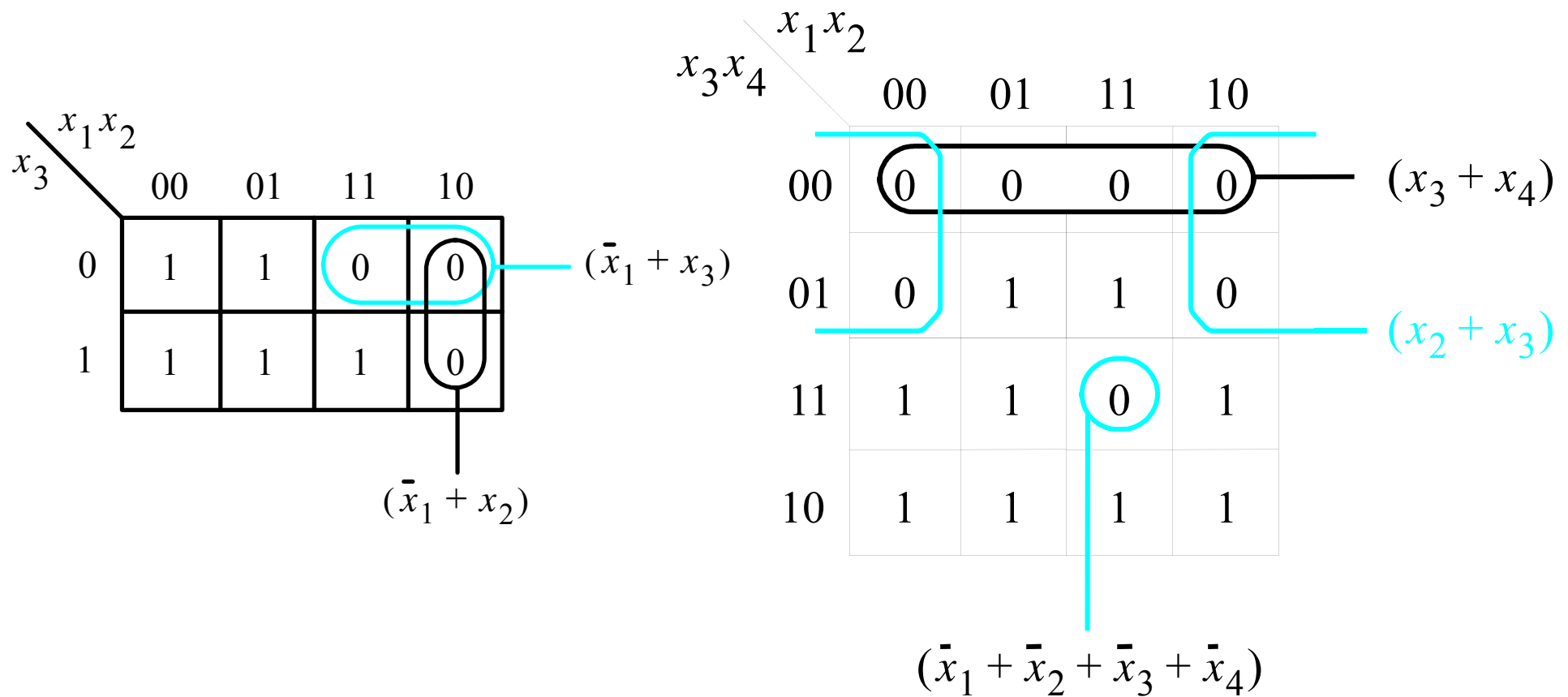

Incomplete Specified Functions

- $f(x_1, \dots, x_4) = \sum m(2,4,5,6,10) + D(12,13,14,15)$

x_1x_2 x_3x_4		00	01	11	10
		00	01	11	10
00	00	0	1	d	0
	01	0	1	d	0
11	11	0	0	d	0
	10	1	1	d	1

$x_2\bar{x}_3$ (points to the 1s in the first two rows, column 01)
 $x_3\bar{x}_4$ (points to the 1s in the last row, columns 00 and 01)

(a) SOP implementation

x_1x_2 x_3x_4		00	01	11	10
		00	01	11	10
00	00	0	1	d	0
	01	0	1	d	0
11	11	0	0	d	0
	10	1	1	d	1

$(x_2 + x_3)$ (points to the 1s in the first two rows, column 01)
 $(\bar{x}_3 + \bar{x}_4)$ (points to the 0s in the first two rows, column 00 and the 0s in the last row, column 10)

(b) POS implementation


Example 4.1 Gate Sharing

$x_3x_4 \backslash x_1x_2$		x_1x_2			
		00	01	11	10
00				1	1
01			1	1	1
11		1	1		
10		1	1		

(a) Function f_1

$x_3x_4 \backslash x_1x_2$		x_1x_2			
		00	01	11	10
00				1	1
01				1	1
11		1	1	1	
10		1	1		

(b) Function f_2

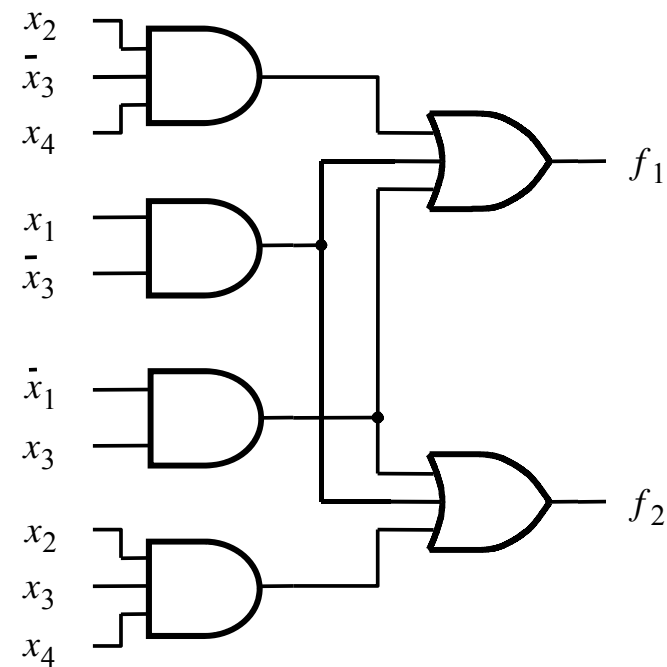

(c) Combined circuit for f_1 and f_2

Example 4.4 Minimized Gate Sharing SOP

$x_3x_4 \backslash x_1x_2$		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01	1	1	1	
	11	1	1	1	
	10		1		

(a) Optimal realization of f_3

$x_3x_4 \backslash x_1x_2$		00	01	11	10
00					
01	1			1	1
11	1			1	1
10		1			

(b) Optimal realization of f_4

$x_3x_4 \backslash x_1x_2$		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01	1	1	1	
	11	1	1	1	
	10		1		

(c) Optimal realization of f_3 and f_4 together

$x_3x_4 \backslash x_1x_2$		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01	1		1	1
	11	1		1	1
	10		1		

Multilevel Synthesis


- A two-level realization is usually efficient for functions of a few variables.
- As the number of inputs increases a two-level circuit may result in fan-in problems (no enough inputs, variables for specific implementations)
- To solve the fan-in problem, f must be expressed in a form that has more than two levels of logic operations.

Factoring

- The distributive law allows


$$\begin{aligned} f &= x_1 \overline{x_6} (x_3 + x_4 x_5) + x_2 x_7 (x_3 + x_4 x_5) \\ &= (x_1 \overline{x_6} + x_2 x_7) (x_3 + x_4 x_5) \end{aligned}$$

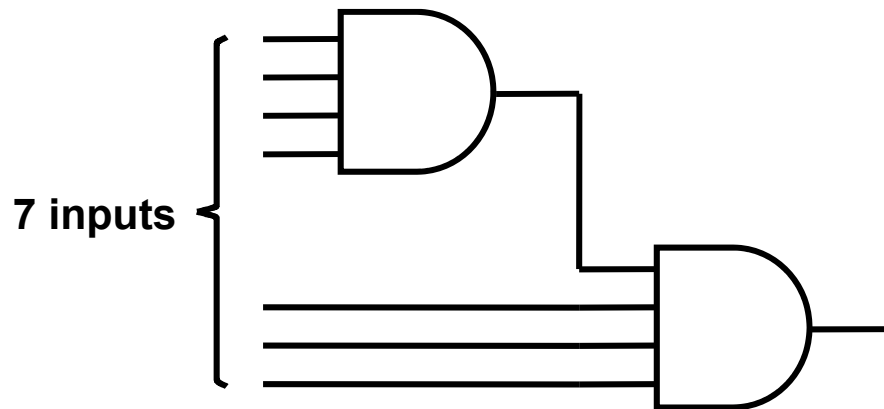- Fan-in problem: e.g. a 7-input product term are re-factoring to 2 four-input AND gates.



A Factored Circuit



- $$f = x_1 \bar{x}_2 x_3 \bar{x}_4 x_5 x_6 + x_1 x_2 \bar{x}_3 x_4 x_5 x_6$$
$$= x_1 \bar{x}_4 x_6 (\bar{x}_2 x_3 x_5 + x_2 \bar{x}_3 x_5)$$

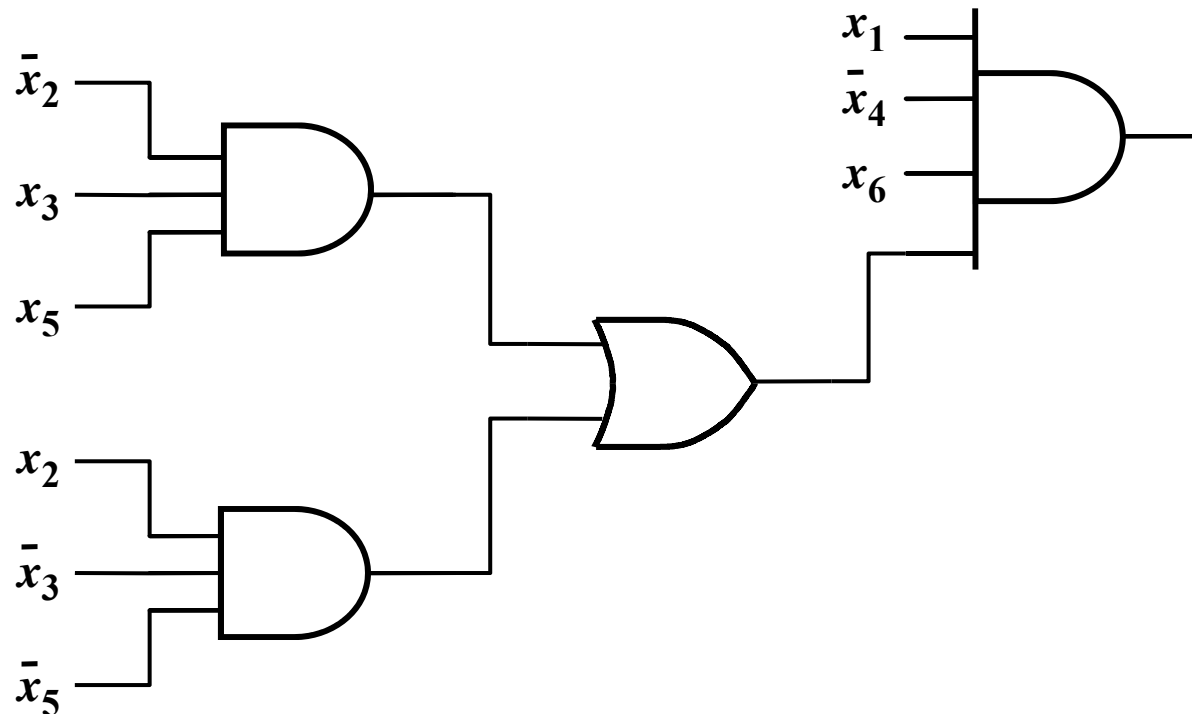

Example 4.6 Function Decomposition

- $f = \overline{x_1}x_2x_3 + x_1\overline{x_2}x_3 + x_1x_2x_4 + \overline{x_1}\overline{x_2}x_4$
 $= (\overline{x_1}x_2 + x_1\overline{x_2})x_3 + (x_1x_2 + \overline{x_1}\overline{x_2})x_4$
- Let $g(x_1, x_2) = \overline{x_1}x_2 + x_1\overline{x_2}$
 $\bar{g} = \overline{\overline{x_1}x_2 + x_1\overline{x_2}}$
 $= \overline{\overline{x_1}x_2} \cdot \overline{x_1\overline{x_2}}$
 $= (\overline{x_1} + x_2)(x_1 + \overline{x_2})$
 $= \overline{x_1}\overline{x_2} + x_1x_2 + \overline{x_1}x_2 + x_1\overline{x_2}$
 $= x_1x_2 + \overline{x_1}\overline{x_2}$
- $f = gx_3 + \bar{g}x_4 = h[g(x_1, x_2), x_3, x_4]$

Example 4.6 Function Decomposition

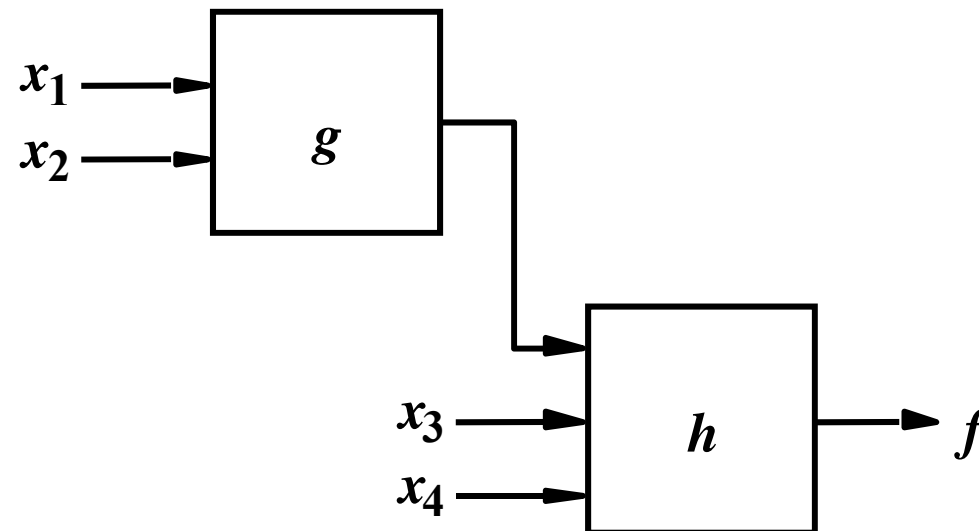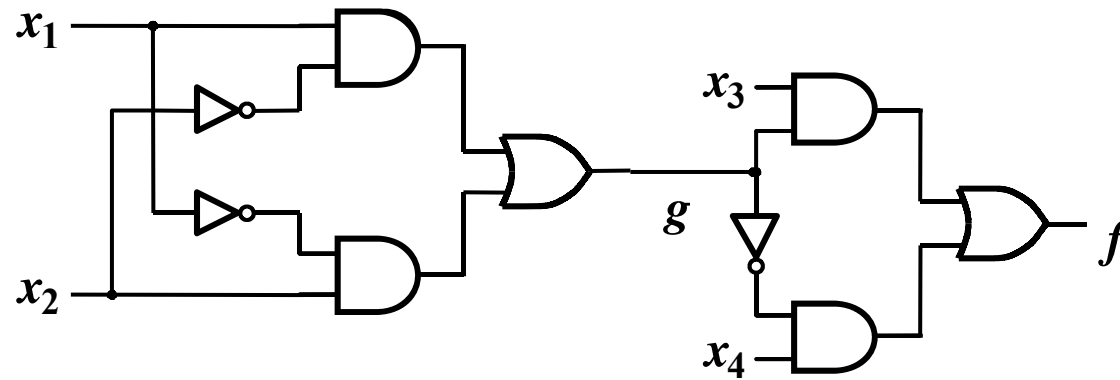

Example 4.7

$x_3x_4 \backslash x_1x_2$					
		00	01	11	10
00	1				
01		1	1	1	
11	1				
10		1	1	1	


$x_3x_4 \backslash x_1x_2$					
		00	01	11	10
00					
01	1	1	1	1	
11					
10	1	1	1	1	

- The patterns, "rows" defines $k = x_3'x_4 + x_3x_4'$
- Within the patterns (blue stripes), "columns" of 1s defines $g = x_1 + x_2 + x_5$ (columns 2,3,4 in $x_5=0$ plane and all columns in $x_5=1$ plane)
- From Ex 4.6 $k' = x_3'x_4' + x_3x_4$

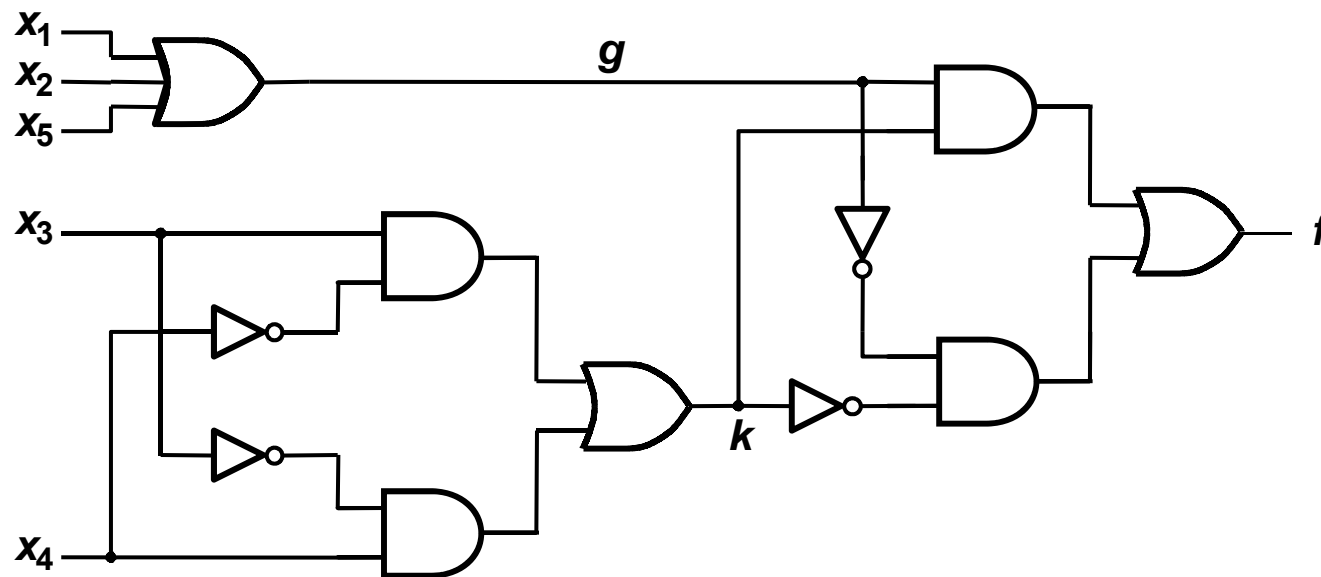
Example 4.7

- Thus decomposition of


$$f = kg \text{ (rows 2,4 \& columns 2,3,4 in } x_5=0 \text{ plane and all columns in } x_5=1 \text{ plane)} \\ + k'g' \text{ (rows 1,3 \& columns 1 in } x_5=0 \text{ plane)}$$



Conversion of NAND Circuit

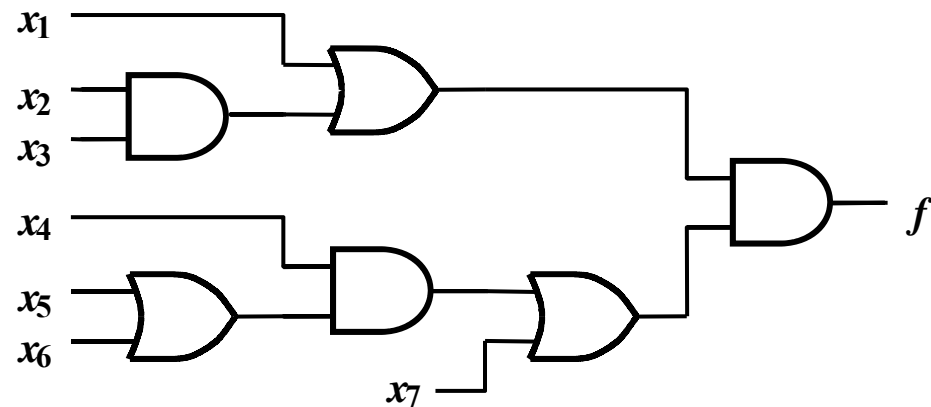


(a) Circuit with AND and OR gates

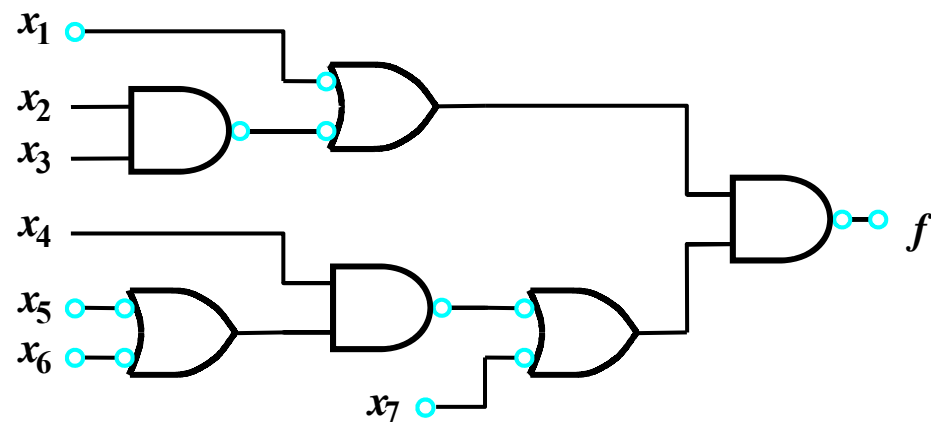

(b) Inversions needed to convert to NANDs



NOR Conversion

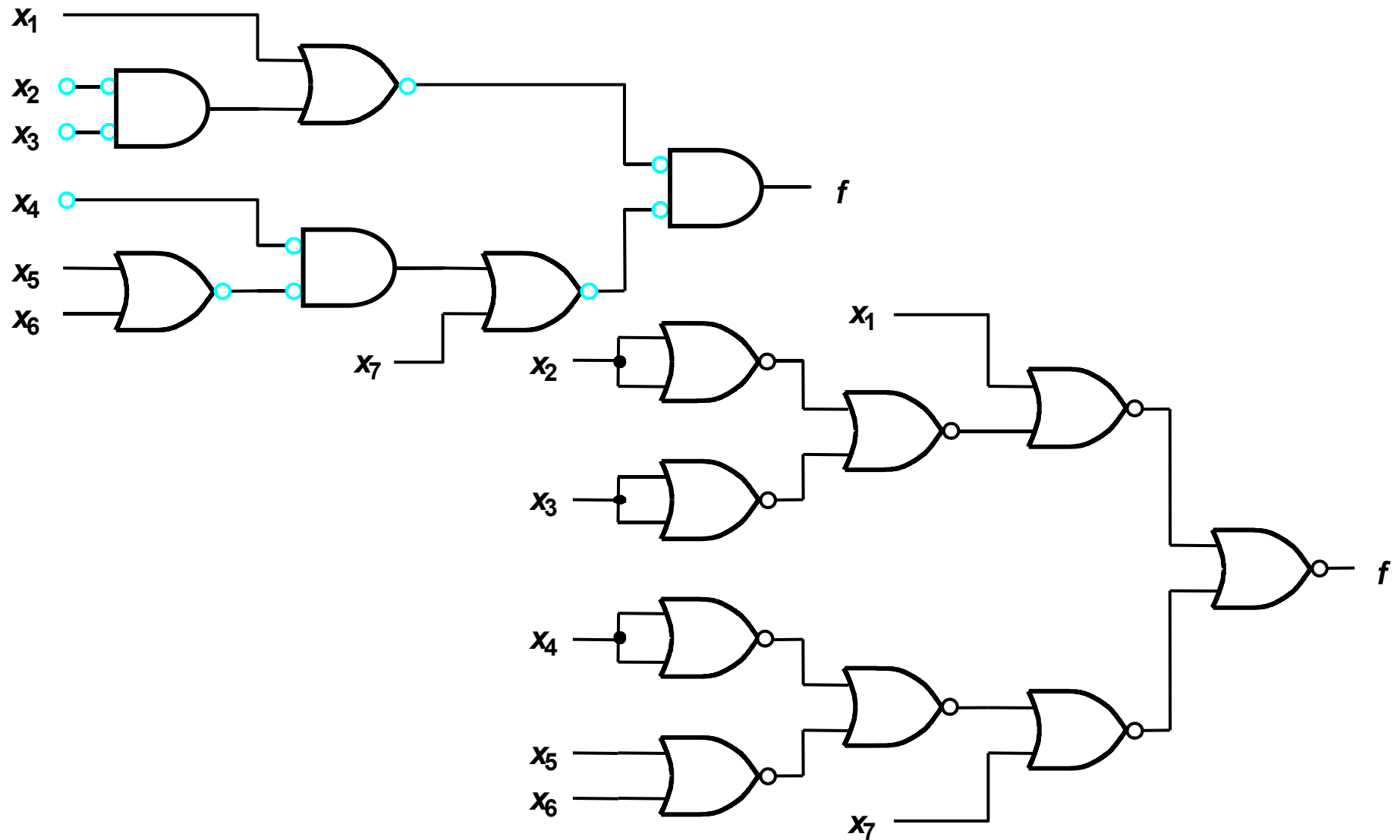

Example 4.10 Multilevel Circuits

- $P_1 = x_2x_3$; $P_2 = x_5 + x_6$; $P_3 = x_1 + P_1$
- $P_4 = x_4P_2 = x_4(x_5 + x_6)$
- $P_5 = P_4 + x_7 = x_4(x_5 + x_6) + x_7$
- $f = P_3P_5 = x_1x_4x_5 + x_1x_4x_6 + x_1x_7 + x_2x_3x_4x_5 + x_2x_3x_4x_6 + x_2x_3x_7$ (cost=6A+10+25i)

