 


Lecture 7

Flip-Flops, Registers, Counters, and a Simple Processor


吳文中

"States" in a Circuit




Control of an alarm system.

Memory Element Implementations

 


A simple memory element.

 

A controlled memory element.


Analog analysis

 - Assume pure CMOS thresholds, 5V rail
- Theoretical threshold center is 2.5 V




Analog analysis

 - Assume pure CMOS thresholds, 5V rail
- Theoretical threshold center is 2.5 V




Analog analysis

 - Assume pure CMOS thresholds, 5V rail
- Theoretical threshold center is 2.5 V



Metastability

 - Metastability is inherent in any bistable circuit




Transfer function:

$$V_{out1} = T(V_{in1})$$




$$V_{out2} = T(V_{in2})$$

- Two stable points, one metastable point


Another look at metastability

 


Stable and Metastable

   


BASIC (RS) Latch

 



A Basic Latch Built with NOR Gates

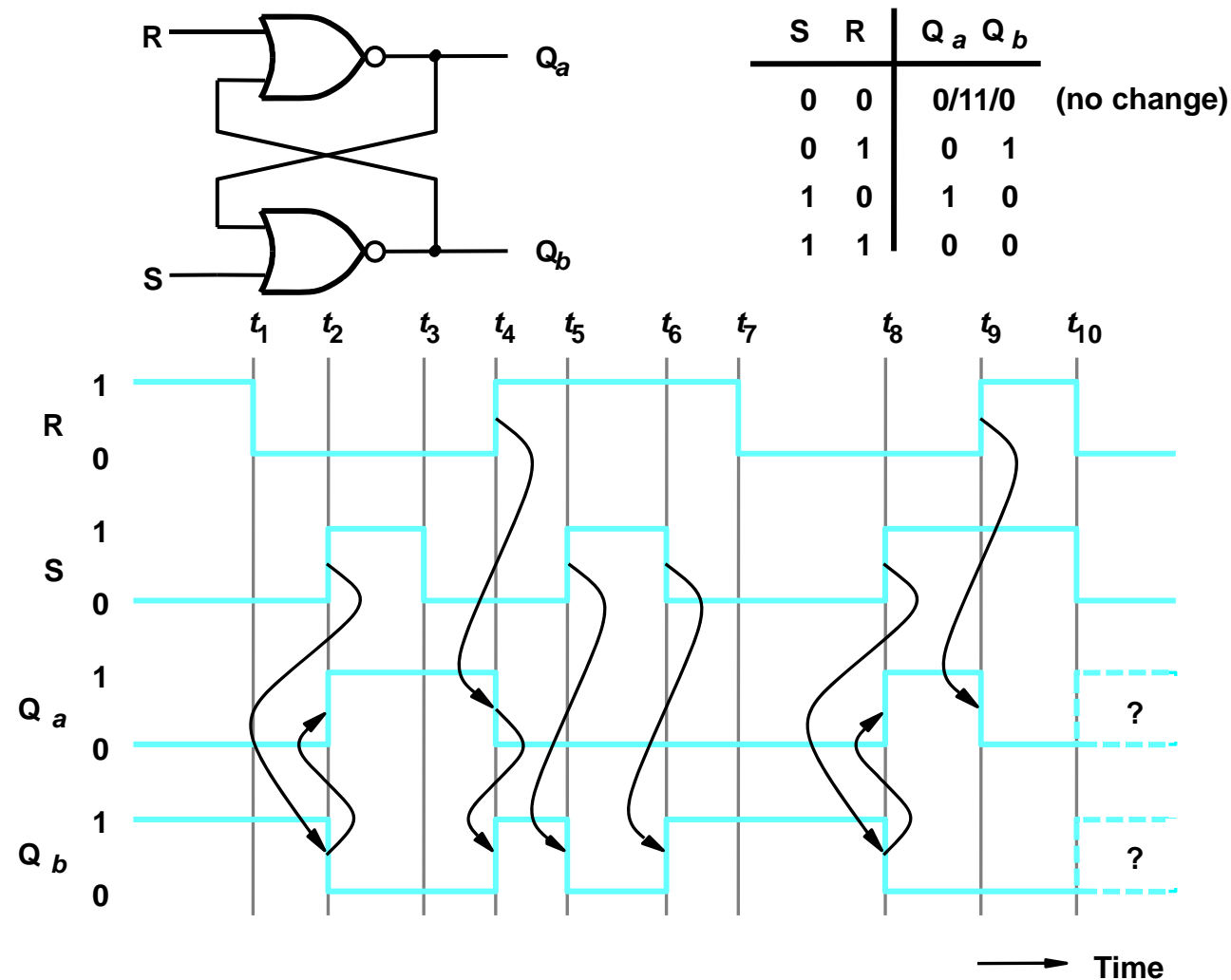


Gates SR Latch

 

Clk	S	R	Q(t+1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	x

  


Gated SR Latch with NAND Gates

 


Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

Gated D Latch

 


Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1


 


Effects of Propagation Delays

 - The minimum time that the D signal must be stable prior to the negative edge of the Clk signal is called setup time, t_{su} .
- The minimum time that the D signal must remain stable after the negative edge of the Clk signal is called hold time, t_h .



Master-Slave D Flip-Flop

  



A Positive-edge-triggered D Flip-Flop

1. Clock=0, P1=P2=1; Latch Hold.

2. P4=D' and P3 = D


3. Clock 0 to 1 (positive edge),
P1=D' and P2=D which
set Q=D and Q'=D'

4. Clock=1, P2=0 when D=0;
P1=0 when D=1

 
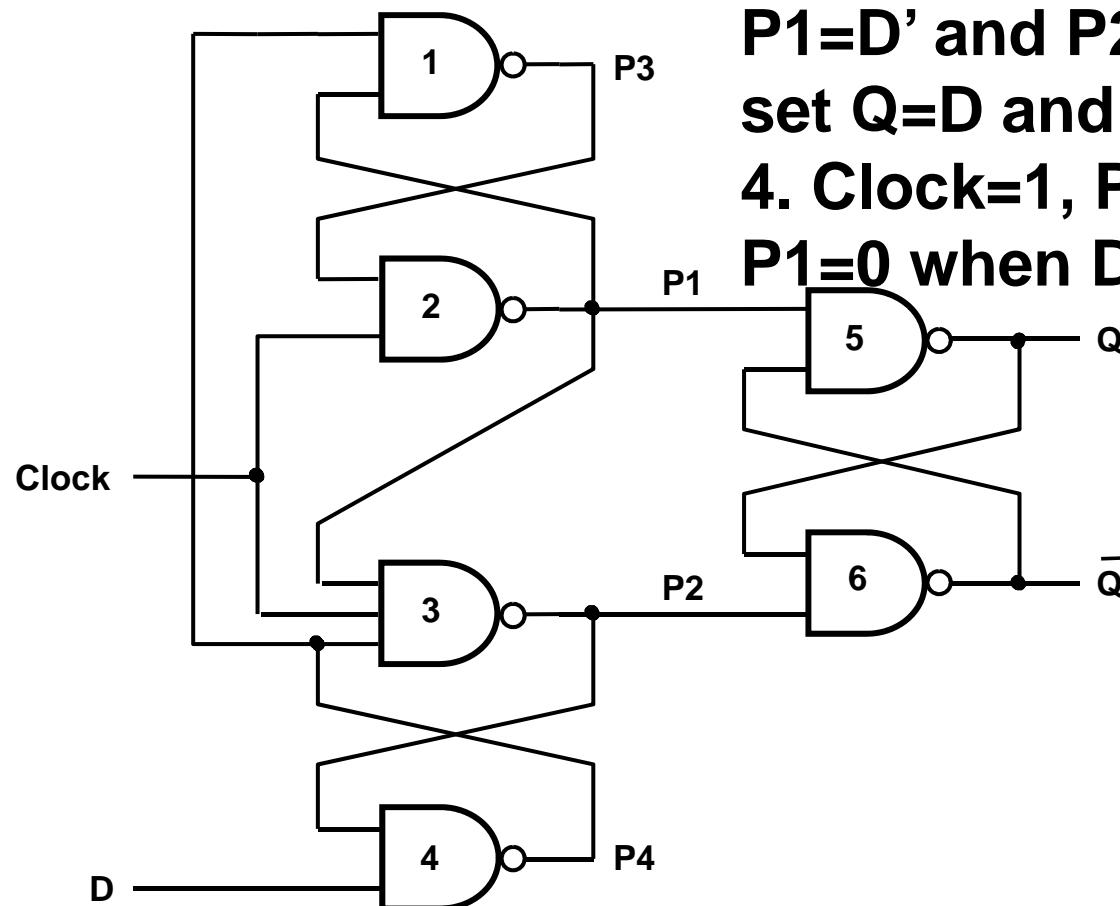


(b) Graphical symbol




Level-Sensitive versus Edge-Triggered

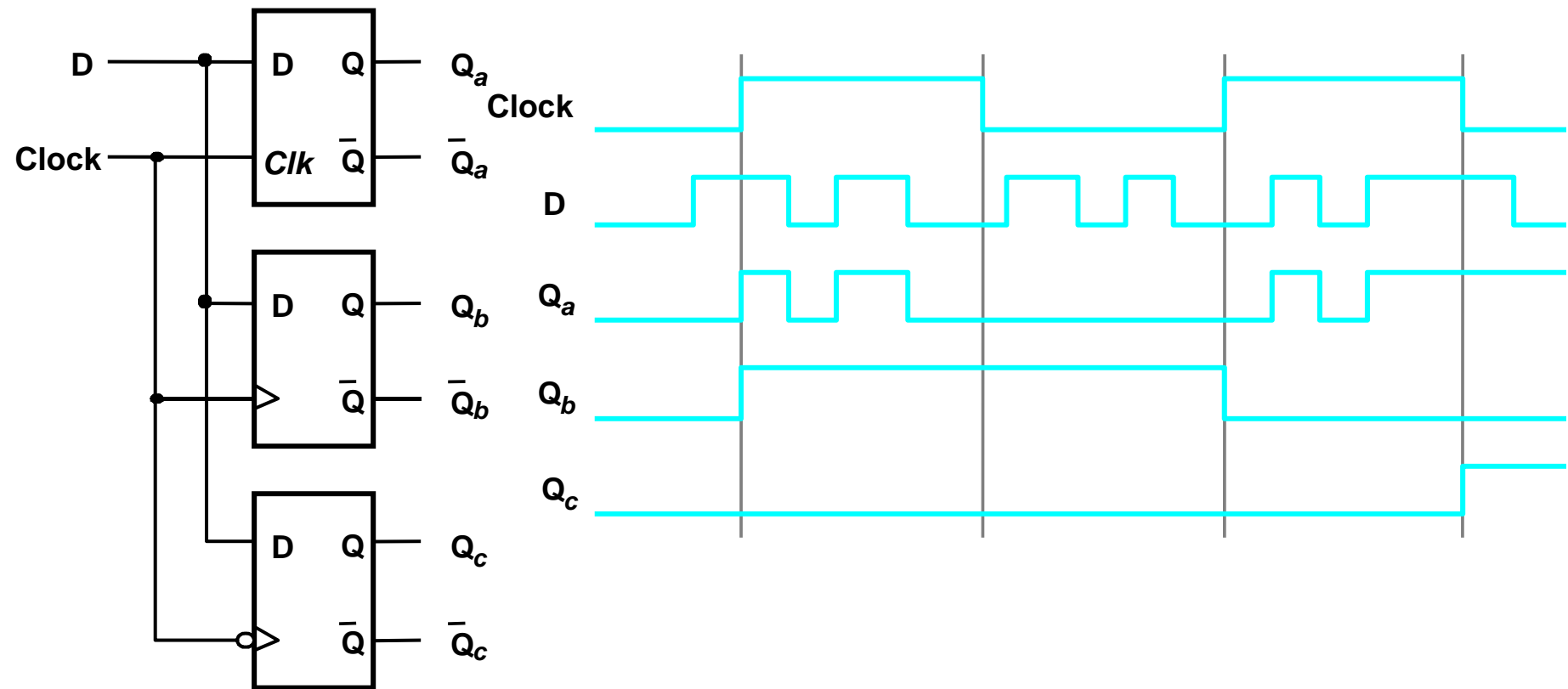

  Master-Slave D Flip-flop with Clear and Preset





  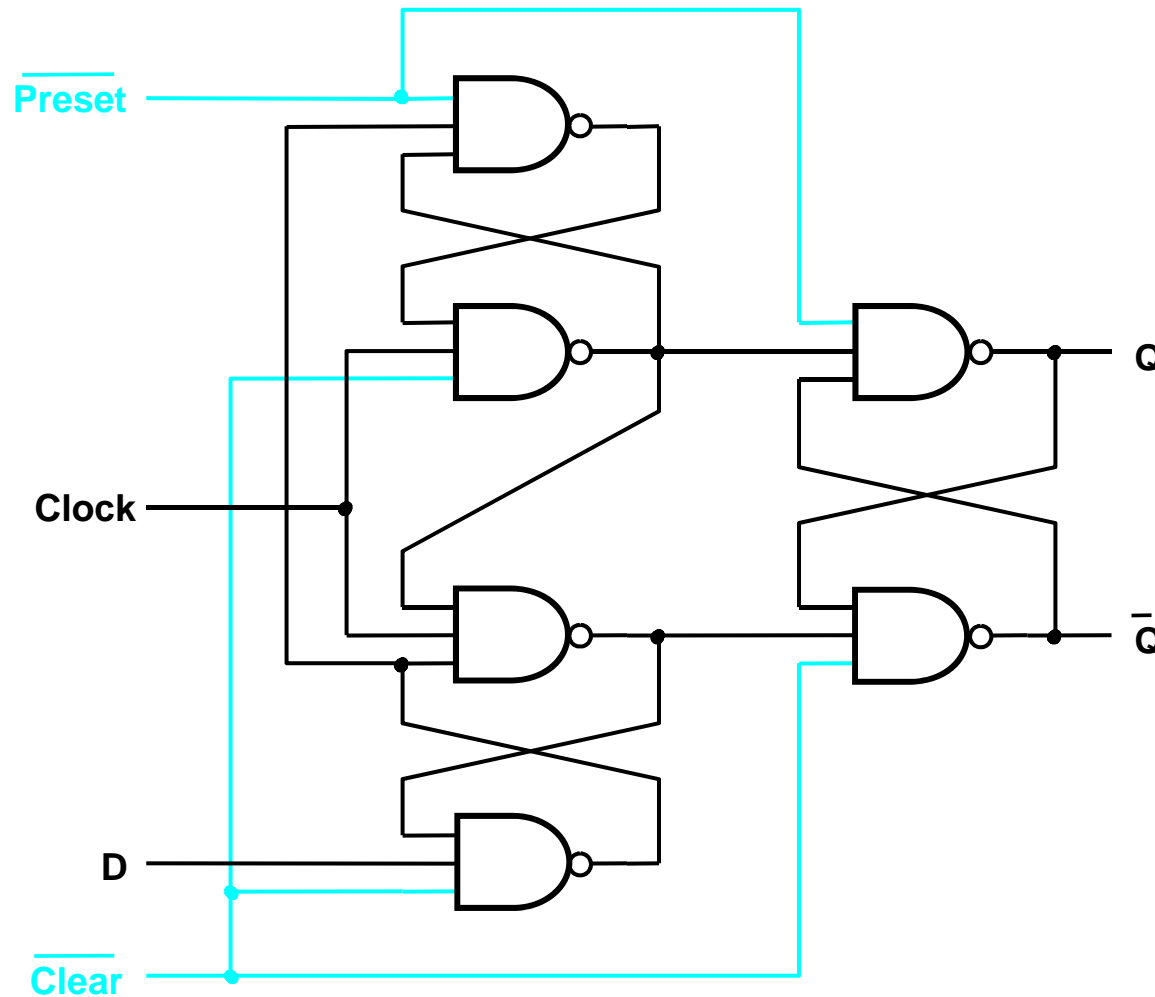Positive-edge-trigger D Flip-flop with Clear and Preset




Adding a synchronous clear



Flip-Flop Timing Parameter

  

T Flip-Flop

 


T	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q}(t)$

  


Configurable Flip-Flops

- In general purpose chips like PLDs, the flip-flops that are provided are sometimes *configurable*, which means that a flip-flop circuit can be configured to be either D, T, or some type.
- HOW?

JK Flip-Flop

 

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

 

Summary of Terminology


- **Basic latch** is a feedback connection of two NOR gates or two NAND gates, which can store one bit of information. It can be set to 1 using S or 0 using R.
- **Gated latch** is a basic latch that includes input gating and a control input signal.
 - **Gated SR latch** uses the S and R inputs to set the latch to 1 or reset to 0 (do have $R=S=0$ exception).
 - **Gated D latch** uses the D input to force the latch into a state that has the same logic value as the D input

- A **flip-flop** is a storage element based on the gated latch principle, which can have its output state changed only on the edge of the controlling clock signals.
 - **Edge-triggered flip-flop** is affected only by the input values present when the active edge of the clock occurs.
 - **Master-slave flip-flop** is built with two gated latches. The master stage is active during half of the clock cycle, and the slave stage is active during the other half. The output value of the flip-flop changes on the edge of the clock that activates the transfer into the slave stage. It can be edge-triggered or level sensitive. (Gated D latch=>edge-triggered; Gated SR latch=> level-sensitive)

Registers

- A flip-flop stores one bit of information.
- When a **set** of n flip-flops is used to store n bits of information, such as an n -bit number, we refer to these flip-flops as a *register*.
- A common clock is used for each flip-flop in a register.

Shift Register

 


	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1


Parallel versus Serial

- Transmitting n bits at once using n separate wires. We say this scheme is **parallel transfer**.
- Transmitting n bits at once using a single wire, by performing the transfer one bit at a time, in n consecutive clock cycles. We say this scheme is **serial transfer**.


Parallel-Access Shift Register

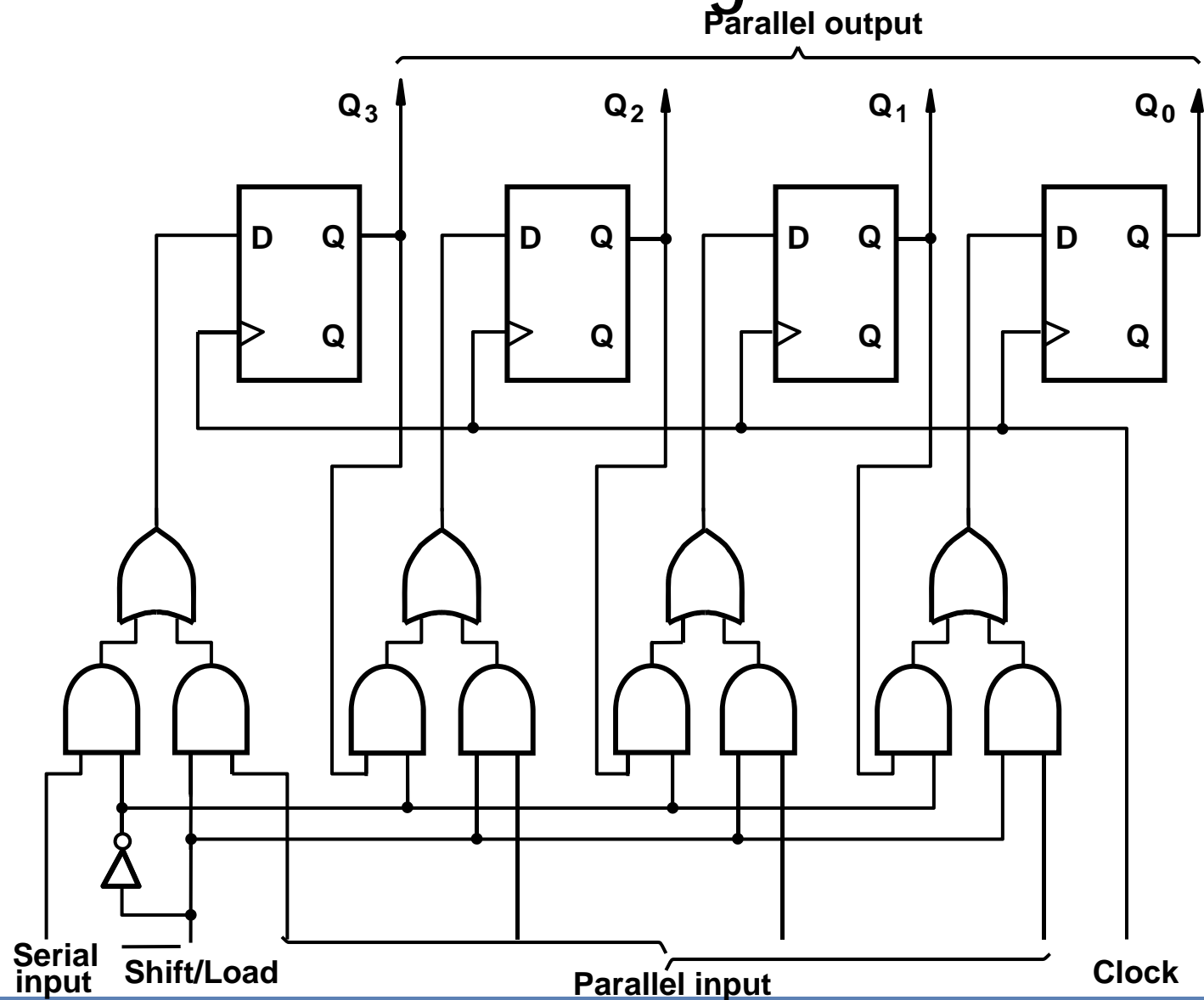

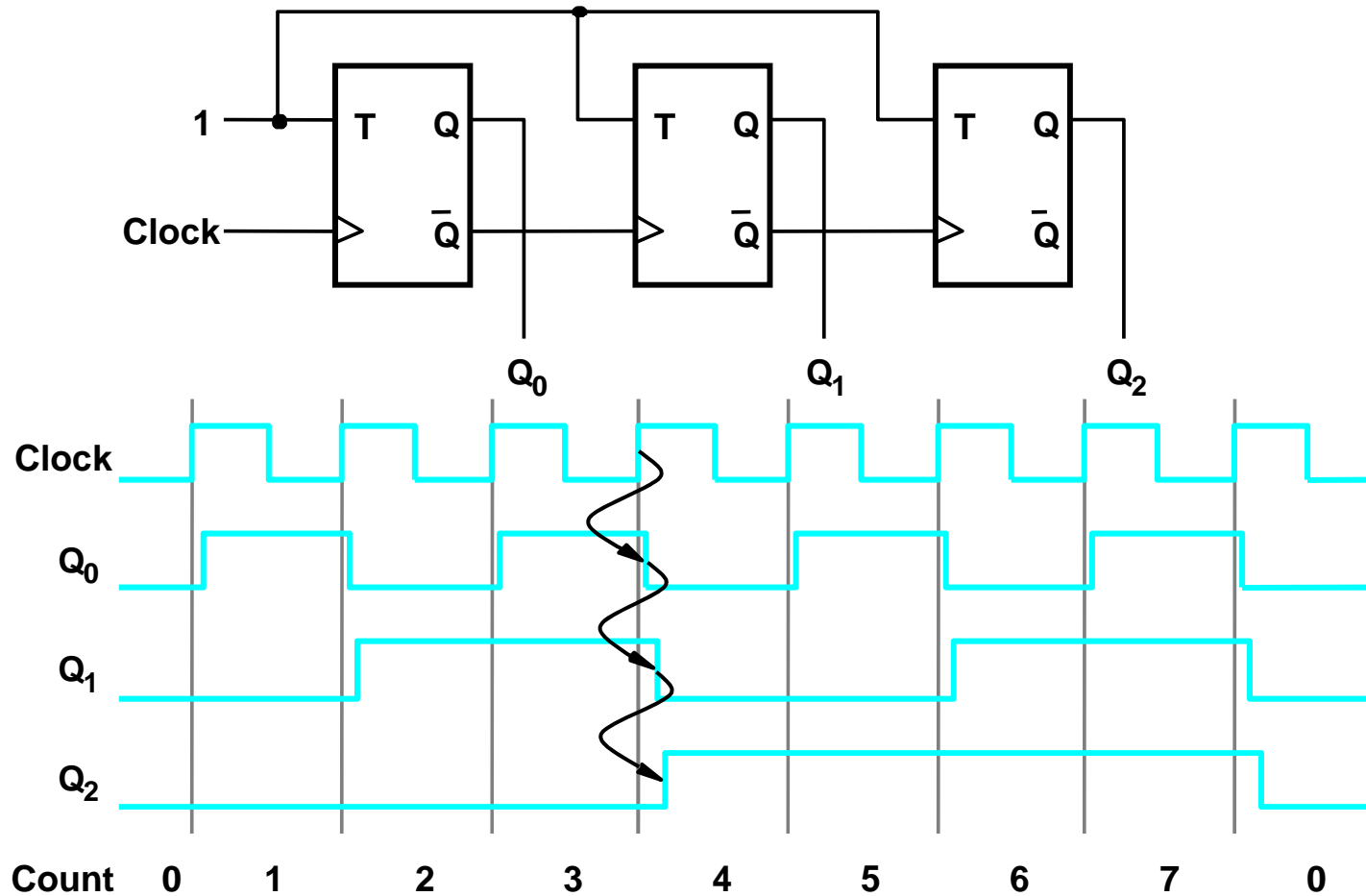Asynchronous Up-Counter with T Flip-flops



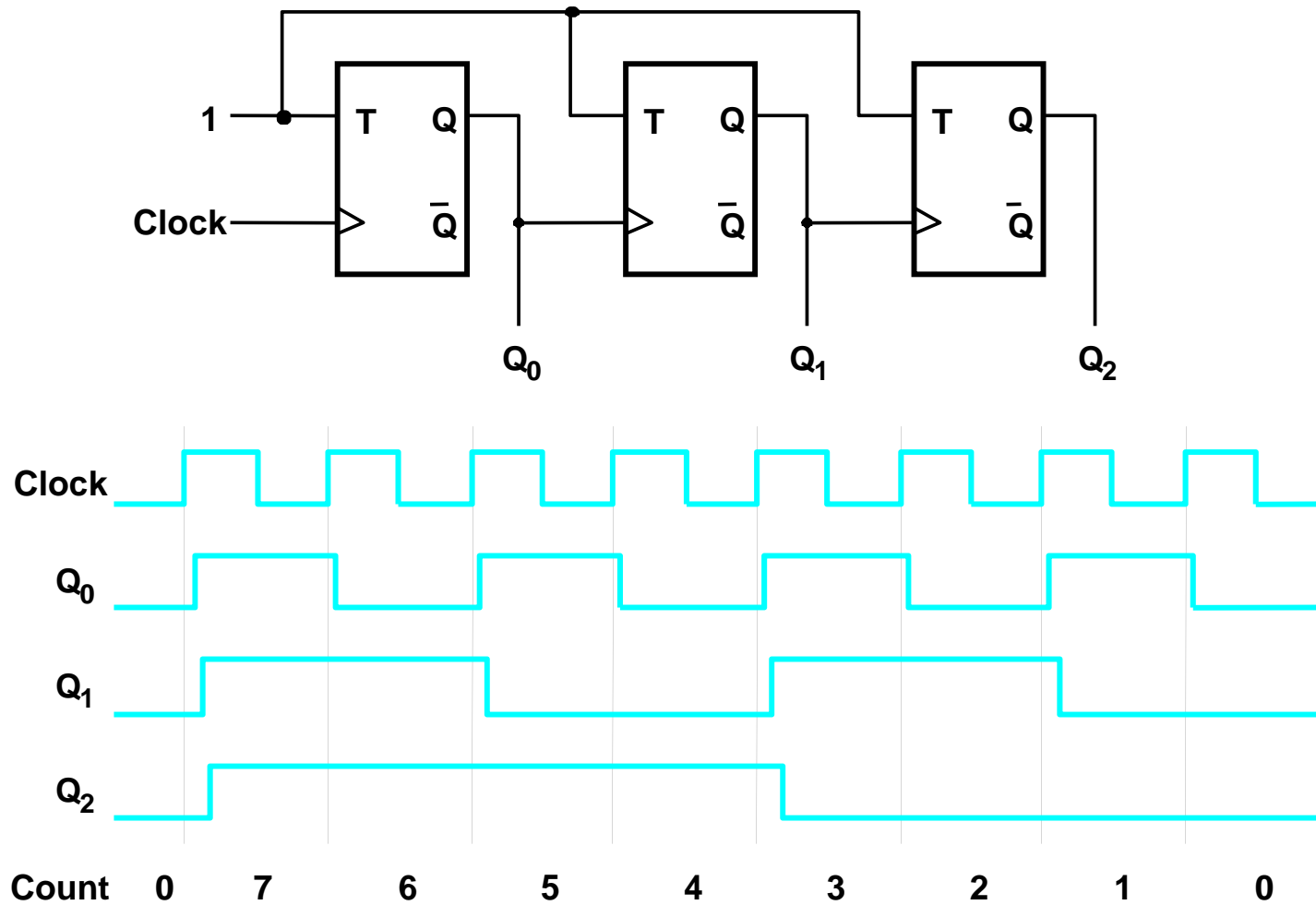Asynchronous Down-Counter with T Flip-flops



Synchronous Counter with T Flip-flops



- $T_0 = 1$
- $T_1 = Q_0$
- $T_2 = Q_0 Q_1$
- $T_3 = Q_0 Q_1 Q_2$
- $T_n = Q_0 Q_1 \dots Q_{n-1}$

Clock cycle	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0


Q₁ changes

Q₂ changes

Synchronous Counter with T Flip-flops

  

Enable and Clear

 


Synchronous Counter with D Flip-flops

- $D_0 = \overline{Q_0} = 1 \oplus Q_0 (= Q_0 \oplus Enable)$
- $D_1 = Q_1 \oplus Q_0 (\cdot Enable)$
- $D_2 = Q_2 \oplus Q_1 Q_0 (\cdot Enable)$
- $D_3 = Q_3 \oplus Q_2 Q_1 Q_0 (\cdot Enable)$
- $D_i = Q_i \oplus Q_{i-1} Q_{i-2} \dots Q_1 Q_0 (\cdot Enable)$


- $$D = Q\bar{T} + \bar{Q}T$$

$$= Q \oplus T$$

Synchronous Counter with D Flip-flops

 


Counter with Parallel-load

 


A Modulo-6 Counter with Synchronous Reset

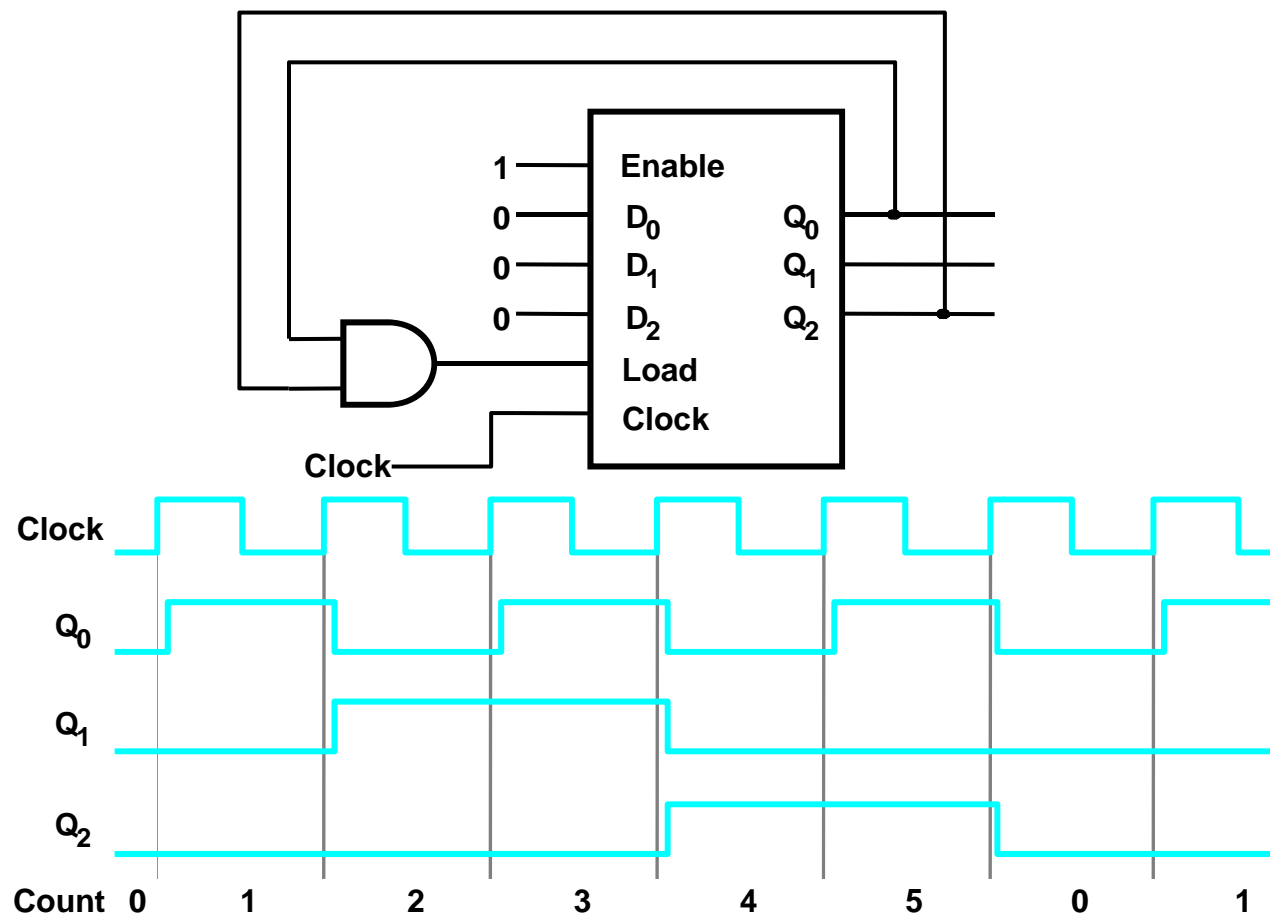- Counting sequence: 0,1,2,3,4,5,0,1, and so on.




A Modulo-6 Counter with Asynchronous Reset


- Modulo 5 or 6?

 


BCD Counter

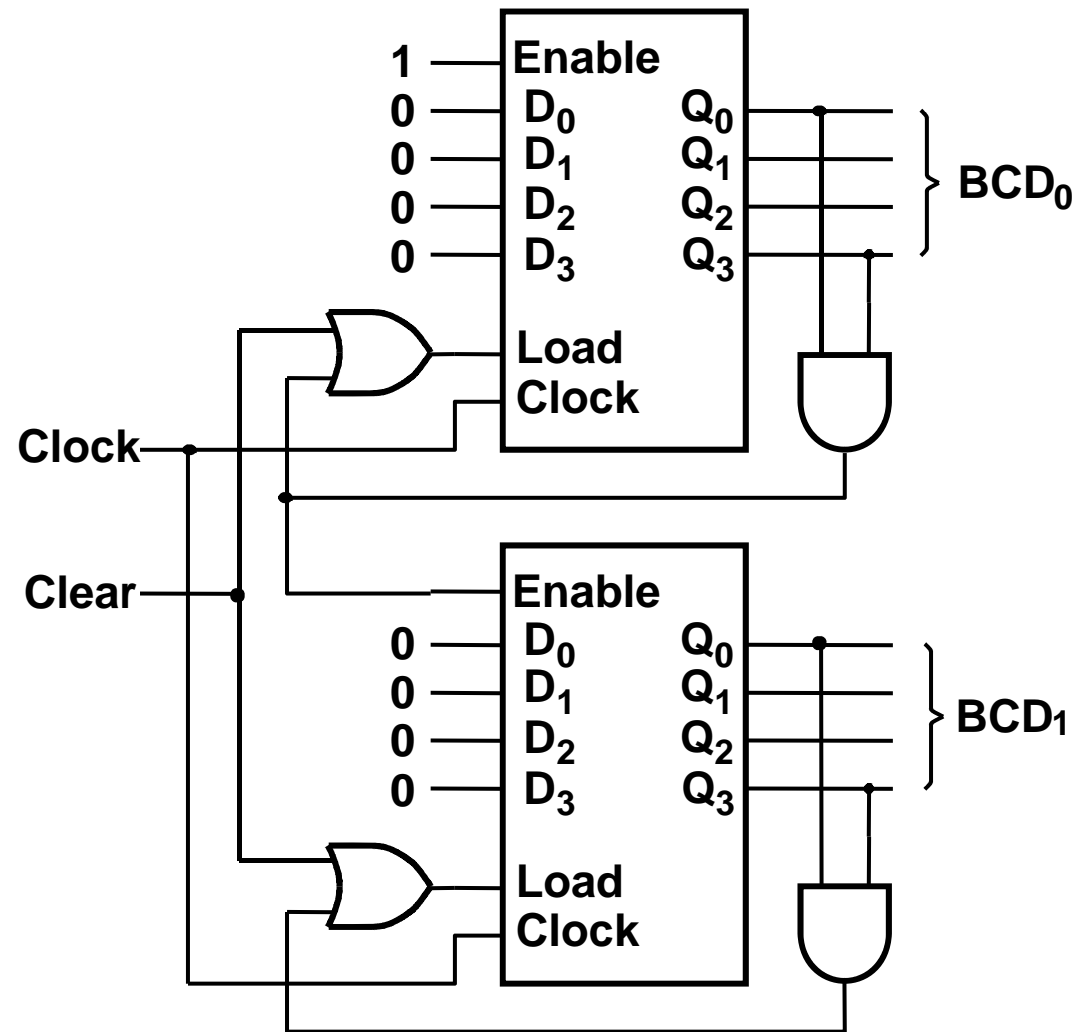


Ring Counter

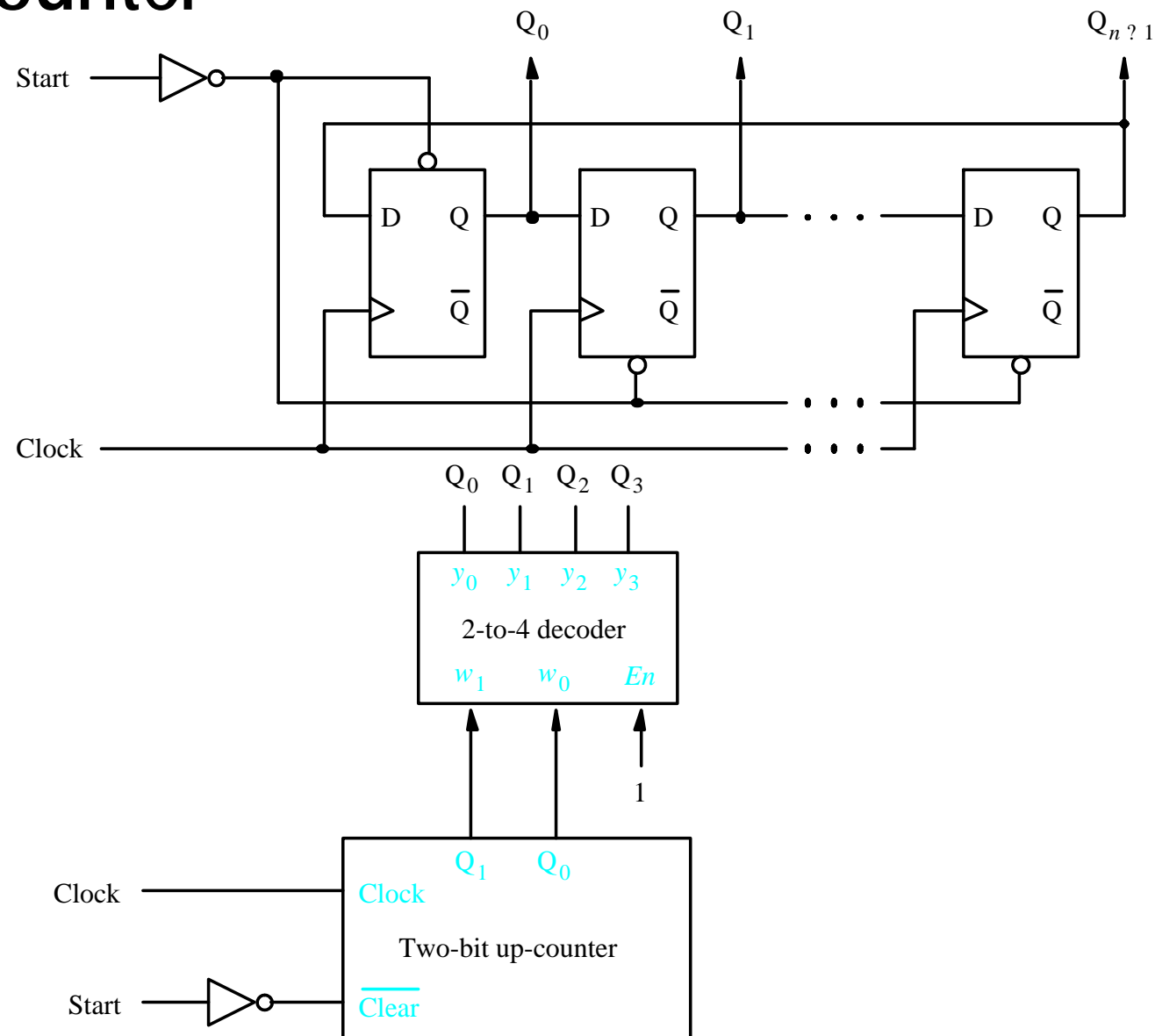


Johnson Counter

 

Design Example: Bus Structure

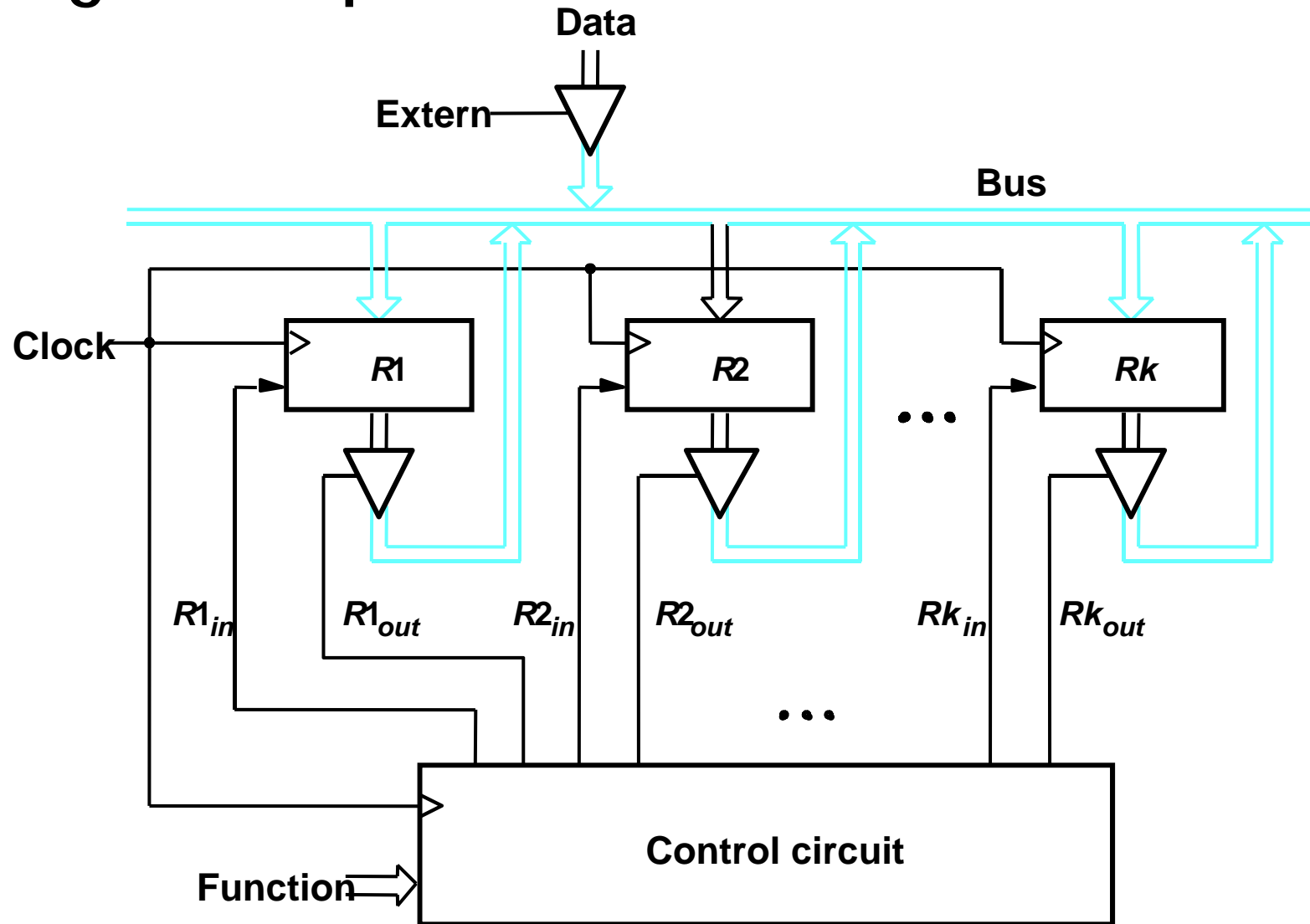


Simple Processor

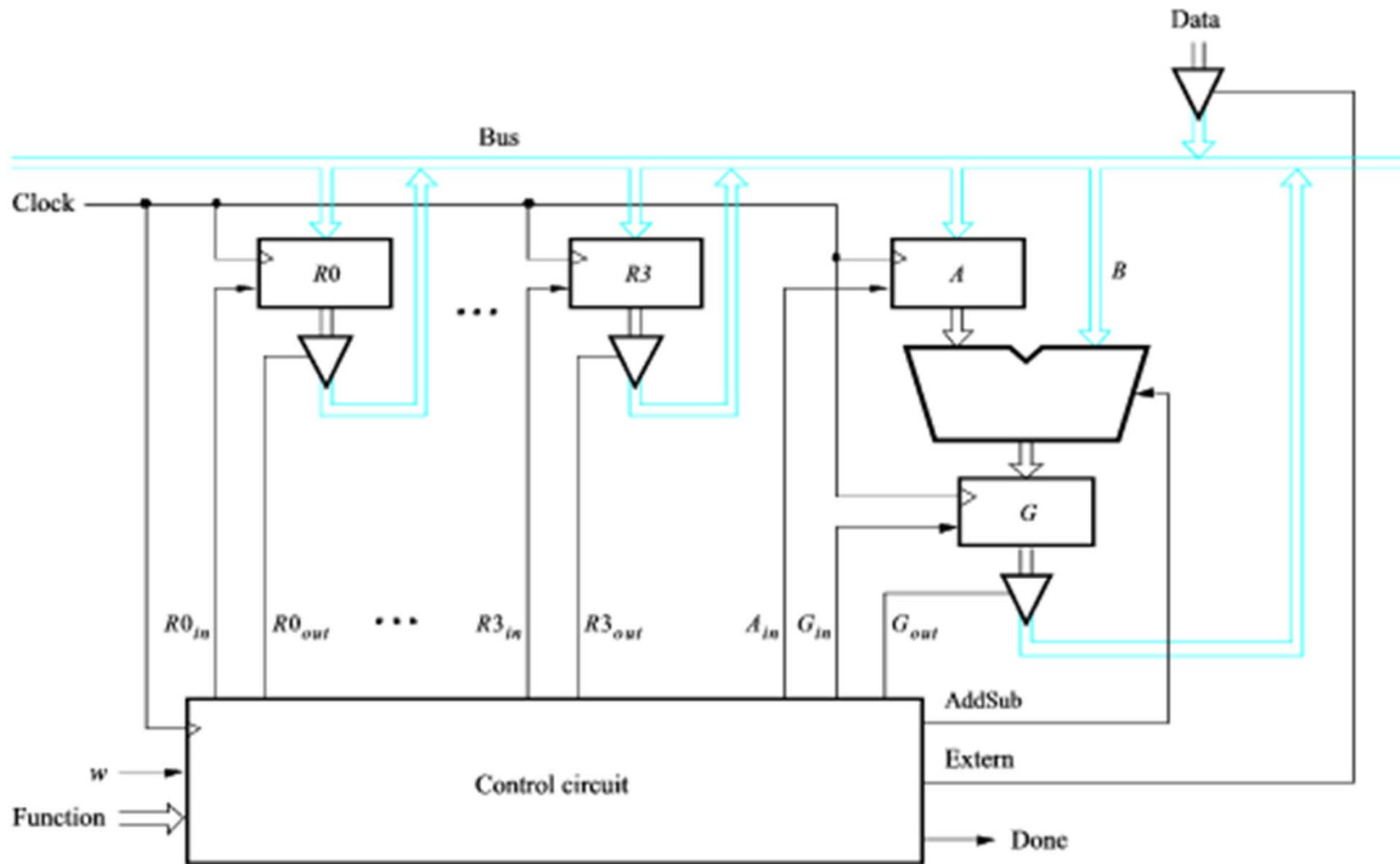

Operation Performed in the Processor


Operation	Function performed
Load $Rx, Data$	$Rx \leftarrow Data$
Move Rx, Ry	$Rx \leftarrow [Ry]$
Add Rx, Ry	$Rx \leftarrow [Rx] + [Ry]$
Sub Rx, Ry	$Rx \leftarrow [Rx] - [Ry]$

Control Circuit

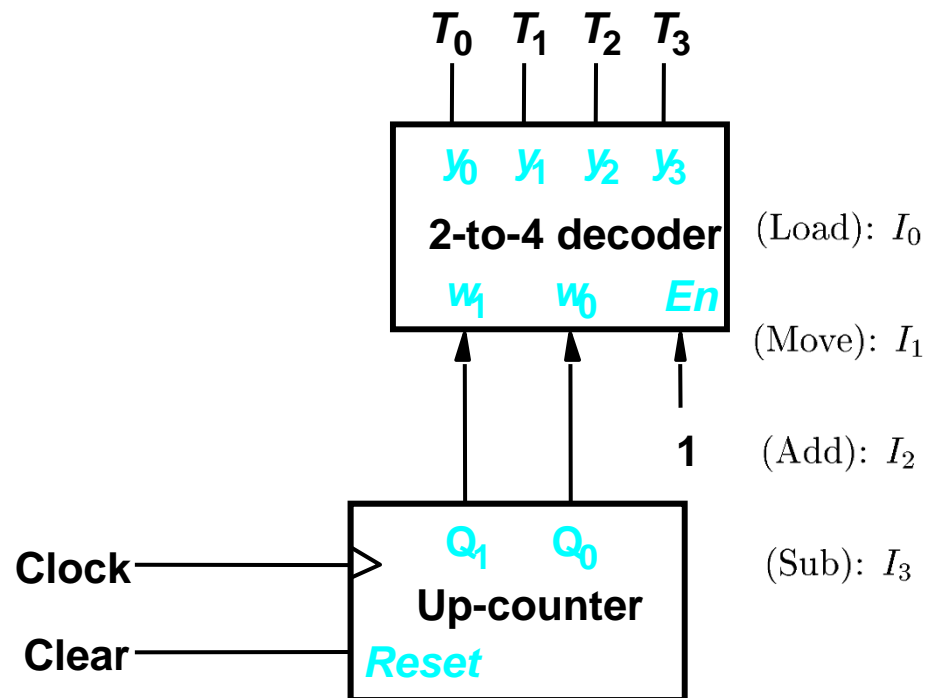


	T_1	T_2	T_3
(Load): I_0	$Extern, R_{in} = X,$ $Done$		
(Move): I_1	$R_{in} = X, R_{out} = Y,$ $Done$		
(Add): I_2	$R_{out} = X, A_{in}$	$R_{out} = Y, G_{in},$ $AddSub = 0$	$G_{out}, R_{in} = X,$ $Done$
(Sub): I_3	$R_{out} = X, A_{in}$	$R_{out} = Y, G_{in},$ $AddSub = 1$	$G_{out}, R_{in} = X,$ $Done$

Control Circuit

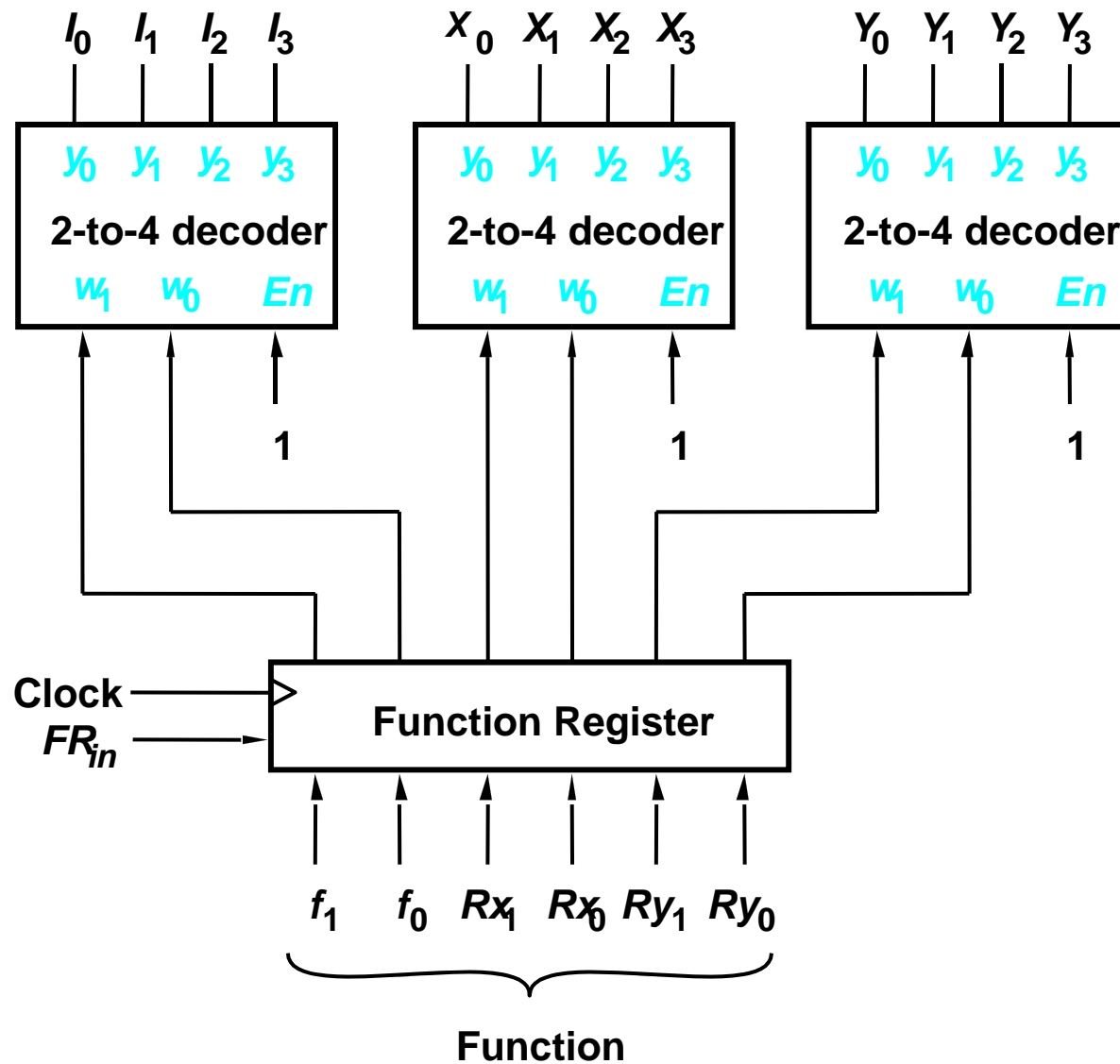


Reaction Timer

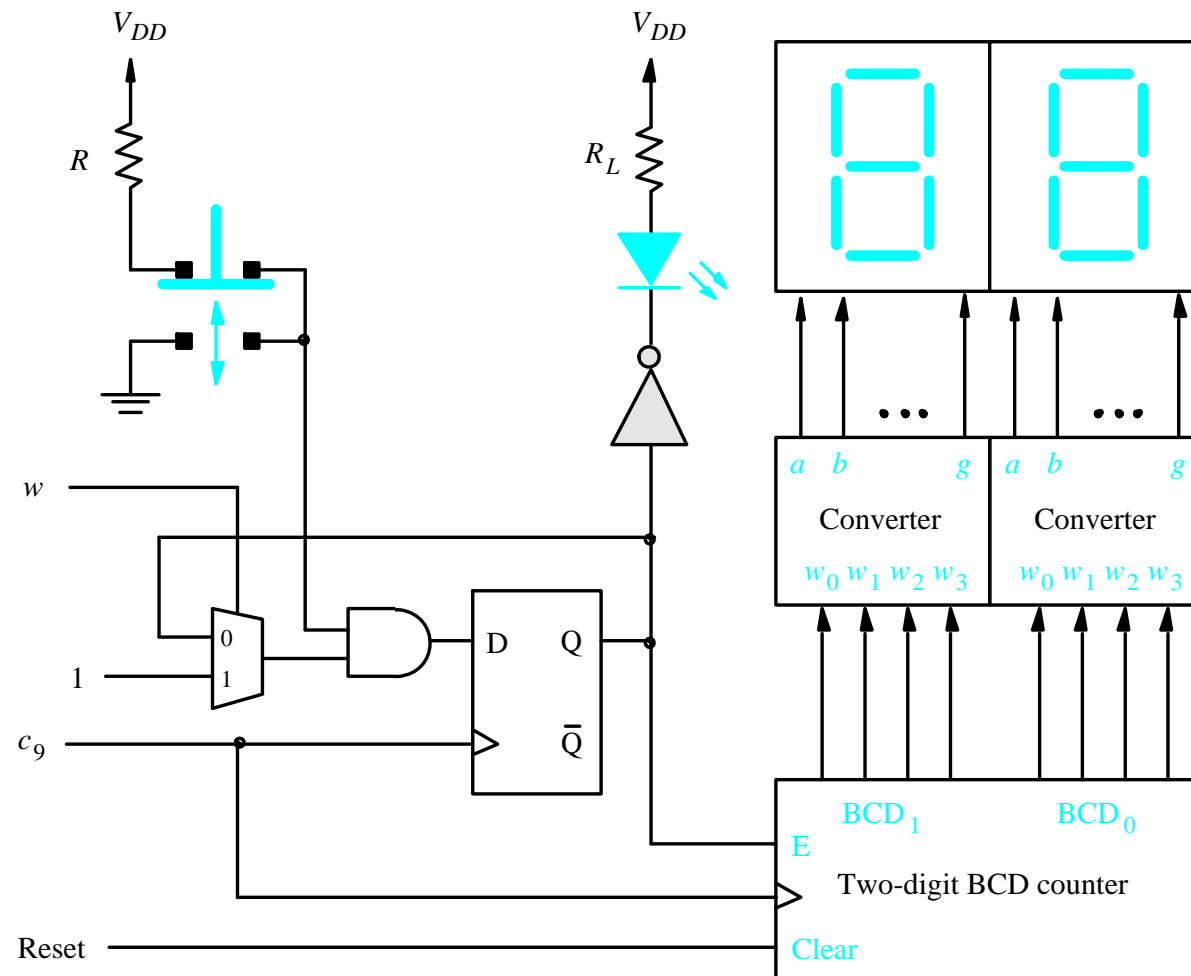

Timing Analysis

 - $T_{min} = t_{cQ} + t_{NOT} + t_{su}$
- $F_{max} = \frac{1}{T_{min}}$
- A simple flip-flop circuit
 - $T_{min} = 1.0 + 1.1 + 0.6 = 2.7ns$
 - $F_{max} = \frac{1}{2.7ns} = 370.37MHz$



Timing Analysis for a 4-bit Counter

- $$T_{min} = t_{cQ} + 3(t_{AND}) + t_{XOR} + t_{su}$$

$$= 1.0 + 3(1.2) + 1.2 + 0.6$$

$$= 6.4ns$$
- $$F_{max} = \frac{1}{6.4ns} = 156.25 \text{ MHz}$$

